

ADC Trends and Impact on SAR


ADC Architecture and Analysis




Jeffrey Fredenburg and Michael P. Flynn

www.eecs.umich.edu/~mpflynn

Improvement in ADC Energy Efficiency

 

Improvement in ADC Energy Efficiency

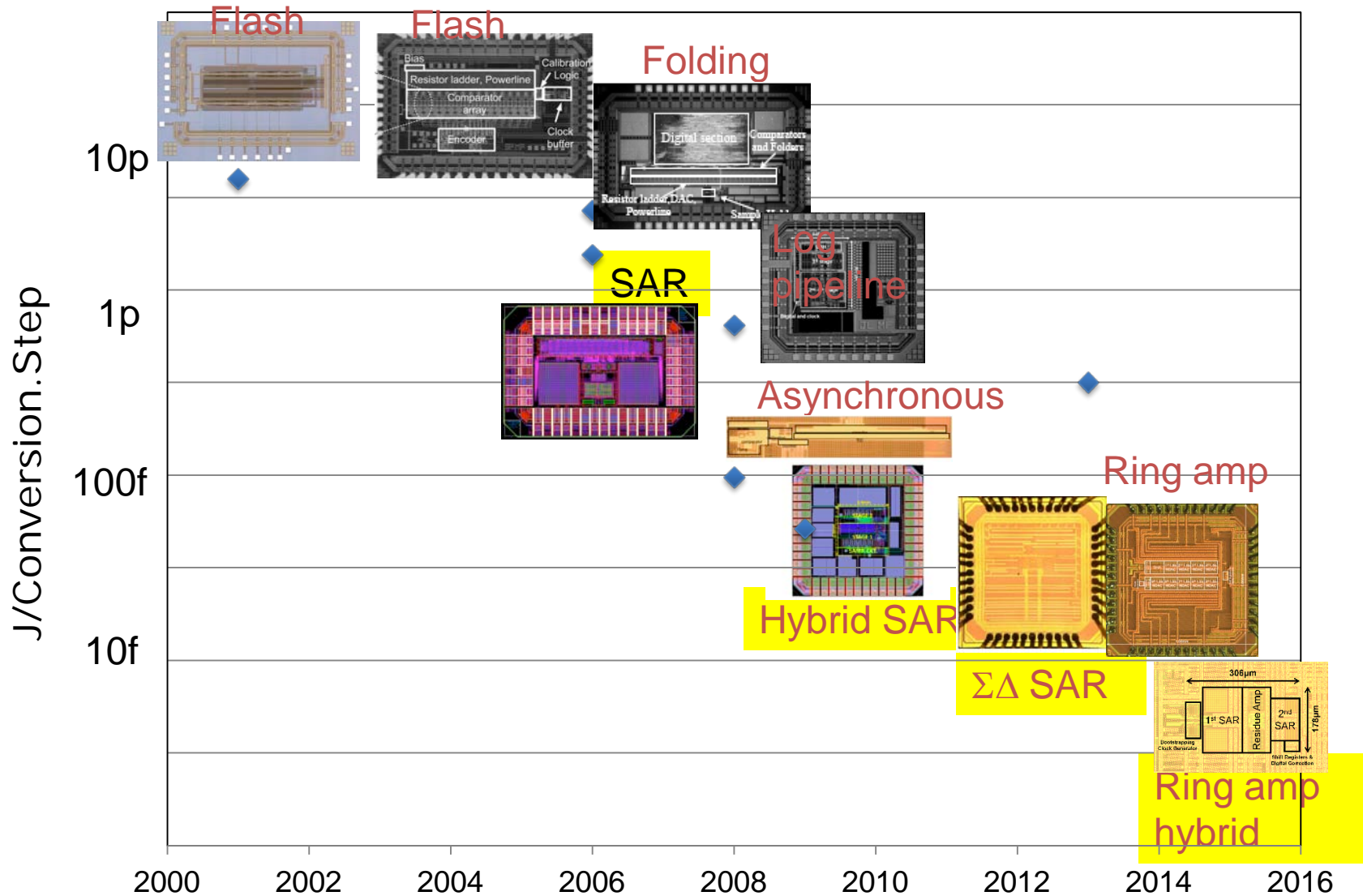

All-MOS Charge Redistribution Analog-to-Digital Conversion Techniques—Part I

JAMES L. McCREARY, STUDENT MEMBER, IEEE, AND PAUL R. GRAY, MEMBER, IEEE


 



Fig. 1. Conceptual 5-bit A/D converter illustrating the sample mode operation.

 

Overview

 
- Review of Trends
- Fundamentals
- Emerging Approaches






[Murmman, 2015]

Sampling Error

 


SNR-Jitter Limit

 

$$\Delta V \cong \frac{\partial V_{IN}}{\partial t} \Delta t$$

$$\Delta V \cong \pi V_{FS} f_{IN} \Delta t$$

SNR-Jitter Limit

 


$$\Delta V \cong \frac{\partial V_{IN}}{\partial t} \Delta t$$

$$\Delta V \cong \pi V_{FS} f_{IN} \Delta t$$


$$SNR \leq 20 \log_{10} \left[\frac{1}{\pi f_{IN} \sigma_{\Delta t}} \right]$$

Bandwidth-Jitter Limit

 


[Murmman, 2015]

Flash ADC

 

**Power related to
 $\sim 2^N$ Comparators**

Walden FOM

 


Power related to
 $\sim 2^N$ Comparators



$$FOM_W = \frac{Power}{BW \times 2^{ENOB}}$$

[Walden, 1994]


Energy-Resolution

 

[Murmman, 2015]

Better FOM

Thermal Noise Limited

 

Trade Power for SNR

Walden FOM

$$FOM_W = \frac{Power}{BW \times 2^{ENOB}}$$

Modified Walden FOM

$$\cancel{FOM_W} = \frac{\text{Power}}{BW \times 2^{ENOB}}$$

$$FOM_S = \frac{\text{Power}}{BW \times 4^{ENOB}}$$

A More Useful Metric

$$\cancel{FOM_W} = \frac{\text{Power}}{BW \times 2^{ENOB}}$$


$$FOM_S = \frac{\text{Power}}{BW \times 4^{ENOB}}$$



For ideal ADC


$$SNR = \frac{3}{2} \times 4^{ENOB}$$

‘Schreier’ FOM

 


[Murmann, 2015]

Power-Bandwidth

 

Digital Circuits

 

$$\Delta E_{dig} \approx \sum \alpha_i C_i V_{DD}^2$$



Overview

- Review of Trends
- Fundamentals
- Emerging Approaches

Capacitor Mismatch SNDR and Yield

[J. A. Fredenburg and M. P. Flynn, "Statistical Analysis of ENOB and Yield in Binary Weighted ADCs and DACs with Random Element Mismatch," *IEEE TCAS I* July 2012]

Cap Accuracy Fundamentals

  


**Cap Mismatch
causes DNL/INL
errors**

First Find DNL

N bit binary DAC

$$V_{DAC} = \sum_{i=1}^N b_i 2^{i-1} (1 + \gamma_i) \Lambda$$

LSB size

 

Error of binary
cap i

DNL Pattern

3 bit binary DAC

$$D_3 = \{d_1 \quad d_2 \quad d_1 \quad d_3 \quad d_1 \quad d_2 \quad d_1\}$$

Error of due to
LSB cap

- Only N unique DNL errors for N bit DAC

DNL at Code i

Already:

$$V_{DAC} = \sum_{i=1}^N b_i 2^{i-1} (1 + \gamma_i) \Lambda$$

DNL

$$d_i = 2^{i-1} \gamma_i - \sum_{j=1}^{i-1} 2^{j-1} \gamma_j$$




**Unique DNL
values**

Noise Associated with Mismatch

Ideal ADC:

$$V_{noise}^2 = \frac{\Lambda^2}{12}$$

Non-ideal ADC:

 

$$V_{noise}^2 = \frac{\Lambda^2}{12} + \frac{\Lambda^2}{2^N} \sum_{i=0}^{2^N-1} INL_i^2$$

Noise Associated with Mismatch


$$V_{noise}^2 = \frac{\Lambda^2}{12} + \frac{\Lambda^2}{2^N} \sum_{i=0}^{2^N-1} INL_i^2$$

$$INL_i = \sum_{j=1}^i DNL_j$$

Using DNL pattern (folding symmetry)

$$V_{noise}^2 = \frac{\Lambda^2}{12} + \frac{\Lambda^2}{4} \left[\gamma_0^2 + \sum_{i=1}^N \left(2^{i-1} \gamma_i \right)^2 \right]$$

Cap Mismatch Noise

 

Noise vs mismatch

$$V_{noise}^2 = \frac{\Lambda^2}{12} + \frac{\Lambda^2}{4} \left[\gamma_0^2 + \sum_{i=1}^N \left(2^{i-1} \gamma_i \right)^2 \right]$$

INL vs Cap Error

$$\text{Mean} (INL^2) = \frac{1}{4} \gamma_0^2 + \frac{1}{4} \sum_{i=1}^N \left(2^{i-1} \gamma_i \right)^2$$

ENOB vs Cap Mismatch

$$V_{noise}^2 = \frac{\Lambda^2}{12} + \frac{\Lambda^2}{4} \left[\gamma_0^2 + \sum_{i=1}^N \left(2^{i-1} \gamma_i \right)^2 \right]$$

$$ENOB = N - \log_4 \left[1 + 3\gamma_0^2 + 3 \sum_{i=1}^{N-1} \left(2^{i-1} \gamma_i \right)^2 \right]$$

$$\gamma_i = \frac{1}{2} \left(\gamma_{i,p} + \gamma_{i,m} \right) \quad i \in \{0, \dots, N-1\}$$


For uniformly distributed input

ENOB vs Cap Mismatch

Sinusoidal input


$$ENOB = N - \log_4 \left[1 + 3\alpha\gamma_0^2 + 3\alpha \sum_{i=1}^{N-1} \left(2^{i-1} \gamma_i \right)^2 \right]$$
 
$$\alpha = \frac{3(4-\pi)}{\pi} \cong 0.8197$$



- First closed form expression for ENOB

Yield vs Cap Matching

 

$$P(ENOB > ENOB_{MIN}) = P(X < 4^{N-ENOB_{MIN}} - 1)$$

$$X = \sum_{i=0}^{N-1} \eta_i$$

$$F_X(x) = \int_0^x \int_0^{\frac{\pi}{2}} \dots \int_0^{\frac{\pi}{2}} \sum_{i=1}^{N/2} B_i e^{-\lambda_i t} d\theta_1 \dots d\theta_{N/2} dt$$

$$B_i = \left[(\lambda_i - s) \prod_{j=1}^{N/2} \left(\frac{A_j}{\lambda_j - s} \right) \right] \Big|_{s \rightarrow \lambda_i}$$

$$A_i = \frac{1}{\pi \sigma_{2i-2} \sigma_{2i-1}} \quad \lambda_i = \frac{\cos^2 \theta_i}{2 \sigma_{2i-2}^2} + \frac{\sin^2 \theta_i}{2 \sigma_{2i-1}^2}$$

- First closed form expression for ENOB CDF
 - Can take weeks for 14 bit

Useful Designer Equations

Simple Yield Equation


```
% Parameter Values  
N = 9; SIGMA = 0.1; ENOB_MIN = 7.7;  
YIELD = 0.95; k = 7.944; b = 13.146;
```

```
% Yield Calculation  
X=4^(N-ENOB_MIN)-1;  
Z=X/2^N/SIGMA^2;  
YIELD=gammainc(b*sqrt(Z),k)
```

Simple Mismatch Equation


```
% Sigma Calculation  
X=4^(N-ENOB_MIN)-1;  
Z=(gammaincinv(YIELD,k)/b)^2;  
SIGMA=sqrt(X/Z/2^N)
```

Accuracy of Design Equation

 


Predicted Yields are within $\pm 0.2\%$
with simple design equation

12 bit Array Example

 


DAC Switching Energy

DAC Switching Energy

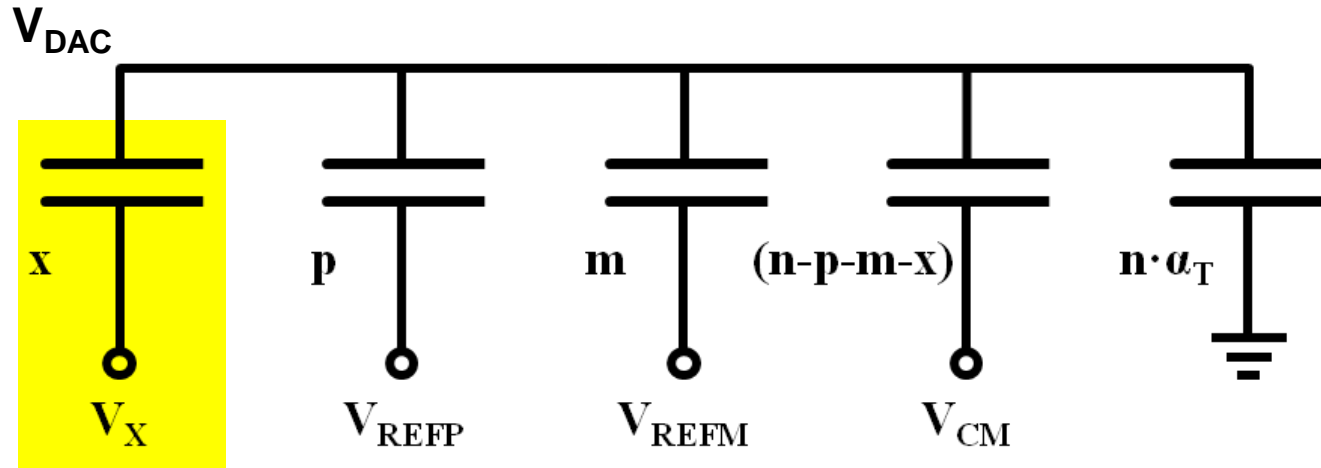


Switch x unit caps

Unit Cap Model

 

$$\Delta E_Y = [C_u (\Delta V_Y - \Delta V_{DAC}) + C_p \Delta V_Y] V_Y$$

Unit Cap Model

 

$$\Delta V_{\text{DAC}} = \frac{x}{n(1 + \alpha_T)} \Delta V_Y$$

$$\Delta E_Y = \left[C_u (\Delta V_Y - \Delta V_{\text{DAC}}) + C_p \Delta V_Y \right] V_Y$$

Energy from References

$$\Delta E = \Delta E_{\text{Independent}} + \Delta E_{\text{Dependent}}$$

$$\Delta E_{\text{Independent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[x(1 + \alpha_p) - \frac{x^2}{n(1 + \alpha_T)} \right]$$

$$\Delta E_{\text{Dependent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[\frac{x(m - p)}{n(1 + \alpha_T)} \right] \text{sign}(\Delta V_{\text{X,DIFF}})$$




**Function of DAC
switching**

Energy from References

$$\Delta E = \Delta E_{\text{Independent}} + \Delta E_{\text{Dependent}}$$

$$\Delta E_{\text{Independent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[x(1 + \alpha_p) - \frac{x^2}{n(1 + \alpha_T)} \right]$$
 
$$\Delta E_{\text{Dependent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[\frac{x(m - p)}{n(1 + \alpha_T)} \right] \text{sign}(\Delta V_{\text{X,DIFF}})$$




Energy from References

$$\Delta E = \Delta E_{\text{Independent}} + \Delta E_{\text{Dependent}}$$

$$\Delta E_{\text{Independent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[x(1 + \alpha_p) - \frac{x^2}{n(1 + \alpha_T)} \right]$$
 
$$\Delta E_{\text{Dependent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[\frac{x(m - p)}{n(1 + \alpha_T)} \right] \text{sign}(\Delta V_{\text{X,DIFF}})$$



Dependent
averages
to 0

Adding for all DAC Steps

$$\Delta E = \Delta E_{\text{Independent}} + \Delta E_{\text{Dependent}}$$

$$\Delta E_{\text{Independent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[x(1 + \alpha_p) - \frac{x^2}{n(1 + \alpha_T)} \right]$$

$$\Delta E_{\text{Dependent}} = \frac{1}{8} C_u V_{\text{FS}}^2 \left[\frac{x(m - p)}{n(1 + \alpha_T)} \right] \text{sign}(\Delta V_{\text{X,DIFF}})$$

Add Independent terms for N bit complete cycle

$$\Delta E_{\text{DAC}} \cong \frac{1}{16} 2^N C_u (1 + \alpha_p) V_{\text{FS}}^2 \left[1 - \frac{1}{3(1 + \alpha_T)(1 + \alpha_p)} \right]$$

DAC Energy vs SNR

Complete N-bit cycle



$$\Delta E_{DAC} \cong \frac{1}{16} 2^N C_u (1 + \alpha_p) V_{FS}^2 \left[1 - \frac{1}{3(1 + \alpha_T)(1 + \alpha_p)} \right]$$

Energy vs SNR


$$\Delta E_{DAC} \cong \frac{kT}{2} \cdot SNR_{DAC} \cdot \left[(1 + \alpha_P) - \frac{1}{3(1 + \alpha_T)} \right]$$

Comparator Energy Consumption

Dynamic Comparator

  


Latch

 


Diff Pair

Reset Energy

 


$$\Delta E_{\text{RESET}} = C_L V_{\text{DD}}^2$$

Simplified Model for Amplification

 

$$\Delta E_{\text{LATCH}} \leq I_{\text{DD,MAX}} V_{\text{DD}} \Delta t$$

Simplified Model for Amplification


 


$$I_{DD,MAX} \cong gm |V_{GS} - V_{TH}| < \frac{1}{2} gm V_{DD}$$

$$\Delta E_{LATCH} \leq I_{DD,MAX} V_{DD} \Delta t$$

Estimate Time Δt


Use small signal model to estimate Δt

  

$$\Delta t = \frac{C_L}{2g_m} \operatorname{arcsinh} \left[\frac{2V_{DD}}{\Delta V_{IN}} \right]$$


$$\Delta E_{LATCH} \leq I_{DD,MAX} V_{DD} \Delta t$$

Latch Energy

 

$$\Delta E_{\text{LATCH}}(\Delta V_{\text{IN}}) = \frac{1}{4} C_L V_{\text{DD}}^2 \operatorname{arcsinh} \left[\frac{2V_{\text{DD}}}{\Delta V_{\text{IN}}} \right]$$


Latch Energy

 

$$\Delta E_{\text{LATCH}}(\Delta V_{\text{IN}}) = \frac{1}{4} C_L V_{\text{DD}}^2 \operatorname{arcsinh} \left[\frac{2V_{\text{DD}}}{\Delta V_{\text{IN}}} \right]$$

ΔV_{IN} ranges from 0 to $V_{\text{DD}}/2^m$

Total Energy for N Cycle SAR

 


$$\Delta E_{\text{COMP}} = \Gamma_N \cdot C_L V_{\text{DD}}^2$$

$$\Gamma_N = N + \underbrace{\frac{1}{2} \sum_{m=0}^{N-1} 2^m \int_0^{2^{-m}} \text{arcsinh} \frac{2}{u} du}_{\text{Amplification}}$$

Reset

Amplification

Total Energy for N Cycle SAR

 


$$\Delta E_{\text{COMP}} \cong \frac{2kT}{23} \left[\frac{2^N}{\sigma_{\text{COMP}}} \right]^2 [N^2 + 12N + 2]$$

$$\Delta E_{\text{COMP}} \cong \frac{2kT}{3} \cdot \text{SNR}_{\text{COMP}} \cdot [N^2 + 12N + 2]$$

Overview

- Review of Trends
- Fundamentals
- Emerging Approaches

Increase Resolution of SAR

 


Challenges

- Capacitor Matching
- DAC Energy consumption
- DAC speed
- Comparator Energy
 - i.e. Comparator Noise


Reduce Comparator Energy

SAR-Assisted Two-Stage Pipeline ADC

 

- Energy efficient hybrid for high resolution


Benefits vs SAR

 

- Low resolution SAR → comparator power ↓
- Pipelining → speed ↑
- Large first stage resolution → linearity ↑


**Reduce DAC Switching
by splitting DAC**

First DAC Noise Requirement

 


- DAC residue: **13b** kT/C ($C_{S1}=2\text{pF}$)

First DAC Noise Requirement

 


- DAC residue: **13b** kT/C ($C_{S1}=2\text{pF}$)
- 1st stage ADC: **6b** kT/C noise

Divided First Stage DAC

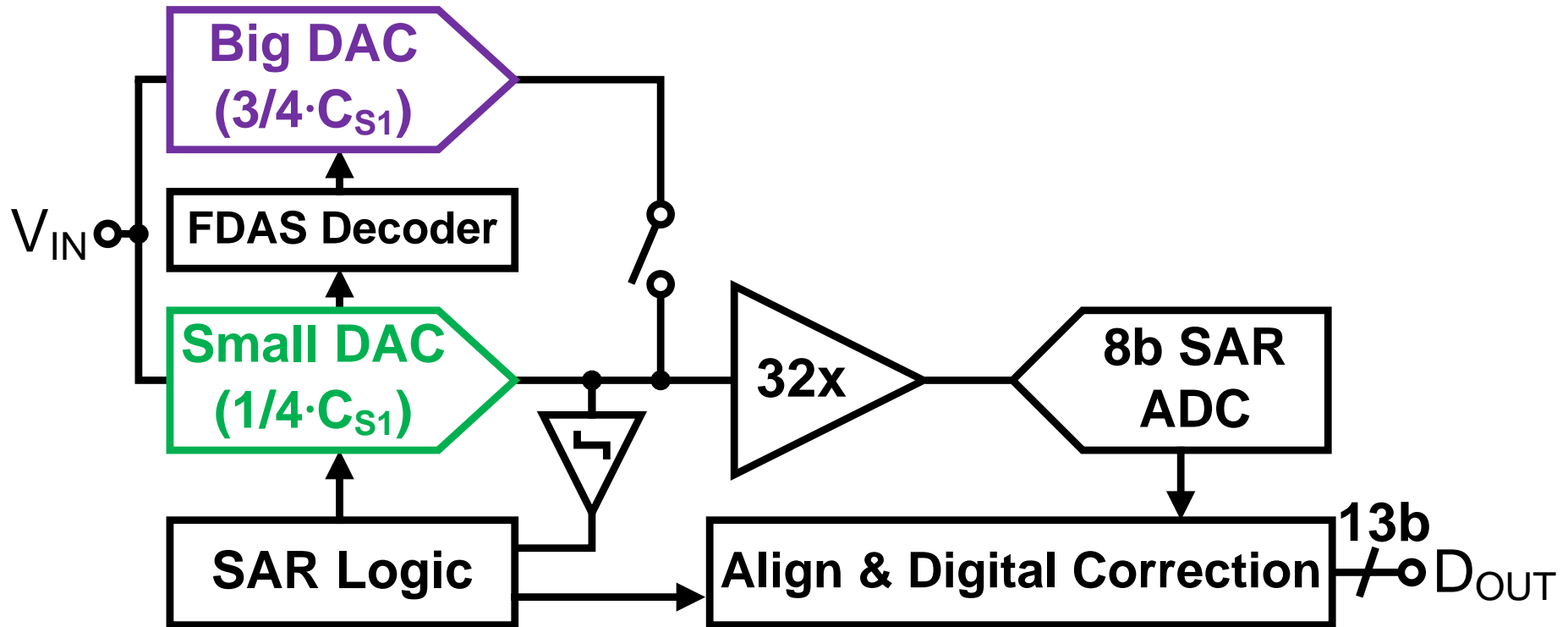

- Reduce DAC switching energy & mismatch


Big DAC Residue Generation (FDAS)

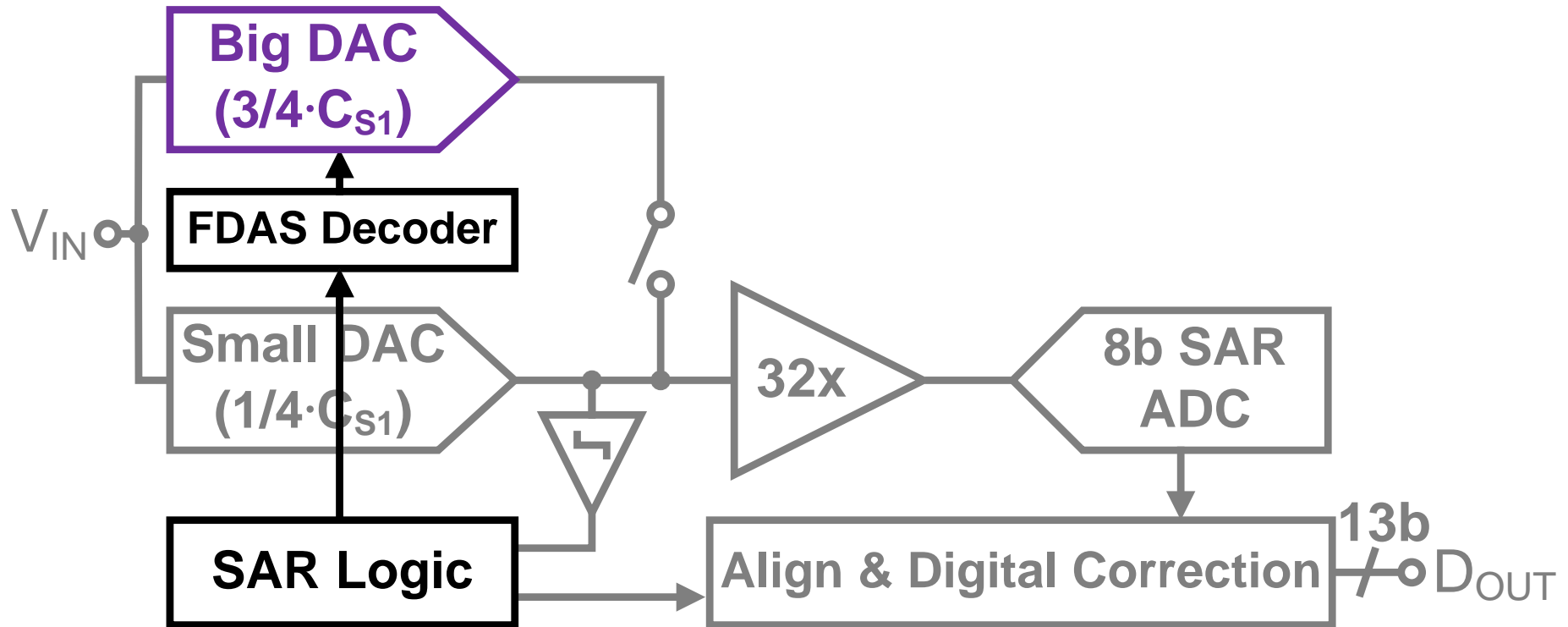

➤ Floated Detect-and-Skip (FDAS)

- Energy efficient switching using small DAC SAR ADC result

Merge Big & Small DAC Residues

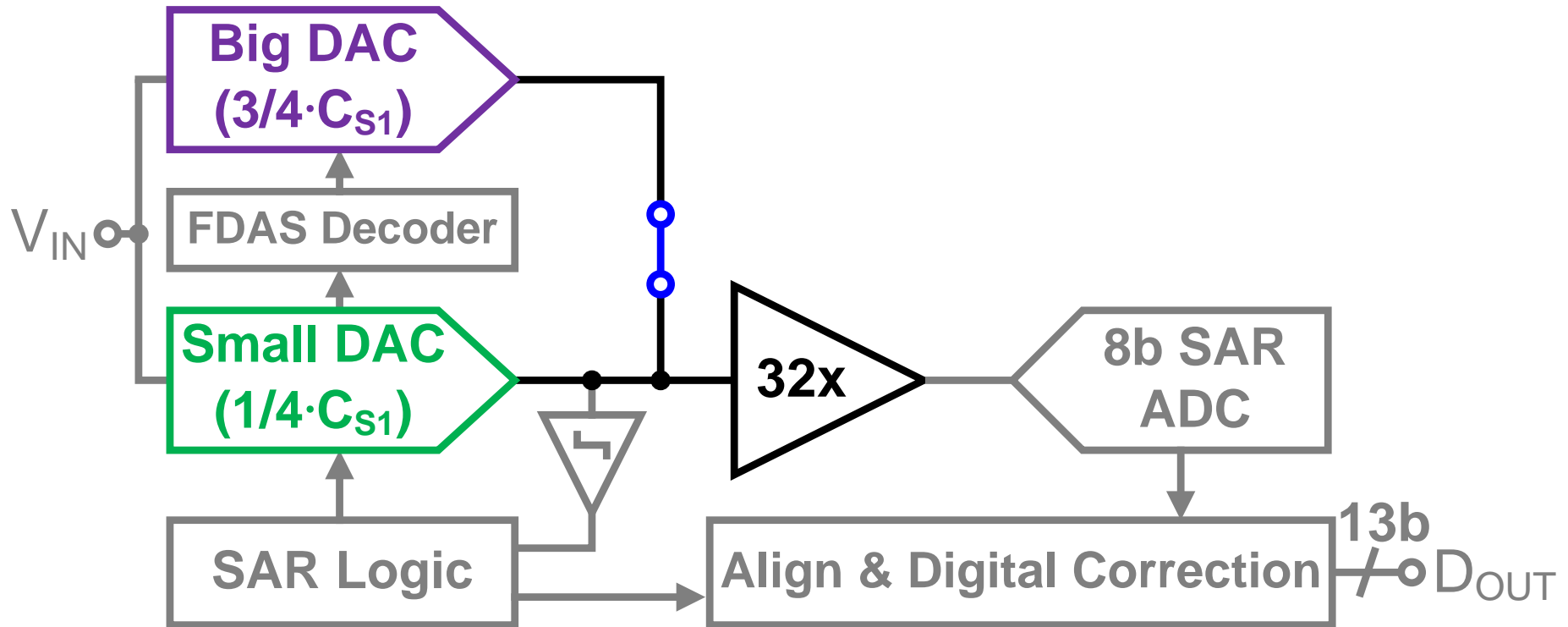


- Meets 13b kT/C noise requirement
- Mismatch between big and small DACs
 - Corrected by 1b stage redundancy

Floated Detect-and-Skip DAC Switching

Switching Energy Reduction


Big DAC Switching Energy Loss

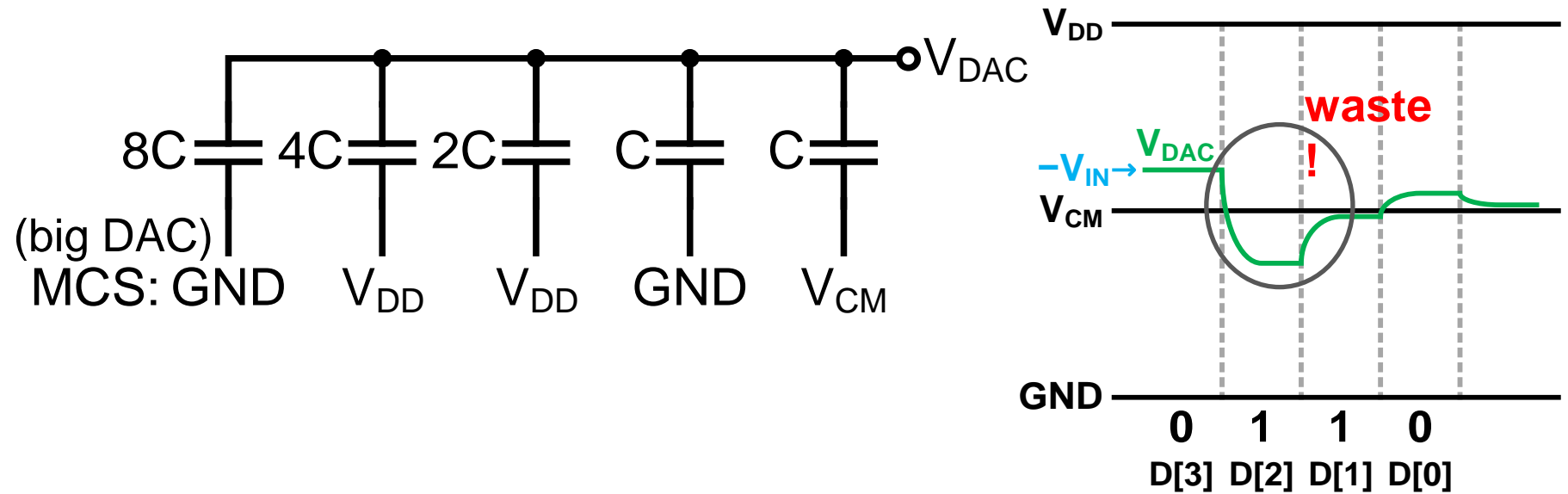

➤ Binary search

- Opposite direction switching → **waste!**

Detect-and-Skip (DAS) Switching

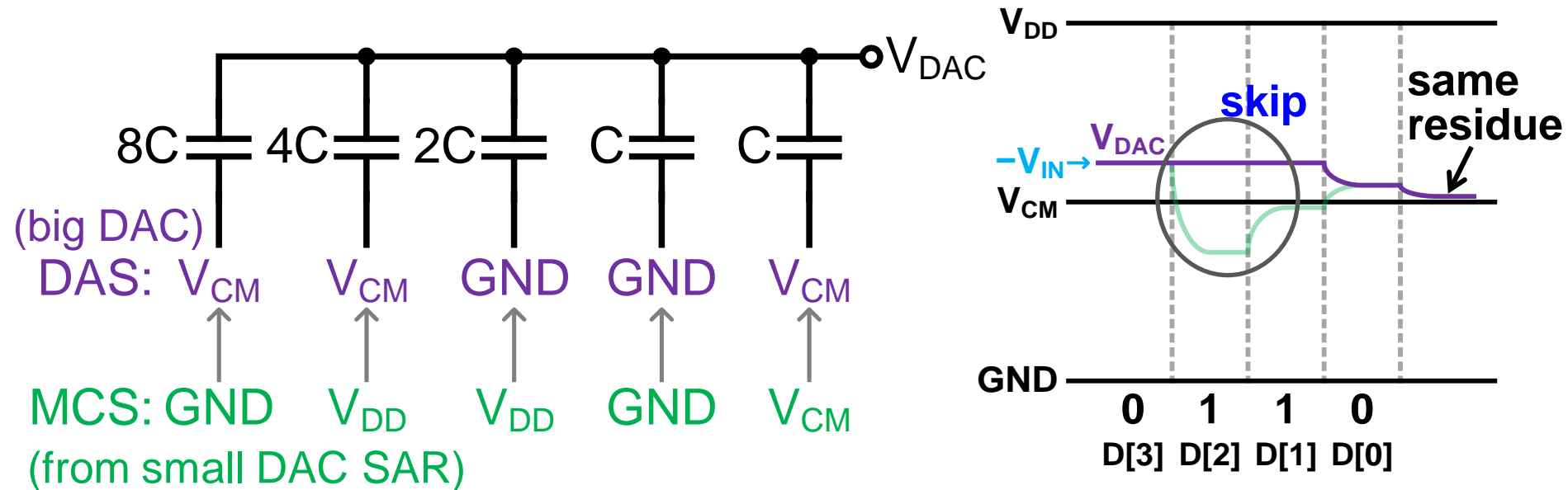


➤ **Skips opposite direction switching**

☺ Saves energy


Big DAC Switching Energy Loss (2)

➤ Successive switching

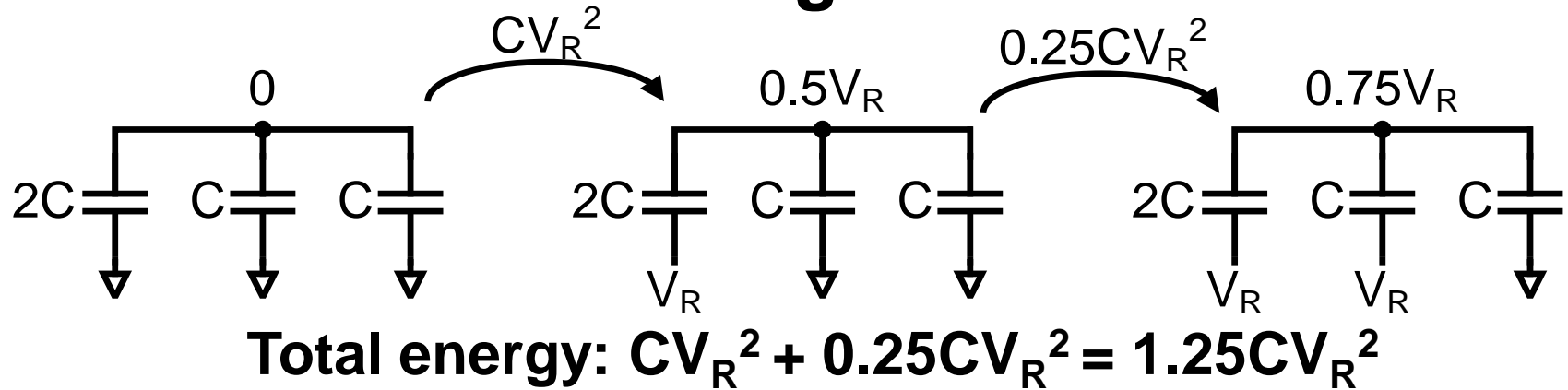


Big DAC Floated DAS Switching

➤ Successive switching

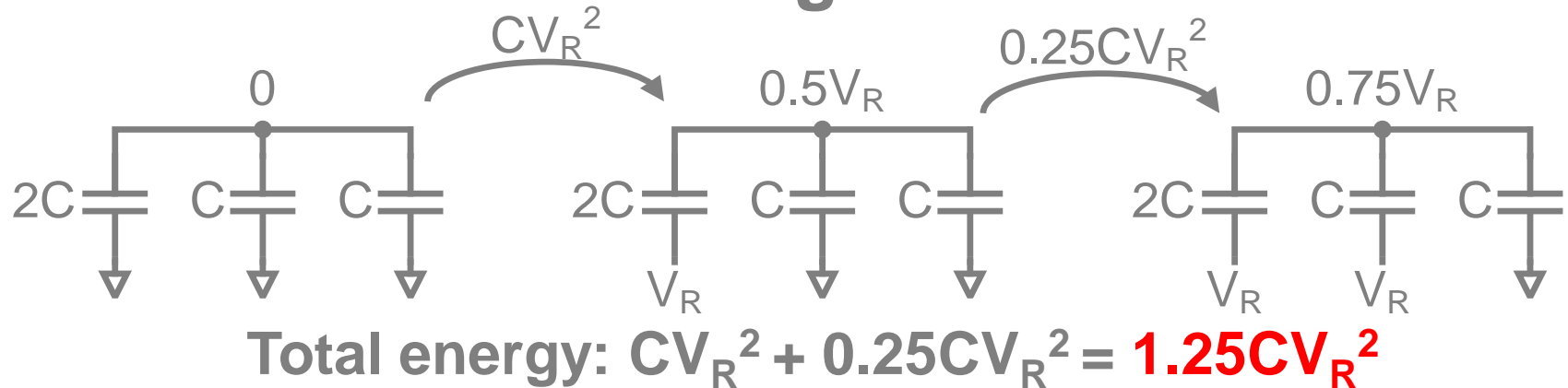


➤ Floated DAS switching

 


☺ Save energy without additional settling time

Big DAC Switching Energy Comparison

 

➤ Big DAC MCS vs. big DAC FDAS

1st DAC Switching Energy Comparison

 

➤ **MCS vs. small DAC MCS + big DAC FDAS**


Floated Detect-and-Skip DAC Switching

DAC Mismatch Reduction

MCS Worst Case INL

➤ MCS

[GND, V_{DD} , V_{DD} , V_{DD} , V_{DD} ,
 V_{DD} , V_{CM}]




Worst case switching

[V_{DD} , GND, GND, GND, GND, GND, V_{CM} ,
MSB, LSB, Dummy]

MCS & FDAS Worst Case INL

➤ MCS


[GND, V_{DD} , V_{DD} , V_{DD} , V_{DD} ,
 V_{DD} , V_{CM}]



[V_{DD} , GND, GND, GND, GND, GND, V_{CM}
]

➤ FDAS

[GND, V_{CM} , V_{CM} , V_{CM} , V_{CM} ,
 V_{CM} , V_{CM}]




[V_{CM} , GND, GND, GND, GND, GND, V_{CM}
]

MCS & FDAS Worst Case INL

➤ MCS


$[\text{GND}, V_{DD}, V_{DD}, V_{DD}, V_{DD}, V_{DD}, V_{CM}]$



$[V_{DD}, \text{GND}, \text{GND}, \text{GND}, \text{GND}, \text{GND}, V_{CM}]$

➤ FDAS

$[\text{GND}, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}]$



$[V_{CM}, \text{GND}, \text{GND}, \text{GND}, \text{GND}, \text{GND}, V_{CM}]$

also

$[V_{DD}, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}]$



$[V_{CM}, V_{DD}, V_{DD}, V_{DD}, V_{DD}, V_{DD}, V_{CM}]$

Worst Case INL Improvement

➤ MCS

$[GND, V_{DD}, V_{DD}, V_{DD}, V_{DD}, V_{DD}, V_{CM}]$

↕

$[V_{DD}, GND, GND, GND, GND, GND, V_{CM}]$

➤ FDAS

$[GND, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}]$

↕

$[V_{CM}, GND, GND, GND, GND, GND, V_{CM}]$

also

↕


$[V_{DD}, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}, V_{CM}]$

➤ Voltage swing halved ($V_{DD} \rightarrow 1/2 \cdot V_{DD} (=V_{CM})$)

😊 Worst case INL halved


Similar work: [J. Guerber /SCAS 2012]

Simulated RMS INL Comparison

 

➤ Big DAC MCS vs. big DAC FDAS


Simulated RMS INL Comparison

 


➤ MCS 1st DAC vs. new1st DAC

Prototype SAR Assisted Pipeline

Ring Amp

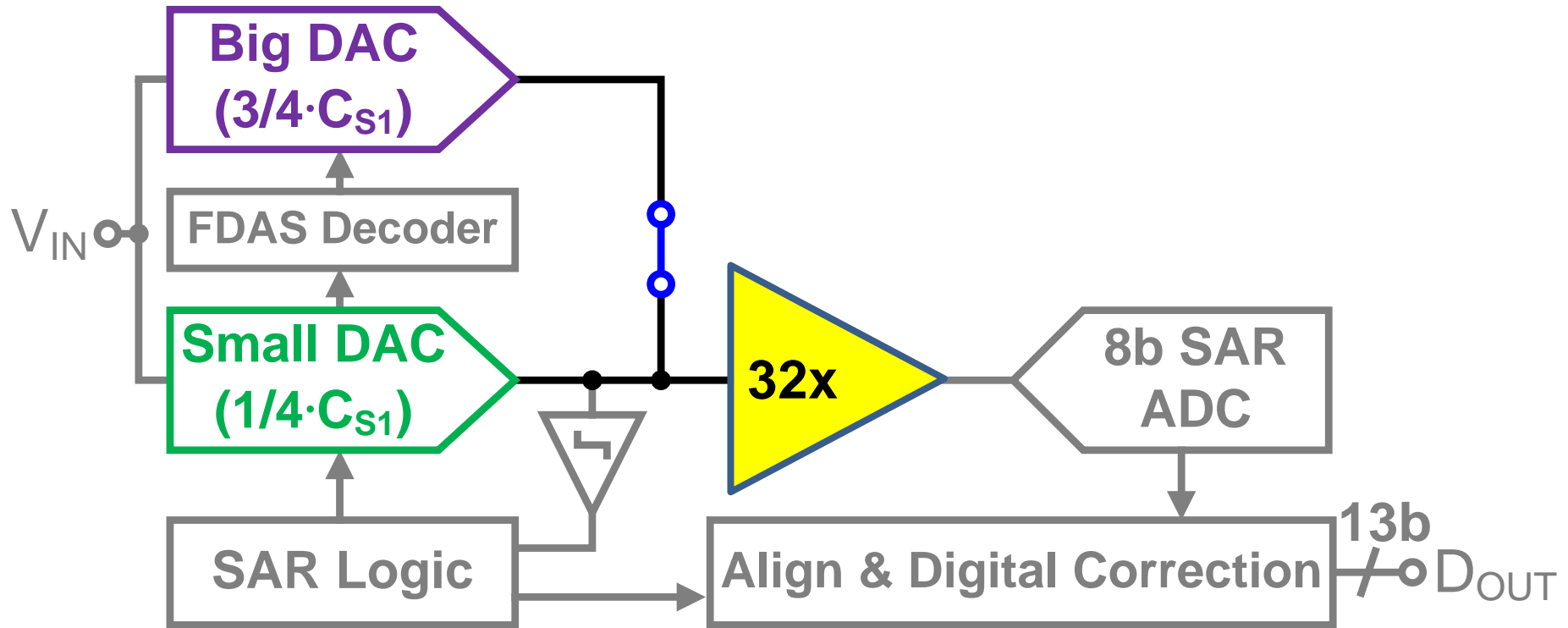


ADC Die Photo

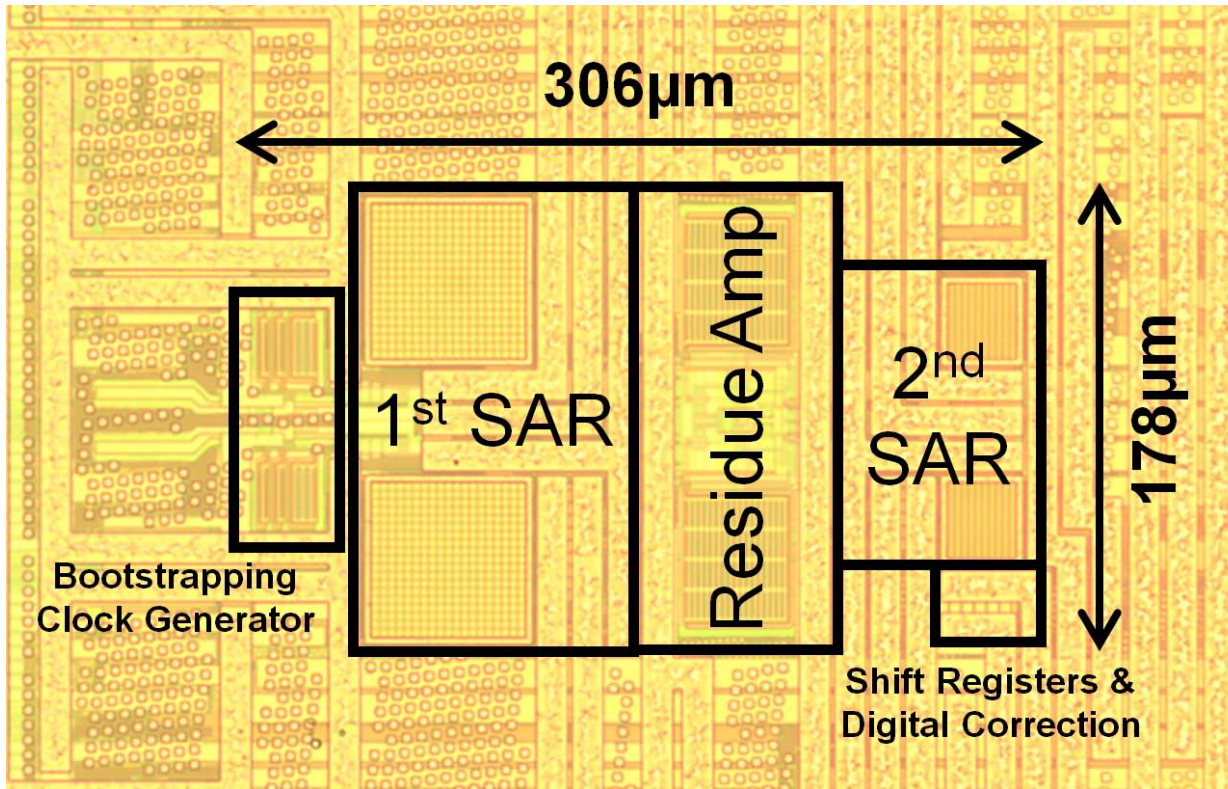


➤ **50MS/s, 11.5b ENOB, 1mW**

■ 65nm CMOS: 0.054mm^2

Dynamic Performance

 

FoM_s Comparison

 


[B. Murmann, ADC Performance Survey 1997-2014]


Noise-Shaping SAR ADC

[Fredenburg and Flynn ISSCC 2012, JSSC 12]

1st Order $\Sigma\Delta$ Modulator

 


Digital Conversion

 


$$D_{OUT} = V_{IN} + Q$$

Conventional DAC Residue

 


$$V_{RES} \neq D_{OUT} - V_{IN}$$

Extended DAC Residue

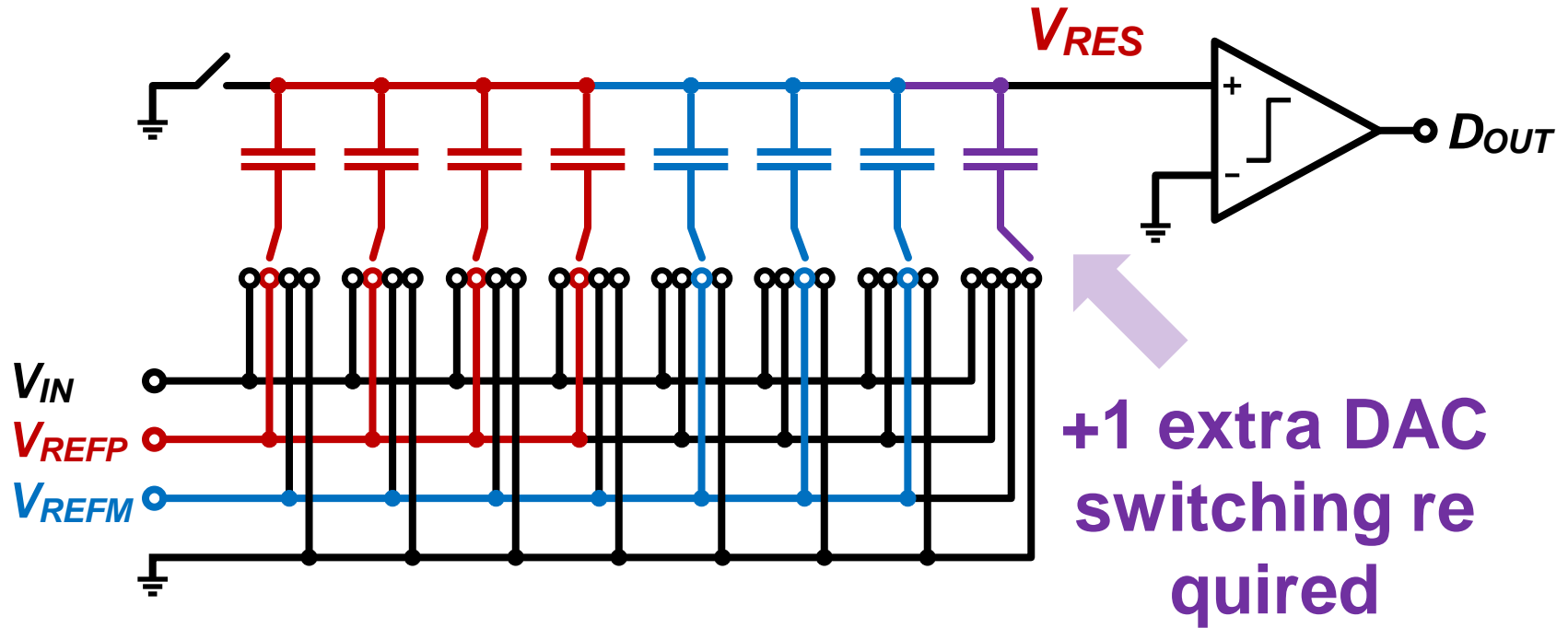


$$V_{RES} = D_{OUT} - V_{IN}$$

DAC Residue

 


$$V_{RES} = D_{OUT} - V_{IN} + V_{N,COMP}$$

Simple SAR Noise Shaping

 


$$D_{OUT}(k) = V_{IN}(k) + Q(k) - V_{RES}(k-1)$$

Simple SAR Noise Shaping

 



$$V_{RES}(k) = D_{OUT}(k) - V_{IN}(k)$$

Simple SAR Noise Shaping

 


$$D_{OUT}(z) = V_{IN}(z) + \frac{1}{1+z^{-1}} [Q(z) + V_{N,COMP}(z)]$$

How To Do It

  


Passively Sample Residue

Signal Flow Diagram

 


Advantages

 


- ✓ Shapes quantization noise
- ✓ **Also shapes comparator noise**

Disadvantages

 


✗ Small resolution improvement

Improved SAR Noise Shaping

 


Improve the Integration Filter

 


One good filter **➔** Two OK filters

Even Better Noise Shaping

 


Adding this simple switch-capacitor FIR filter enhances the overall noise shaping

Better Noise Transfer Function

 

- ✓ Enhances a lossy IIR filter
- ✓ Widens attenuation bandwidth

Die Micrograph

 

65nm CMOS

0.03 mm²

11 MHz BW

800 μW

10 bit ENOB

36 fJ/conv-step

Conclusions

- **SAR ADCs are driving ADC efficiency**
- **Fundamentals of yield and power**
- **New architectures exploit SAR for higher performance**