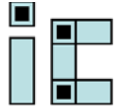


Scaling Analog Circuits into Deep Nanoscale CMOS: Obstacles & Ways to Overcome Them

Peter Kinget

Analog & RF  Design Research



Outline

- Why ...
 - We have no choice
 - We can enable novel applications
- What are the obstacles
when scaling analog circuits
- How ...
 - Solutions for analog circuits in nanoscale CMOS:
 - Scale V_{DD} , new architectures, use digital gates
 - Leveraging nanoscale CMOS in different ways
 - Novel circuits and analog information representation
- Outlook & Conclusions

Why?

What drives the need for scaling
analog & RF circuits?

It's All About The Interfaces...

World is Analog * ^ % ! ! & * \$



Wireless

Display

Touch

Analog/RF Interfaces

Digital Core

Audio

Battery Mgmt



Wired /
Computer

'Analog & RF connect the bits to life'


Why?

Scaled CMOS enables the creation
of new classes of devices and
applications

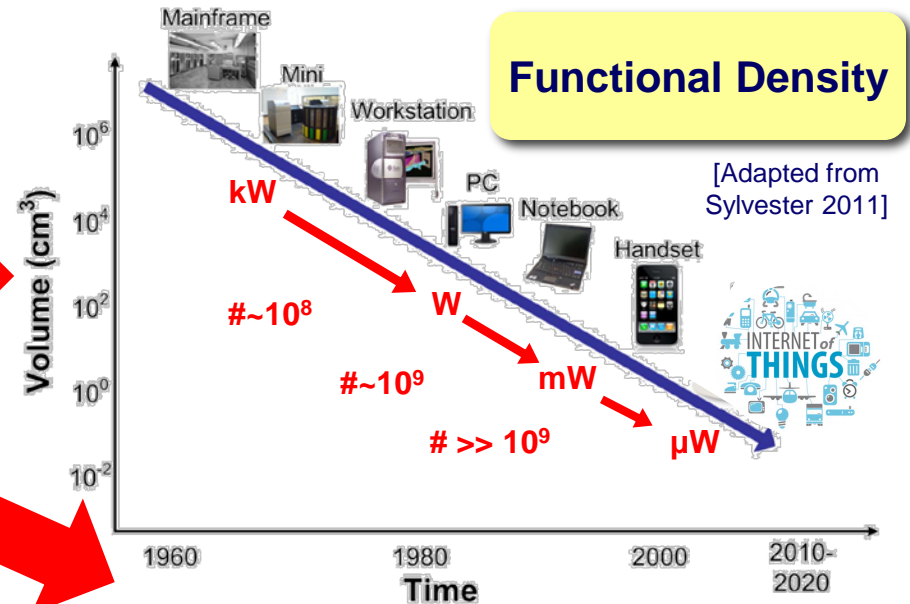 
50 Years of Moore's Law: A Different Look




Short Range Wireless:
Energy per bit

 

 Analog-to-Digital Conversion:
Energy per Conv.




Computation:
Energy per Operation


 


Scaling & Circuits

CMOS Scaling

 

Device speed & density ↑

  

Supply Voltage ↓

CMOS scaling is targeted
at improving
digital performance

[ITRS CMOS Roadmap]

Performance & Scaling


- **Digital Performance Metrics**

$$Power \propto f_{CLK} C_{gates} V_{DD}^2$$

$$Area \propto L_{min}^2$$

Device size scaling
helps directly!

- **Analog Performance Metrics**
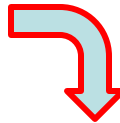
$$SNR \propto \left(\frac{V_{RMS}^2}{4 \cdot kT \cdot \Gamma \cdot 1/g_m \cdot BW} \right)$$


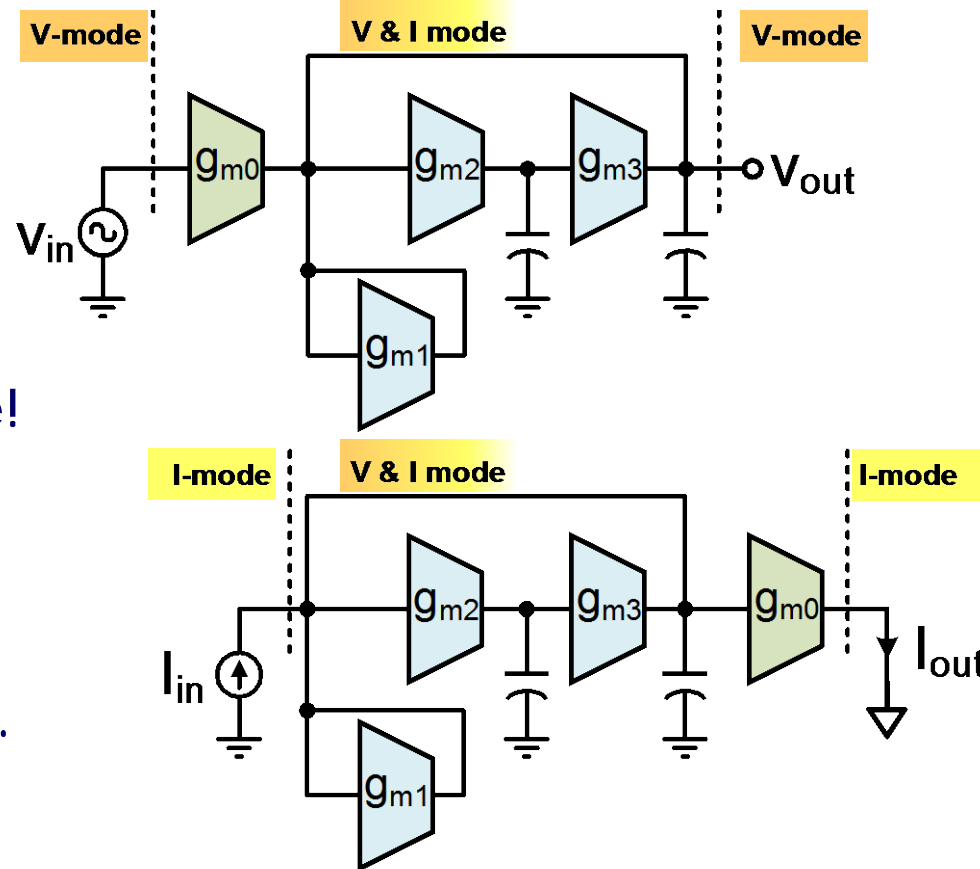
$$Power \propto kT \cdot BW \cdot SNR \cdot \left(\frac{1}{V_{DD}} \right) \cdot \frac{\Gamma}{(g_m/I)}$$

Device size scaling
does not help directly!


Scaling means **supply reduction**, gain reduction, more leakage, more substrate & supply interference, more mismatch, more 1/f noise ...

We Are Stuck With Voltages

- MOS transistor is V-I converter
 - Only a square i-v relationship (at best ...)
 - Always current & voltage mode!
 - Sub-threshold
 - Exponential i-v
 - But, low f_T
- Power supplies are voltage ...
- Most sensors, signal sources are voltage ...
- But, there are some new interesting opportunities



V_{DD} Scaling

 


[Kinget ESSCIRC13]

Scaling the Analog V_{DD}

What to expect

A- V_{DD} Scaling: Constant g_m/I_D

 

Constant BW scaling

$$\sigma^2(V_n) \approx kT/C$$

$$\sigma^2(V_{OS}) \approx A_{VT}^2/(WL)$$

$$SNR \approx V_{out}^2/\sigma^2(V_n)$$


$$Acc. \approx V_{out}^2/\sigma^2(V_{OS})$$

$$P = I_{BIAS} V_{DD}$$

Area

Caution: only first order approximations!!

A- V_{DD} Scaling: Constant g_m/I_D

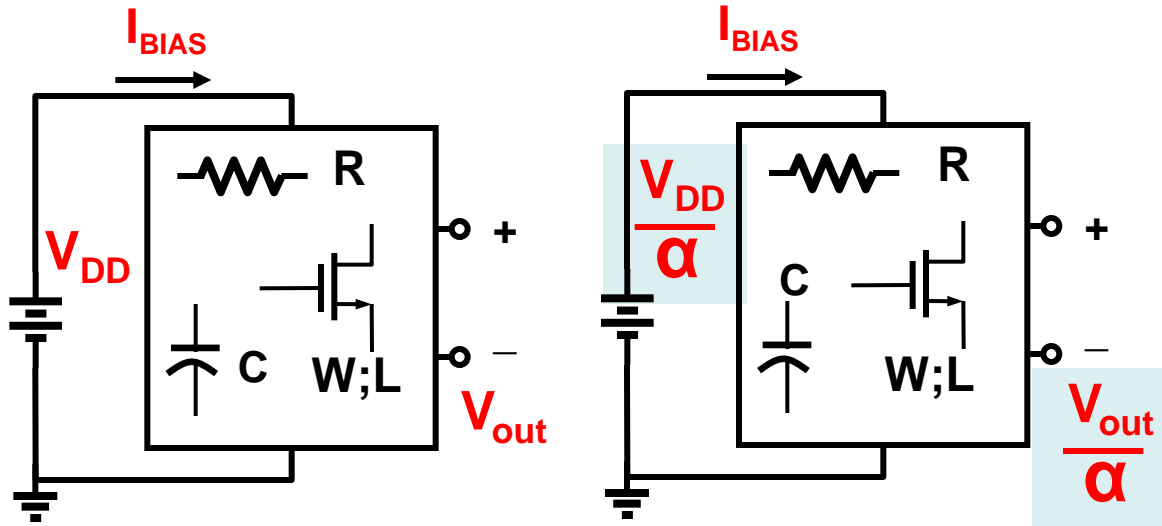



Constant BW scaling

$\sigma^2(V_n) \approx kT/C$	$\sigma^2(V_n)$
$\sigma^2(V_{OS}) \approx A_{VT}^2/(WL)$	$\sigma^2(V_{OS})$
$SNR \approx V_{out}^2/\sigma^2(V_n)$	SNR / α^2
$Acc. \approx V_{out}^2/\sigma^2(V_{OS})$	$Accuracy / \alpha^2$
$P = I_{BIAS} V_{DD}$	P / α
Area	Area

Caution: only first order approximations!!





A- V_{DD} Scaling: Constant g_m/I_D

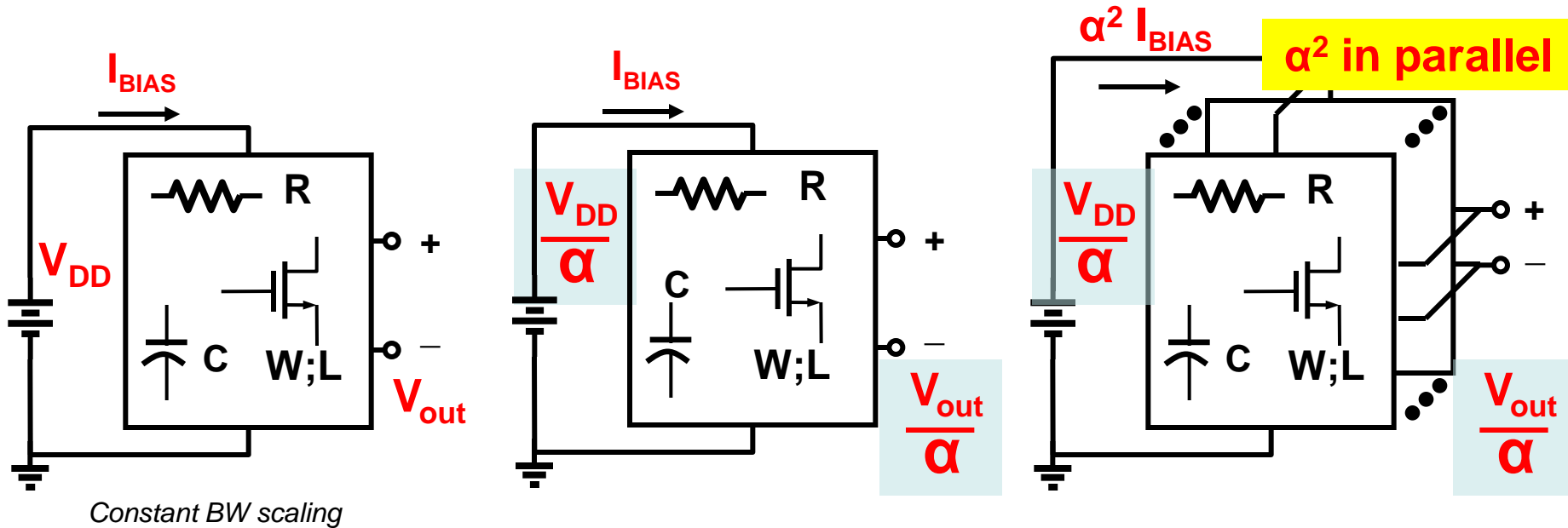

$\sigma^2(V_n) \approx kT/C$	$\sigma^2(V_n)$	$\sigma^2(V_n) / \alpha^2$
$\sigma^2(V_{OS}) \approx A_{VT}^2/(WL)$	$\sigma^2(V_{OS})$	$\sigma^2(V_{OS}) / \alpha^2$
$SNR \approx V_{out}^2/\sigma^2(V_n)$	SNR / α^2	SNR
$Acc. \approx V_{out}^2/\sigma^2(V_{OS})$	$Accuracy / \alpha^2$	$Accuracy$
$P = I_{BIAS} V_{DD}$	P / α	$P \alpha$ 
Area	Area	Area α^2


Caution: only first order approximations!!

Analog Perspective on Technology Scaling

    

[Kinget ESSCIRC13]

A- V_{DD} Scaling: Scaling g_m/I_D

 


Constant BW scaling

$\sigma^2(V_n) \approx kT/C$	$\sigma^2(V_n) / \alpha$
$\sigma^2(V_{OS}) \approx A_{VT}^2 / (WL)$	$\sigma^2(V_{OS}) ?$
$SNR \approx V_{out}^2 / \sigma^2(V_n)$	SNR / α
$Acc. \approx V_{out}^2 / \sigma^2(V_{OS})$	Accuracy ?
$P = I_{BIAS} V_{DD}$	P / α
Area	Area α

Caution: only first order approximations!!


A- V_{DD} Scaling: Scaling g_m/I_D

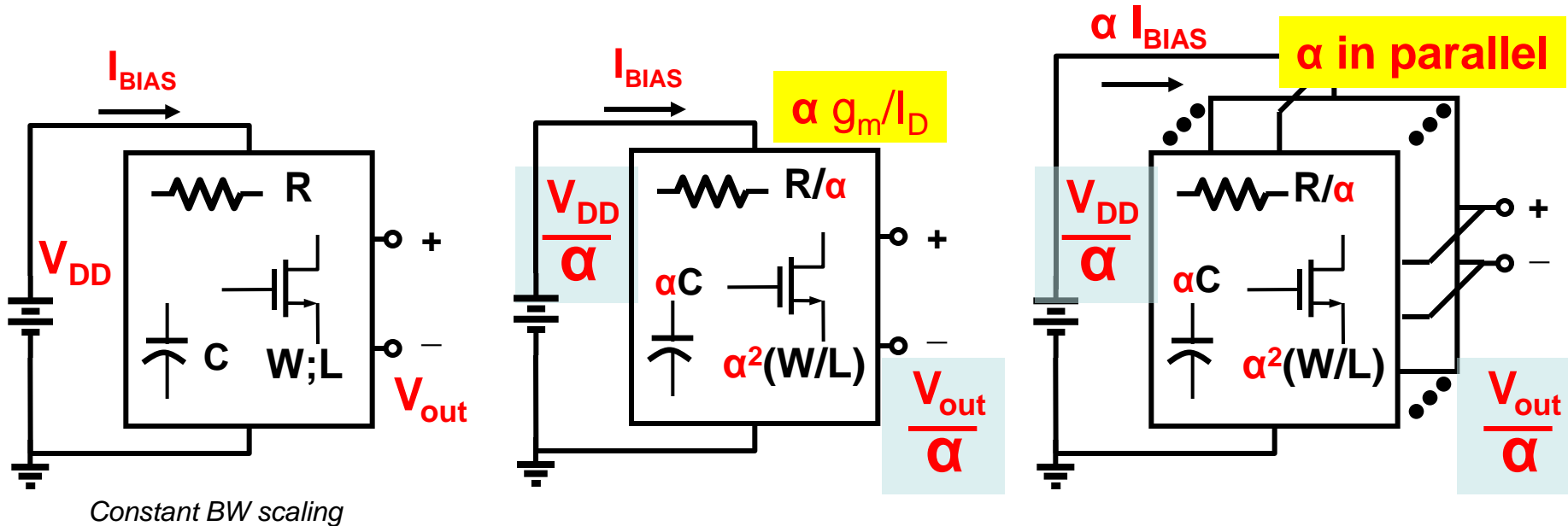

$\sigma^2(V_n) \approx kT/C$	$\sigma^2(V_n) / \alpha$	$\sigma^2(V_n) / \alpha^2$
$\sigma^2(V_{OS}) \approx A_{VT}^2/(WL)$	$\sigma^2(V_{OS}) ?$	$\sigma^2(V_{OS}) ?$
$SNR \approx V_{out}^2/\sigma^2(V_n)$	SNR / α	SNR
$Acc. \approx V_{out}^2/\sigma^2(V_{OS})$	$Accuracy ?$	$Accuracy ?$
$P = I_{BIAS} V_{DD}$	P / α	P
Area	Area α	Area α^2



Theoretical Power Limits for Analog

 

$$V_{DD} = 2\sqrt{2}V_{RMS}$$



- Noise limited circuits [Vittoz90]:

Independent of V_{DD}

$$SNR = \frac{V_{RMS}^2}{v_{n,RMS}^2}$$

$$\overline{v_{n,RMS}^2} = \frac{kT}{C}$$

$$I_{DC} = 2fC\sqrt{2}V_{RMS}$$

$$P \geq 8kTfSNR$$

ideal class B & Load Dominated

- Mismatch limited circuits [Kinget96,05]:


$$Acc = \frac{V_{RMS}^2}{3\sigma^2(V_{os})}$$

$$\sigma^2(V_{os}) = \frac{C_{ox}A_{VT}^2}{C}$$

$$I_{DC} = 2fC\sqrt{2}V_{RMS}$$

$$P \geq 24C_{ox}A_{VT}^2fAcc$$


A- V_{DD} Scaling: Load Dom. Scaling

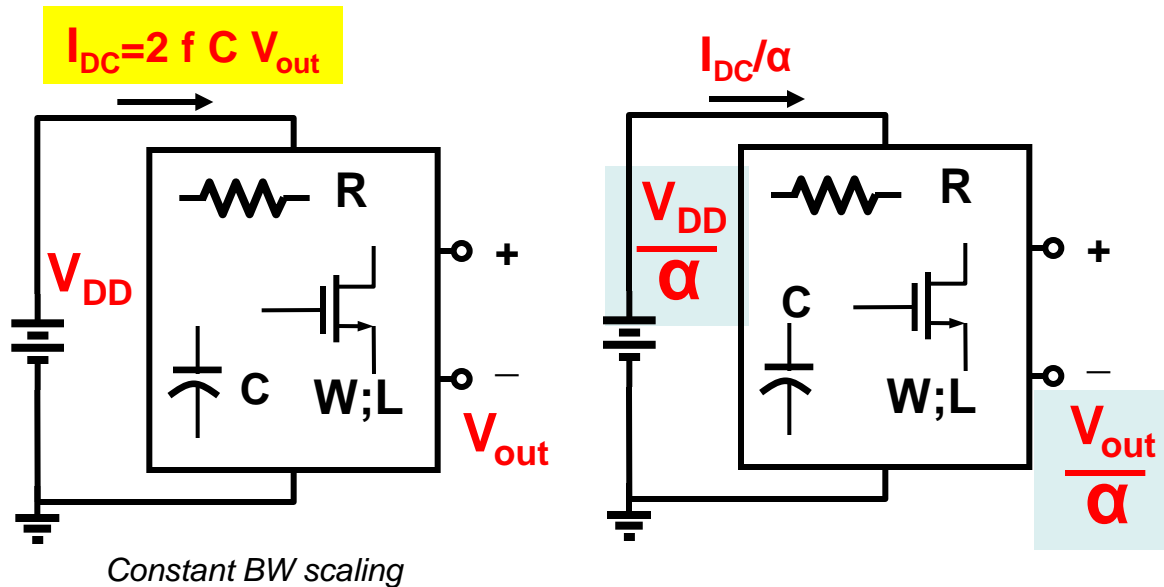

$\sigma^2(V_n) \approx kT/C$	$\sigma^2(V_n)$
$\sigma^2(V_{OS}) \approx A_{VT}^2/(WL)$	$\sigma^2(V_{OS}) ?$
$SNR \approx V_{out}^2/\sigma^2(V_n)$	SNR / α^2
$Acc. \approx V_{out}^2/\sigma^2(V_{OS})$	$Accuracy / \alpha^2$
$P = I_{DC} V_{DD}$	P / α^2
Area	Area

Caution: only first order approximations!!

A- V_{DD} Scaling: Load Dom. Scaling

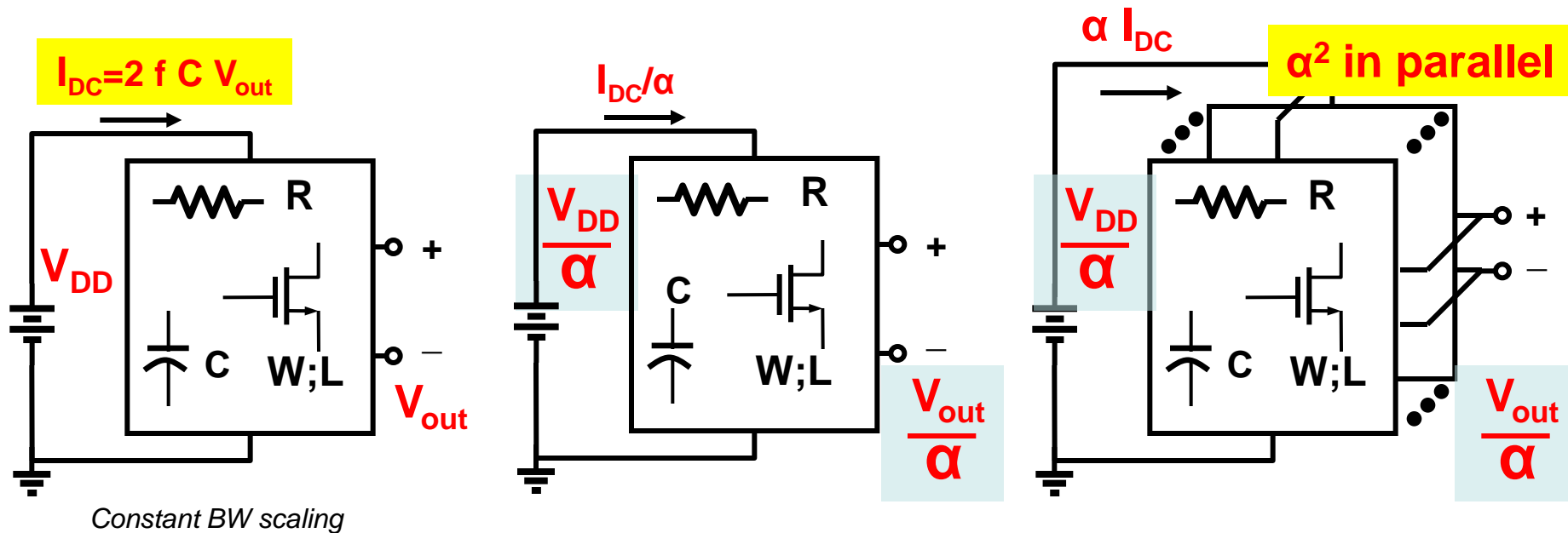

$\sigma^2(V_n) \approx kT/C$	$\sigma^2(V_n)$	$\sigma^2(V_n) / \alpha^2$
$\sigma^2(V_{OS}) \approx A_{VT}^2/(WL)$	$\sigma^2(V_{OS}) ?$	$\sigma^2(V_{OS}) / \alpha^2$
$SNR \approx V_{out}^2/\sigma^2(V_n)$	SNR / α^2	SNR
$Acc. \approx V_{out}^2/\sigma^2(V_{OS})$	$Accuracy / \alpha^2$	$Accuracy$
$P = I_{DC} V_{DD}$	P / α^2	P
Area	Area	Area α^2






Caution: only first order approximations!!

Analog V_{DD} Downscaling Strategies

Fixed BW & SNR performance target




1. Fixed g_m/I_D

– “W-scaling” → Power  & Area  

2. Scaling g_m/I_D

– “W/L & W-scaling” → Power  & Area   (?)

3. Load dominated scaling

– “Ideal Scaling” → Power  & Area  

Caveat: for area, we assumed constant $fF/\mu m^2$

$V_{DS,sat}$ Power Wall


$$P \geq 8 kT f SNR$$

$$1 + \frac{2V_{DS,sat}}{V_{DD} - 2V_{DS,sat}}$$


Power Penalty Factor

Signal swing REDUCES MORE than proportionally to V_{DD}

Power Penalty Factor

 
 
$$V_{DD} = 2\sqrt{2}V_{RMS} + 2V_{DSsat}$$



[Kinget ESSCIRC13]

© 2015 Peter Kinget

Analog V_{DD} Scaling Design Strategies

Fixed BW & SNR performance target

1. Fixed Gm/I

– “W-scaling”

→ Power ↑ & Area ↑↑

2. Scaling Gm/I

– “W/L & W scaling”



→ Power ↔ & Area ↑↑ (?)

3. Load dominated scaling

– “Ideal Scaling”

→ Power ↔ & Area ↑↑


Limited by
device scaling

  

Needs circuit
innovation

With $V_{DS,sat}$
power penalty

Power ↑

 

Needs circuit
innovation

Scaling the Analog V_{DD}

How it can be done




3.3V

1.8V


1.0V

0.5V



Telescopic Cascode

   Folded Cascode
Gain BoostingPseudo-Diff. & CMFF
Neg. Resistance
Body Bias


Transmission Gate THA

 


Bootstrapped THA

  Feedback THA
with Level Shift


Columbia's 0.5-0.6V Analog & RF Roadmap

 


135kHz LPF
+ Tuning

 


Body- & Gate-input
OTAs

 


CT 74dB
25kHz $\Sigma\Delta$ A/D

 


10b 1Ms
THA

 


2.4GHz
LO Synth.

 


900MHz RF
Front-end

 


2.4GHz
RCV

 


8b 10Ms
A/D

 


2.4GHz
RCV+Synth
WPAN

 


900MHz
RCV
Cell.

 

70MHz
SMOA LPF

 

0.6V V_{DD}
V-Reference

 

2004

2005

2006

2007

2008

2009

2010


2014

Leveraging Nanoscale CMOS


Different Architectures for Analog

Zero-Crossing-Based Sampled Circuits

OTA Based Circuits

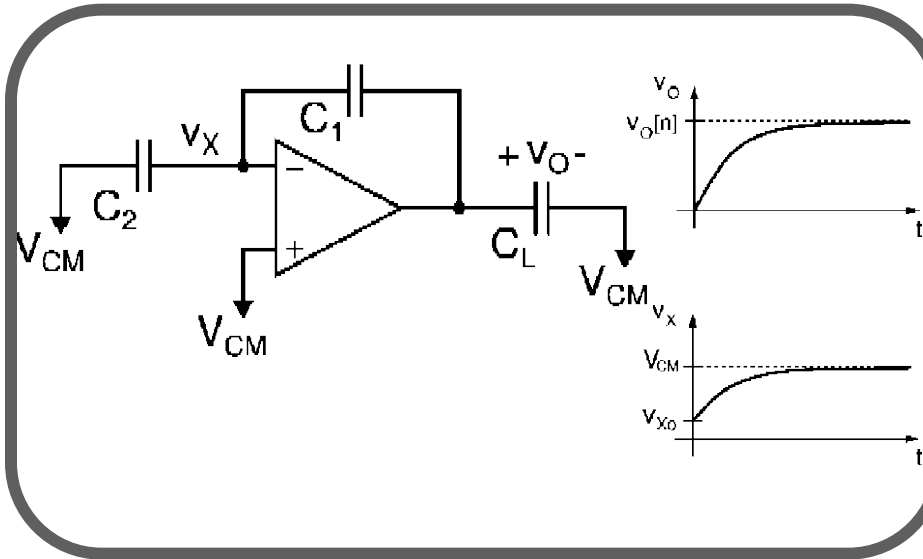


Comparator Based Circuits

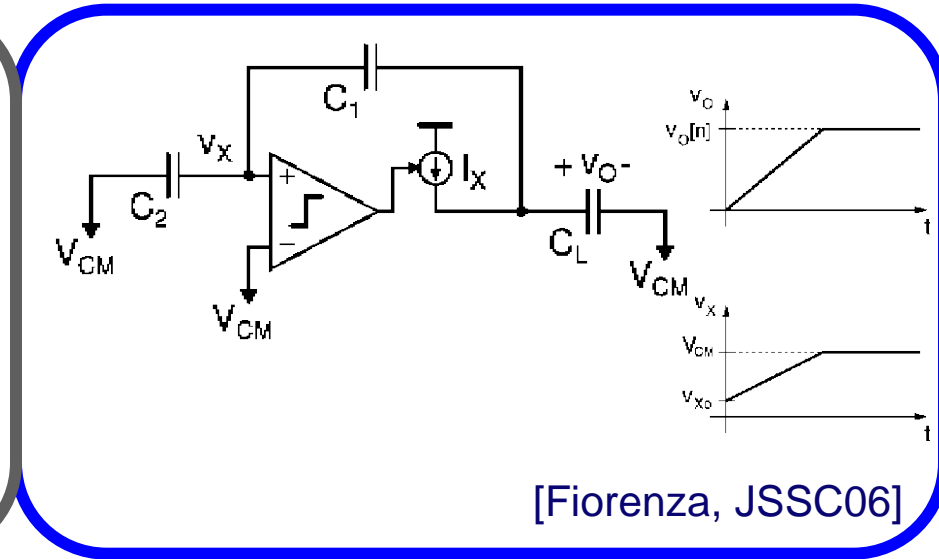

[Fiorenza, JSSC06]


- High gain OTA replaced by zero-crossing-detecting CT comparator + current sources
- 'Linear' exp. settling replaced by slew-based charging
- Closed loop stability constraints issues avoided

ZCB Circuits: In Detail

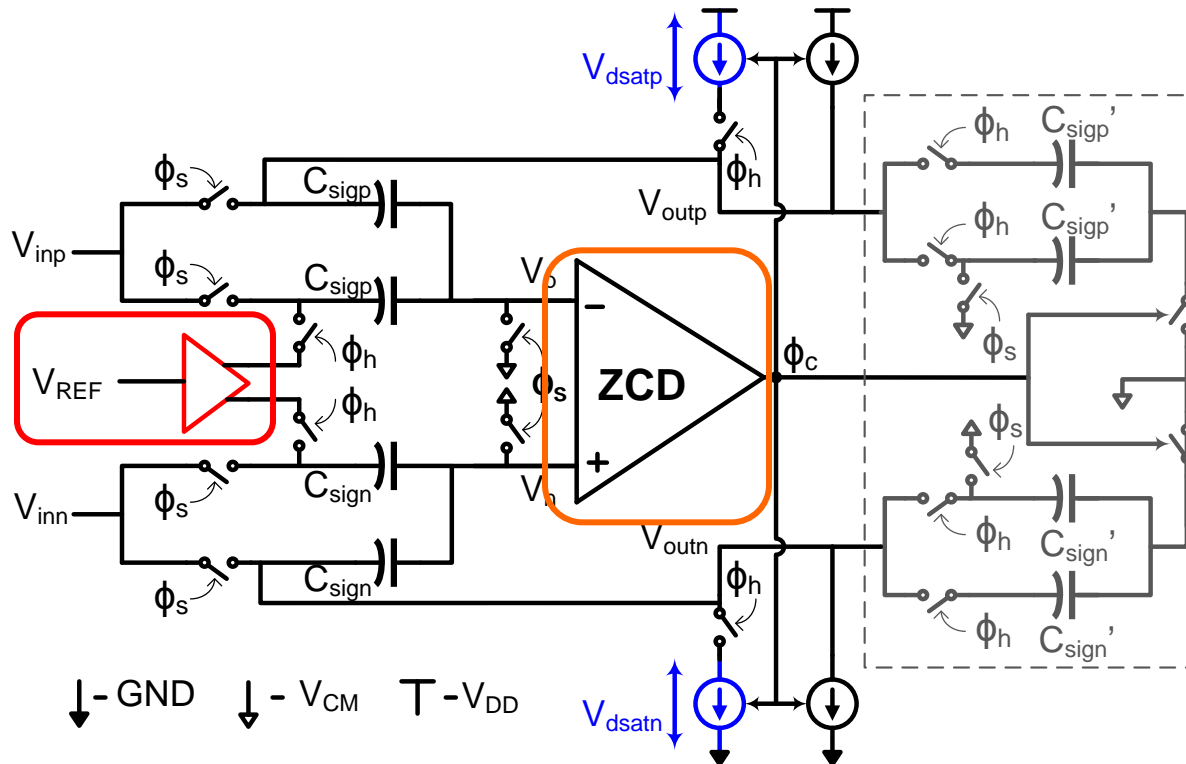


- MDAC linearity determined by linearity of **output current sources**
 - Voltage headroom: limited voltage swing
- MDAC noise performance determined by **ZCD noise-performance**
 - Conventional analog noise-scaling
- **Reference buffer design** is more complicated than OTA-based MDACs
- Accurate settling requires overshoot cancellation

Ring Amplifiers for Sampled Circuits

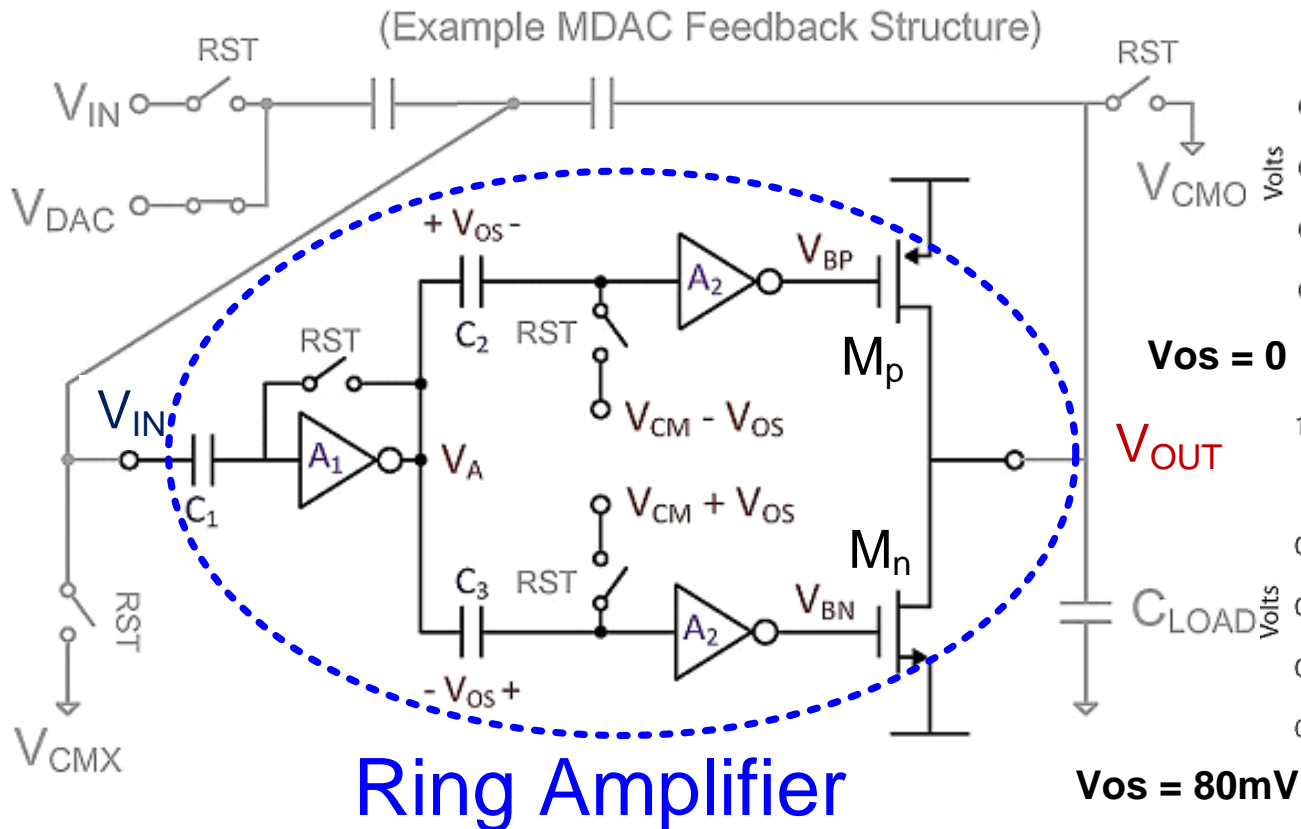

 
- OTAs in MDACs replaced by Ring Amplifiers
 - Ring Oscillators with embedded offset
- Potential low-voltage operation
 - M_p and M_n operate as switched current sources
 - Slew rate need not be constant (no headroom required)



[Hershberg, JSSC12]



Leveraging Nanoscale CMOS

 Different Approaches to Analog Signal Representation



**Exploiting
Device Speed**





Circuit Primitives

  

Signal Representation



Topologies

    

[Kinget13]



V & I → Delay or Phase

	V/I	Delay (or Phase)
Signal Swing	$V_{SS}+X \rightarrow V_{DD}-X$	$T_{\min} \rightarrow T_{\max}$
Noise	1/f & Thermal	Jitter & Phase noise
Distortion	Active $V \rightarrow I$ is non-linear but feedback with <i>linear passives</i> helps	$V \rightarrow T$ & $T \rightarrow V$ non linear !?
Integration	Active RC, G_m -C	VCO or CCO ($V \rightarrow \Phi$ or $I \rightarrow \Phi$)
Amplification	Intrinsic gain, cascode, multi-stage	??
Analog SHA	store Q on C	Recirculating DLL


VCO-Based Quantizers

V or I based Quantizer

VCO Based Quantizer

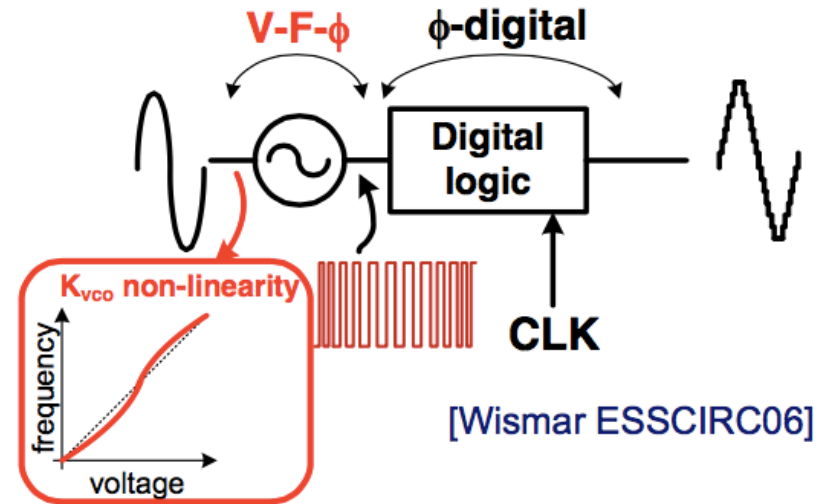 

- Diff. Open Loop Example

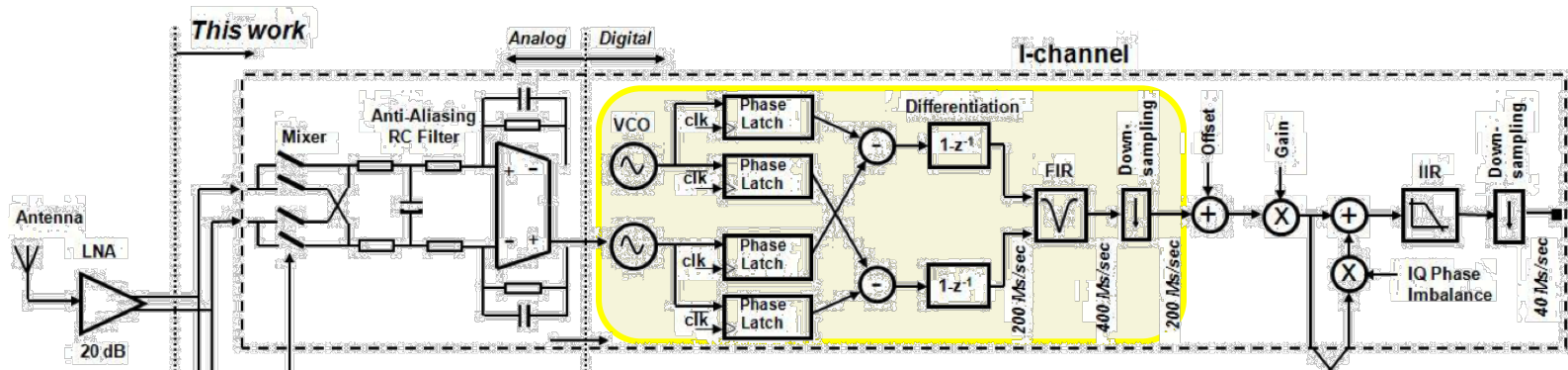


[Op 't Eynde, ISSCC10]



- Still requires analog AAF

VCO-Based Quantizers

Open Loop

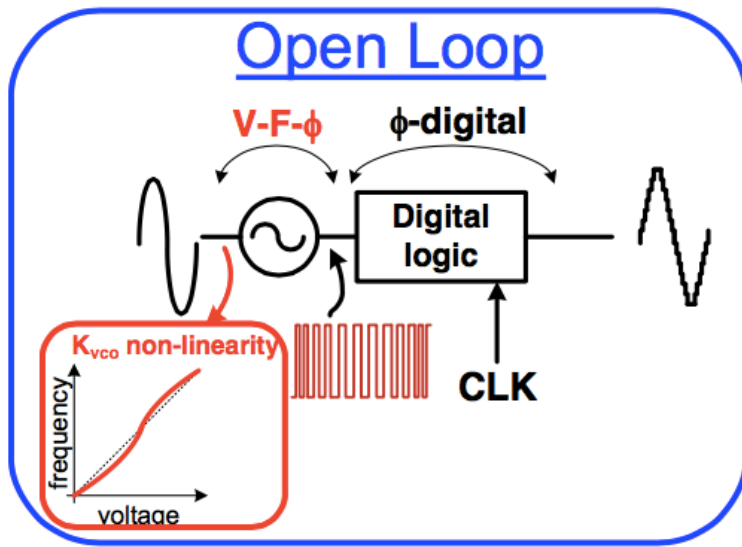

"Feedback Linearization"

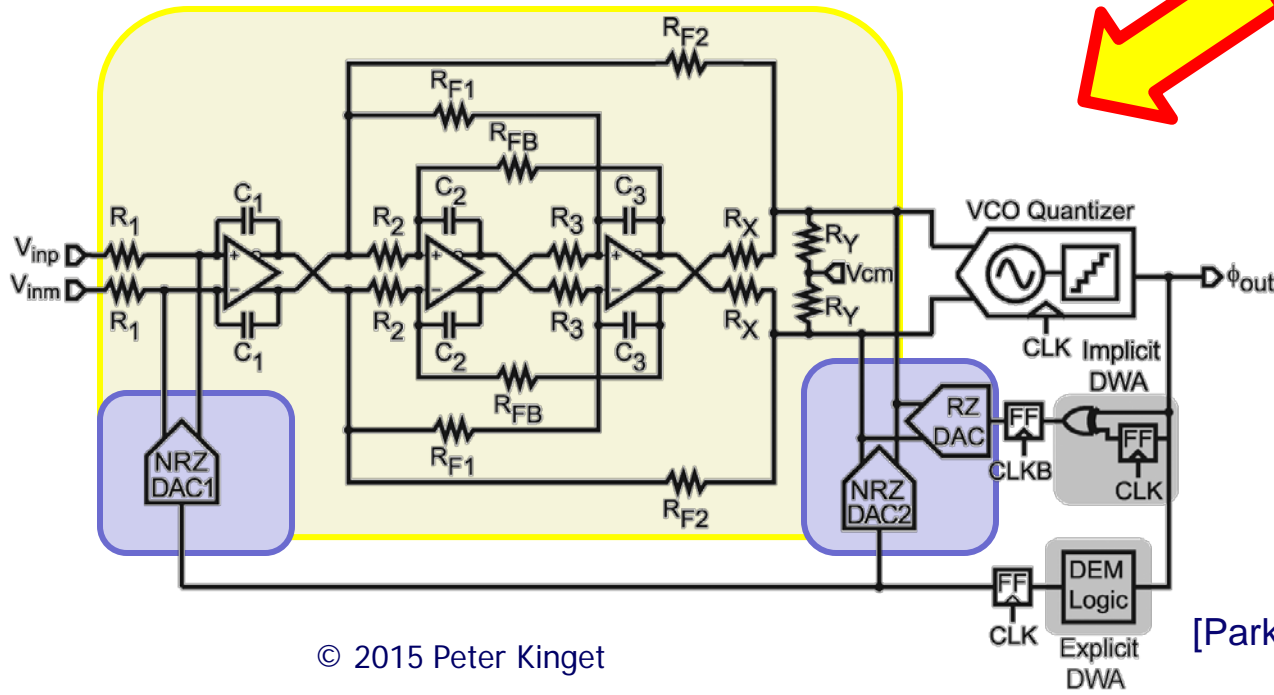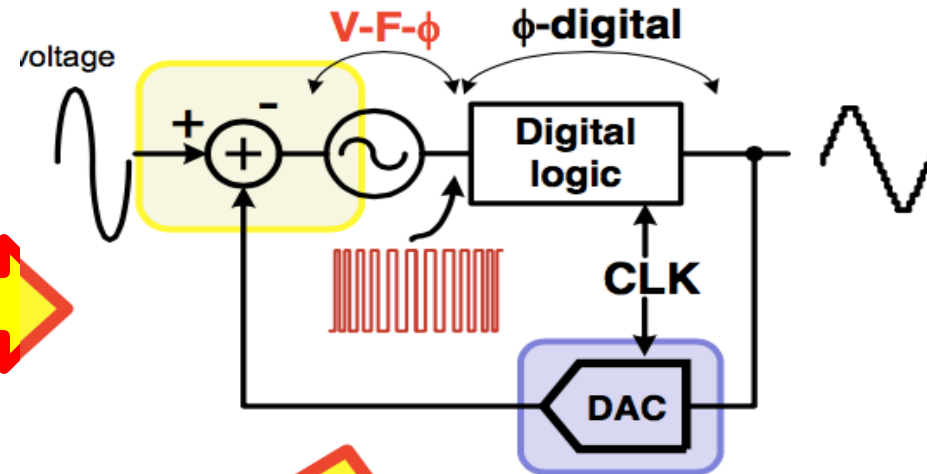


- Quantizer exploits phase domain processing
- Linearization still relies on OTA-RC based voltage/current domain circuits



VCO-Based CT Filters

Active RC or Gm-C Integrator

VCO Based Integrator

 


• Biquad Gm-C Filter

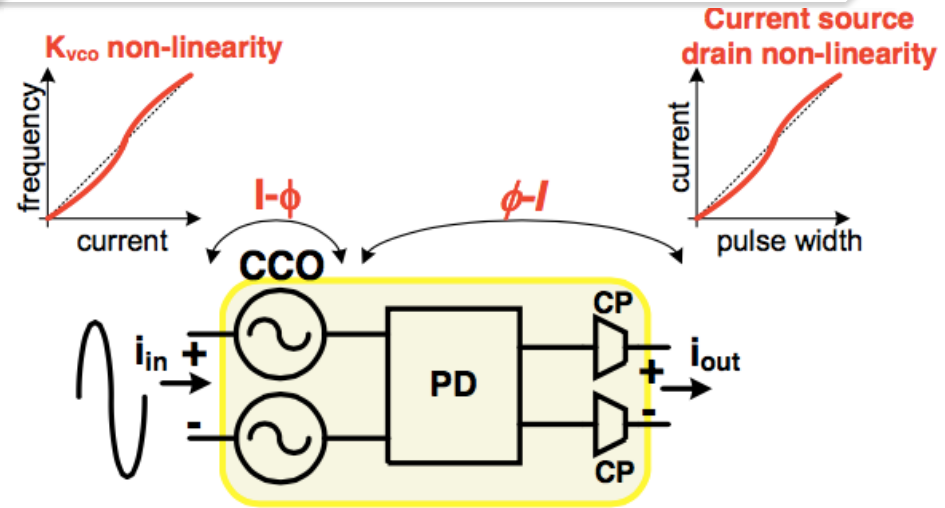 

'Perfect' integration, but o/p swing limited by CS



0.55V

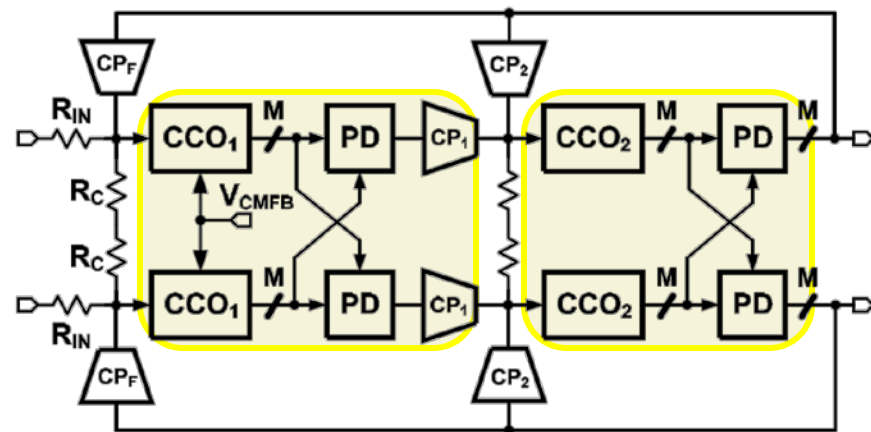


VCO-Based OTA & Filter

Active RC Integrator
with OTA

  
VCO Based OTA with zero for freq.
compensation




Zero for compensation

 

Complete Active Filter

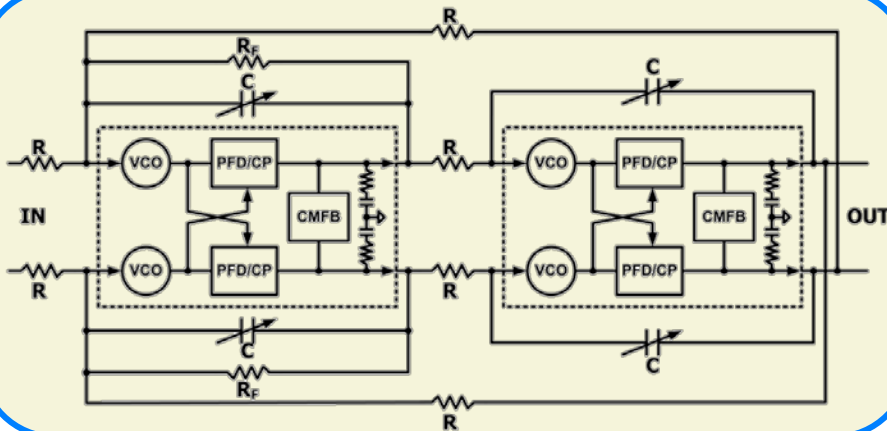


VCO Based OTA

 

- Very high DC gain


VCO-Based OTA & Filter

A 40MHz 4th-order Active-UGB-RC Filter


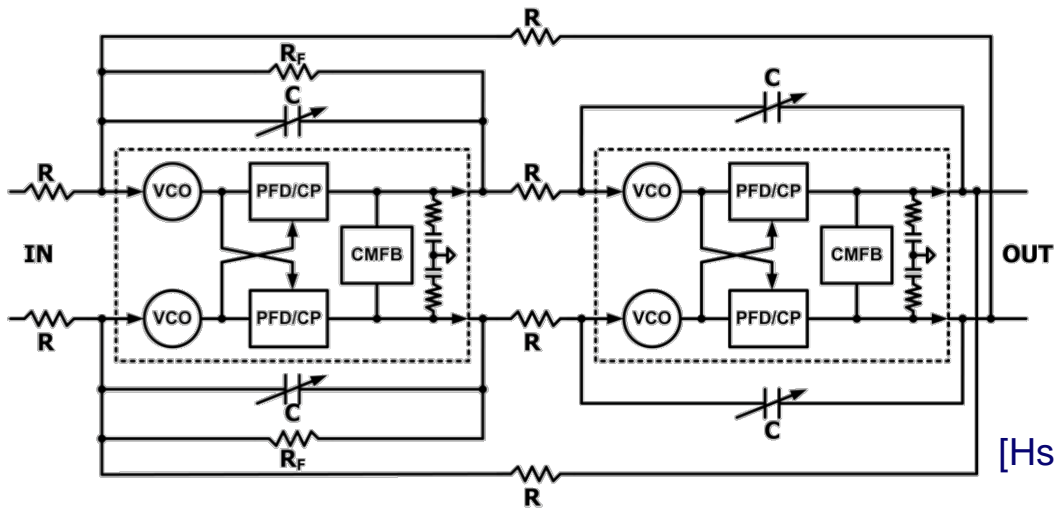


1.2V
7.8mW
0.07mm²

[Hsu ESSCIRC14]

 


55nm CMOS

  




Switched Mode OpAmps

 - 'Standard' analog V_{DD} scaling
 - Strong $V_{DS,sat}$ penalty for $V_{DD} \ll 1V$
 - Small o/p swing
 - ➔ more power in *noise-limited* first stage
 - High o/p stage efficiency is also difficult



Switched Mode OpAmps

  
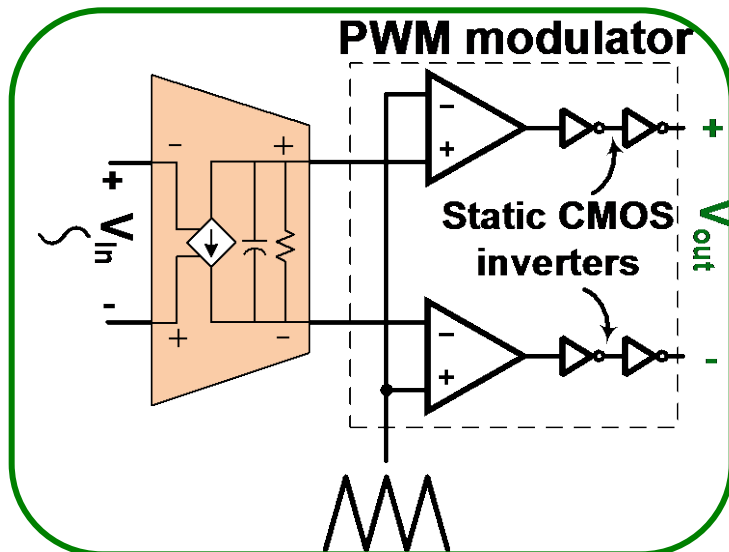
- 'Standard' analog V_{DD} scaling
 - Strong $V_{DS,sat}$ penalty for $V_{DD} \ll 1V$
 - Small o/p swing
 - more power in *noise-limited* first stage
 - High o/p stage efficiency is also difficult
- Switched Mode Operational Amplifier
 - Rail-to-rail output swing
 - Low Z_{out}
 - Large BW
 - **Performance gets BETTER with SCALING!!**




[Vigraham JSSC14]

Switched Mode OpAmps

  - 'Standard' analog V_{DD} scaling
 - Strong $V_{DS,sat}$ penalty for $V_{DD} \ll 1V$
 - Small o/p swing
 - more power in *noise-limited* first stage
 - High o/p stage efficiency is also difficult
- Switched Mode Operational Amplifier
 - Rail-to-rail output swing
 - Low Z_{out}
 - Large BW
 - **Performance gets BETTER with SCALING!!**



 Breaking through the $V_{DS,sat}$ Power Wall





1.2x @0.6V



[Vigraham JSSC14]

A 0.6V 70MHz 4th Order CT Butterworth Filter


Active RC Biquads with SMOAs

 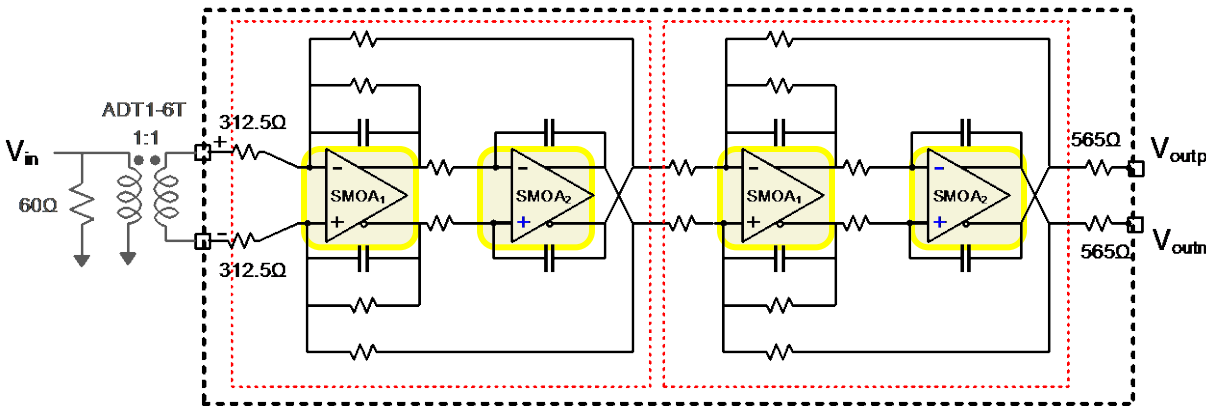


65nm

[Vigraham JSSC14]

Multi-Phase SMOA


 


17-level
signal

 



A 0.6V 70MHz 4th Order CT Butterworth Filter

Active RC Biquads with SMOAs

 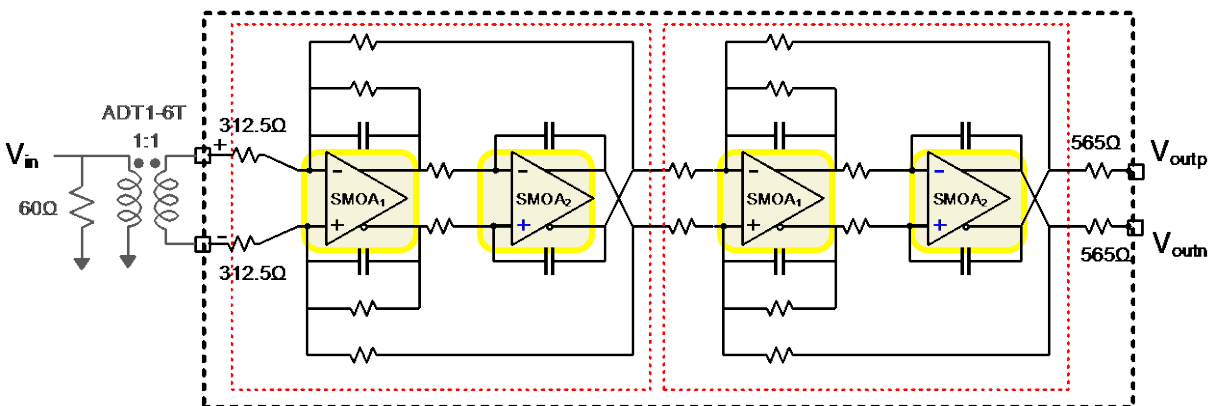



65nm

[Vigraham JSSC14]

  


A 0.6V 70MHz 4th Order CT Butterworth Filter

Active RC Biquads with SMOAs

  

[Vigraham JSSC14]

Figure of Merit

 


Outlook


New Devices

28nm FD-SOI CMOS



TWO gates !

 

 
<http://www.stericsson.com/technologies/FD-SOI.jsp>



22nm FinFET

  

 
<http://www.realworldtech.com/intel-22nm-finfet/>



Faster @ lower V_{DD} → lower Power!
Better short channel control → better analog performance?


Analog Circuits in Microprocessors

"More Moore"
==
More Analog

 

[Greg Taylor, Intel, "Analog/Mixed Signal Design: The Technology Scaling Rate Limiter?"]


"More than Moore"

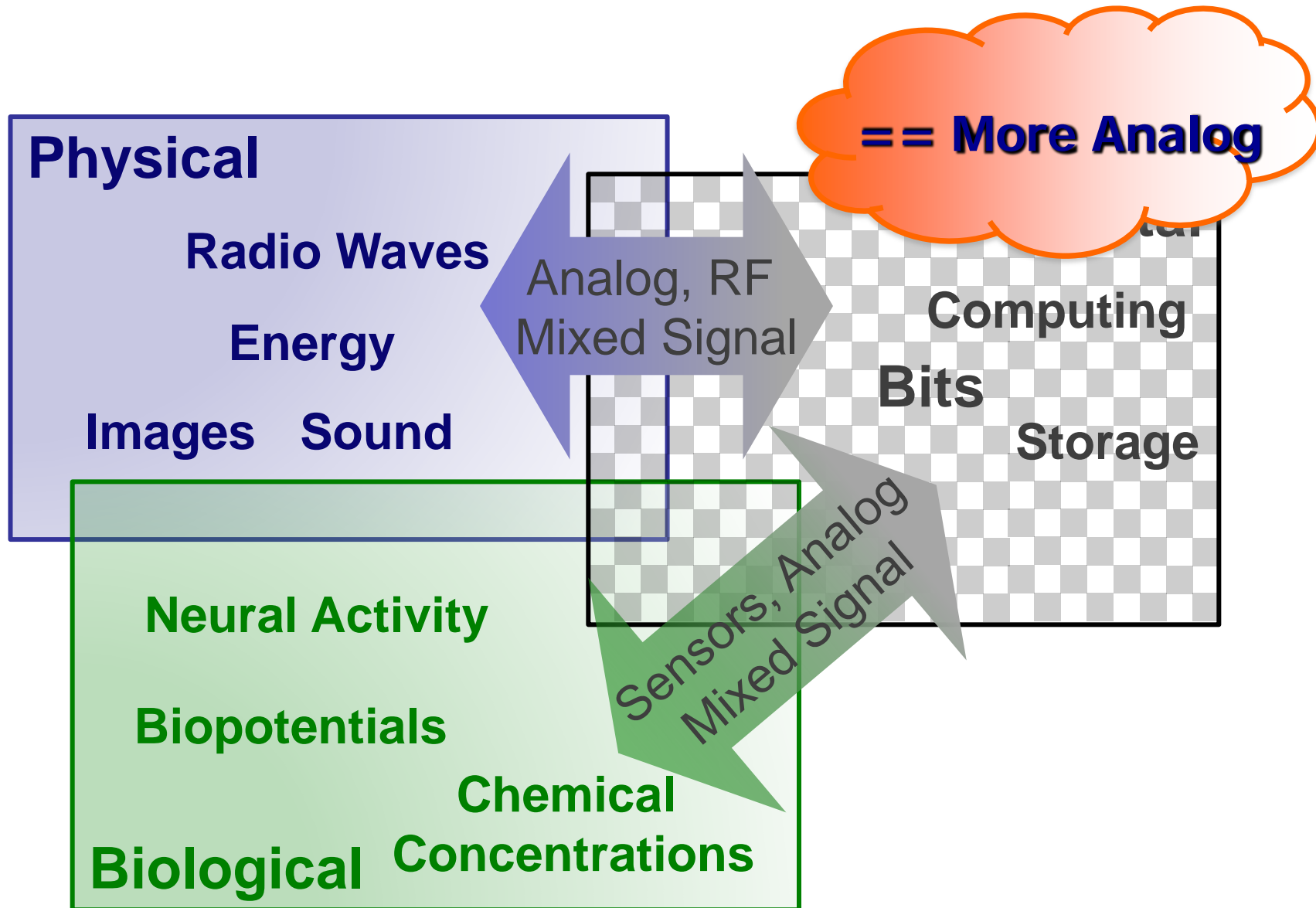

CMOS: Just a Step .

Beyond CMOS

The physical world remains
ANALOG...

 

[Wikipedia: Kurzweil's extension of Moore's law]

Scaling Analog Circuits

Exciting Opportunities Ahead

- Device scaling introduces challenges to 'traditional' analog design
 - Supply scaling arguably being the most severe challenge, but it can be overcome
- Device scaling offers new opportunities for analog design
 - Novel circuit approaches
 - Different representation for analog information
 - New device architectures hold interesting promises

“Digital scaling” makes analog design actually more interesting & important

Acknowledgments

- Collaborators: Y. Tsvividis, K.P. Pun (Chinese Univ. Hong Kong), S. Chatterjee (now IIT Delhi), A. Balankutty (now Intel), J. Shen (now ADI), N. Stanic (now SiLabs), S. Yu (now VIA), B. Vighram (now Maxlinear), J. Kuppambatti (now Seamless Devices), C. Hsu (now ADI).
- Funding Support: Analog Devices, Intel, SRC, Silicon Labs, Texas Instruments, DARPA, National Science Foundation.
- Fabrication Support & Donation: CMP, ST Microelectronics, UMC and VIA Telecom.
- Tools: Integrand Software for EMX software and Berkeley Design Automation (Mentor) for BDAsim


Thank You for your attention



We Are Stuck With Analog


The Physical World is ANALOG...

Physical World to Digital

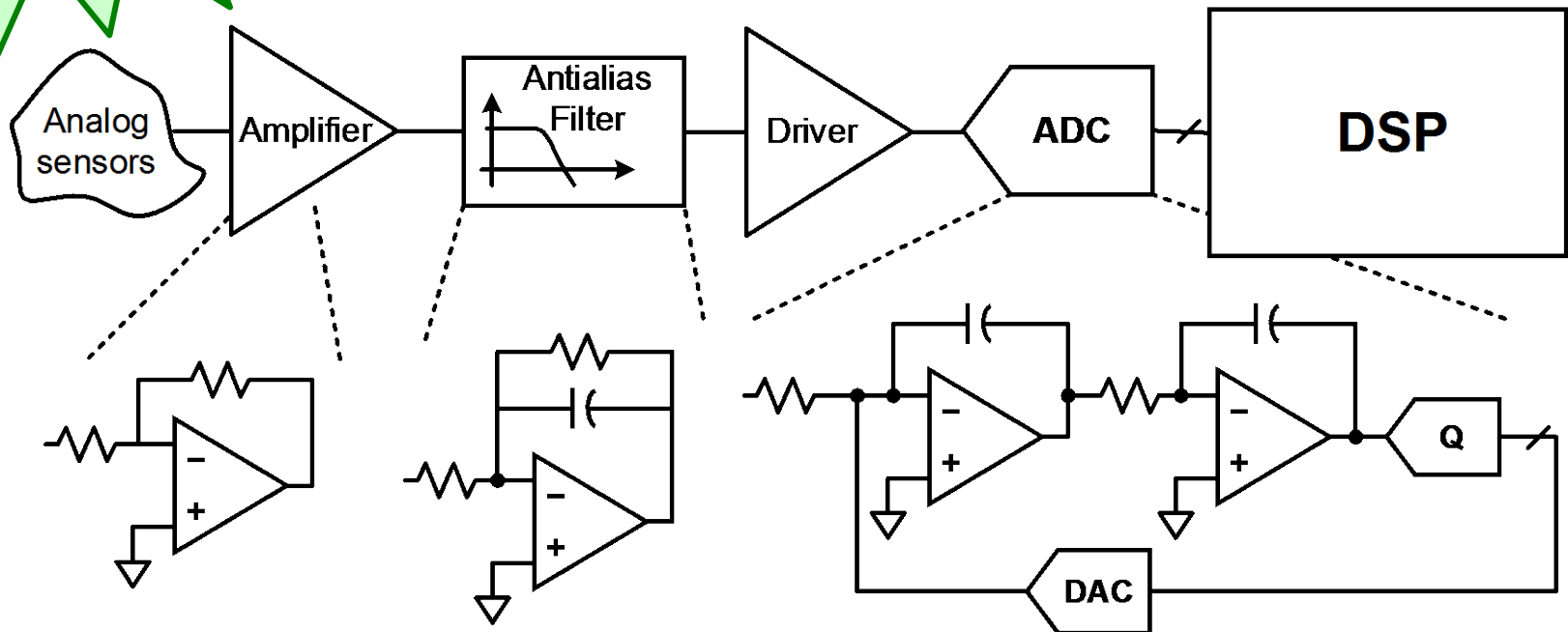

Also, CLK generation, I/O, RF, D/A, Power Mgmt, ...

ADC FOM vs V_{DD}

 

Data adapted from B. Murmann, "A/D Converter ISSCC Performance Data," 2013