

Advanced Wireless Power and Data Transmission Techniques for Implantable Medical Devices



Hyung-Min Lee
Post-Doc, MIT



*Custom Integrated Circuits Conference
September 30, 2015*

Maysam Ghovanloo

GT-Bionics Lab

School of Electrical and Computer Engineering



Mehdi Kiani
Assistant Prof.
Penn State




Wireless IMD Applications



**Boston
Retinal
Prosthesis**



**Nucleus
Cochlear
Implant**

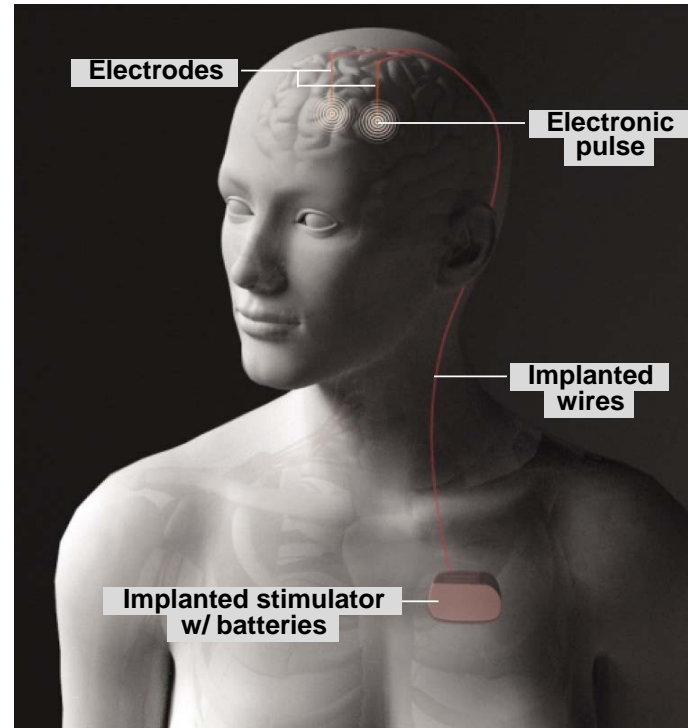


**Chest-
mounted
Deep Brain
Stimulation
(DBS)**

IMD: Implantable Medical Device


- Treat neurological diseases (e.g. DBS) or substitute sensory modalities (retinal/cochlear implant), high power, large volume
- Battery-powered chest-mounted DBS
 - Head-mounted DBS with wireless power transfer

Wireless IMD Applications

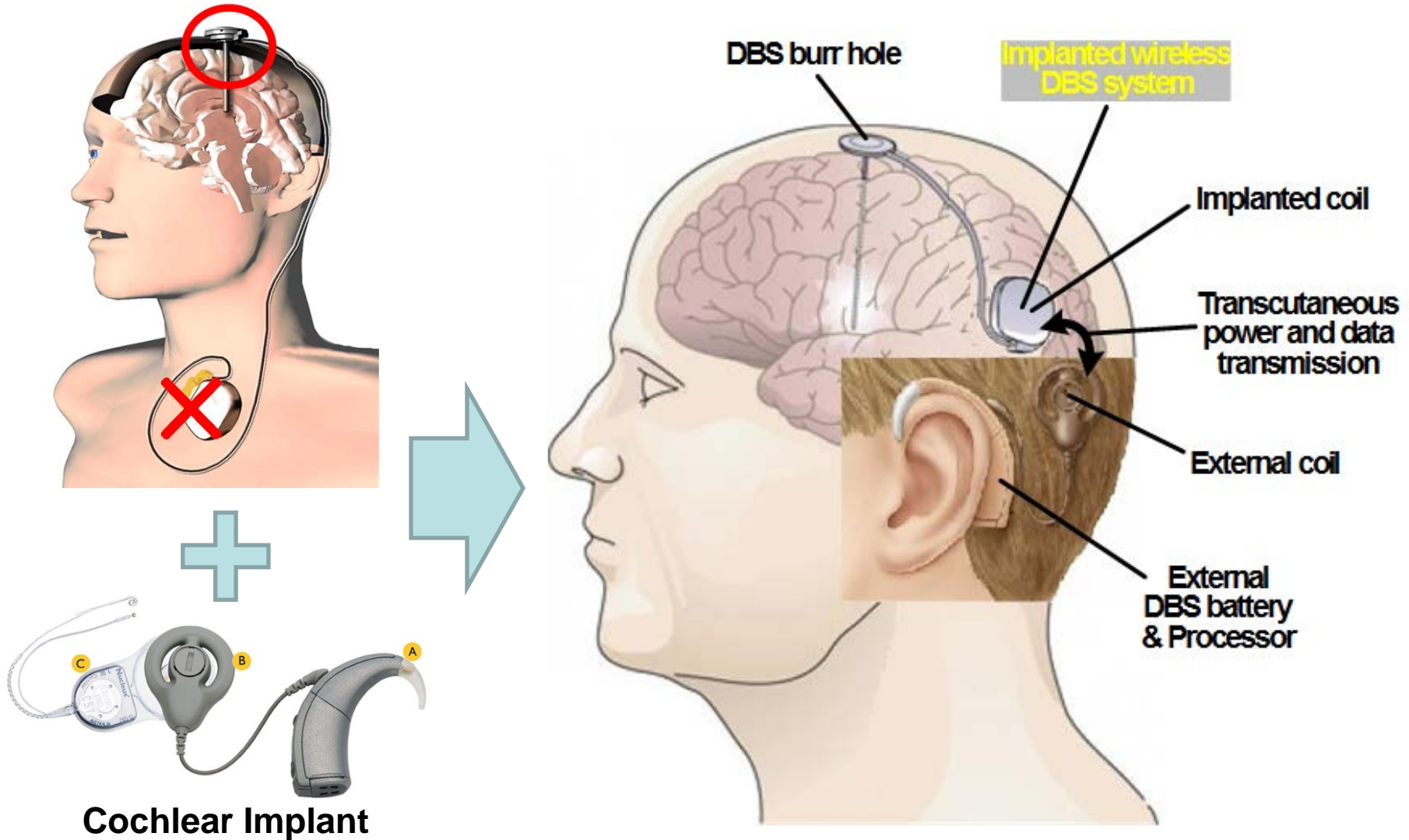


Head-mounted DBS with wireless power transfer

Wireless IMD Applications

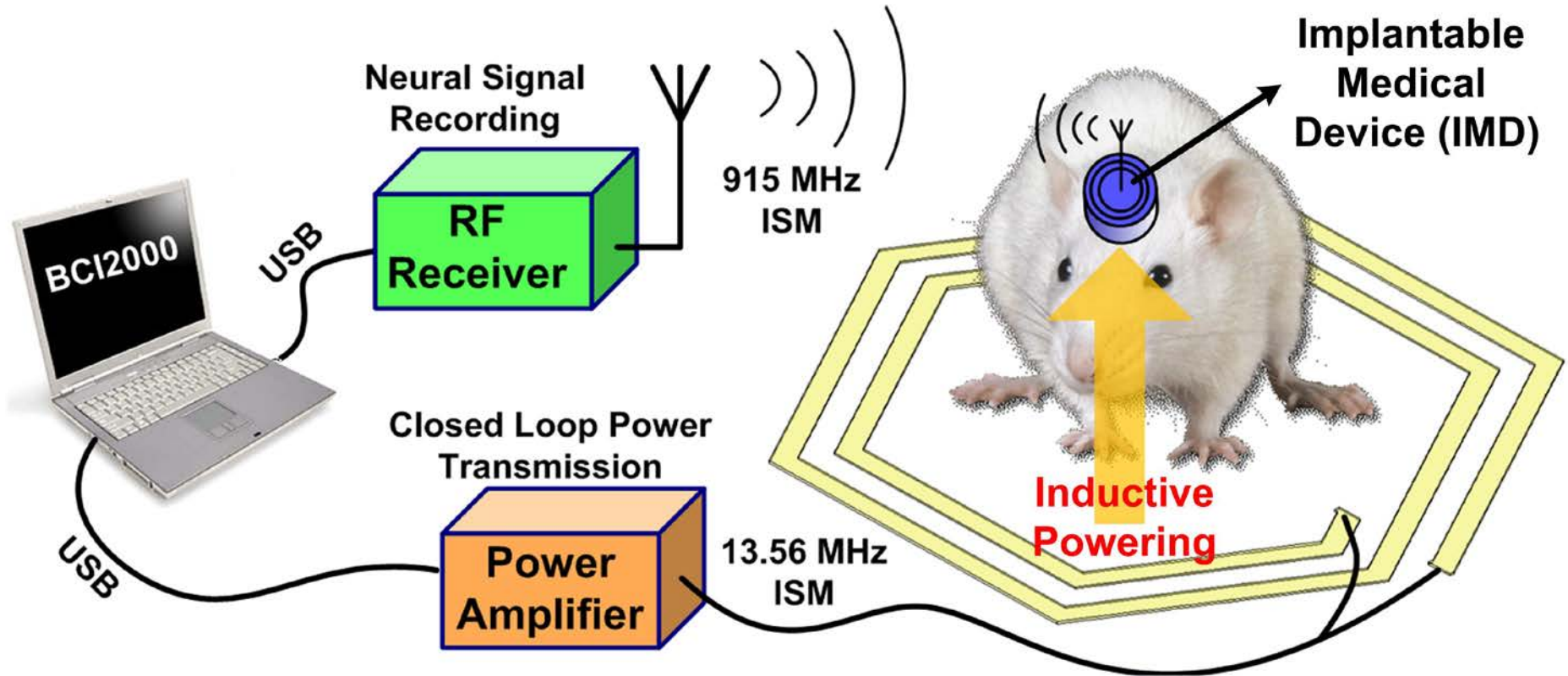

- Size/weight of batteries affect animal movements and behavior.
→ Wireless power transmission via inductive links
- Inductively powered IMDs for **long-term** uninterrupted electrophysiology experiments on small **freely moving animal**.


Wireless Power Transmission Efficiency

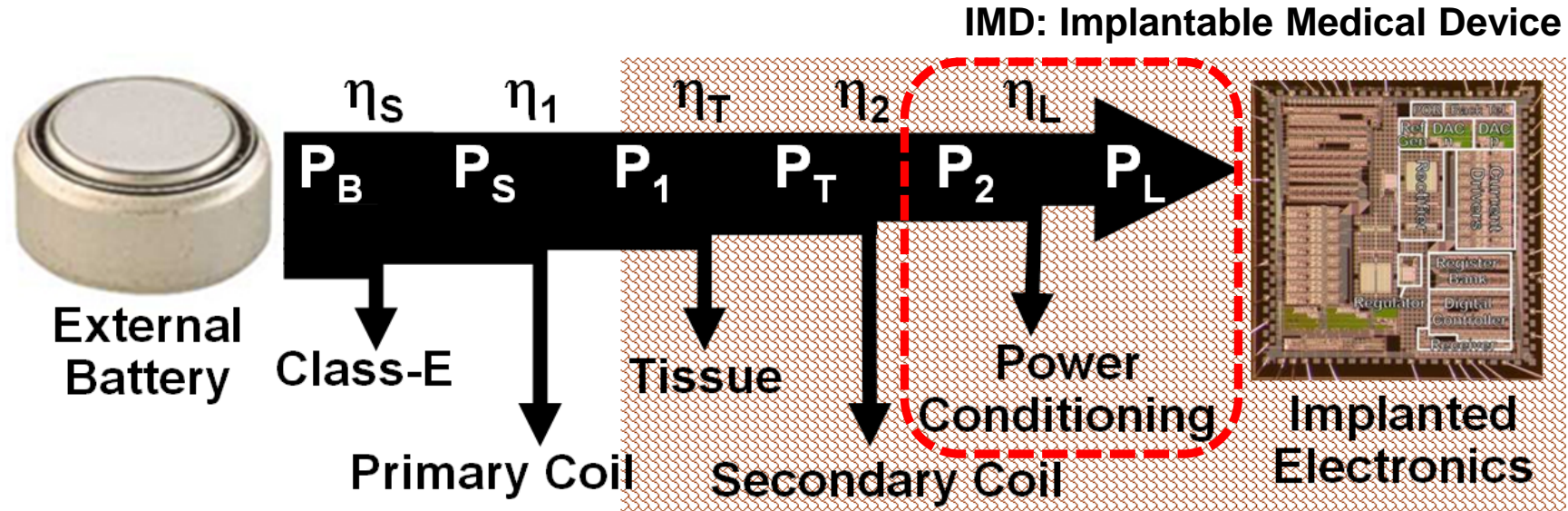

With **higher IMD power efficiency** from the secondary coil to the tissue:

- The IMD can operate with **lower received power** from a **further coil distance** (small coils implanted deep in the body).
- Small power consumption in IMDs reduces the **risk of tissue damage** from heating and interference.

Wirelessly-Powered IMD Structure

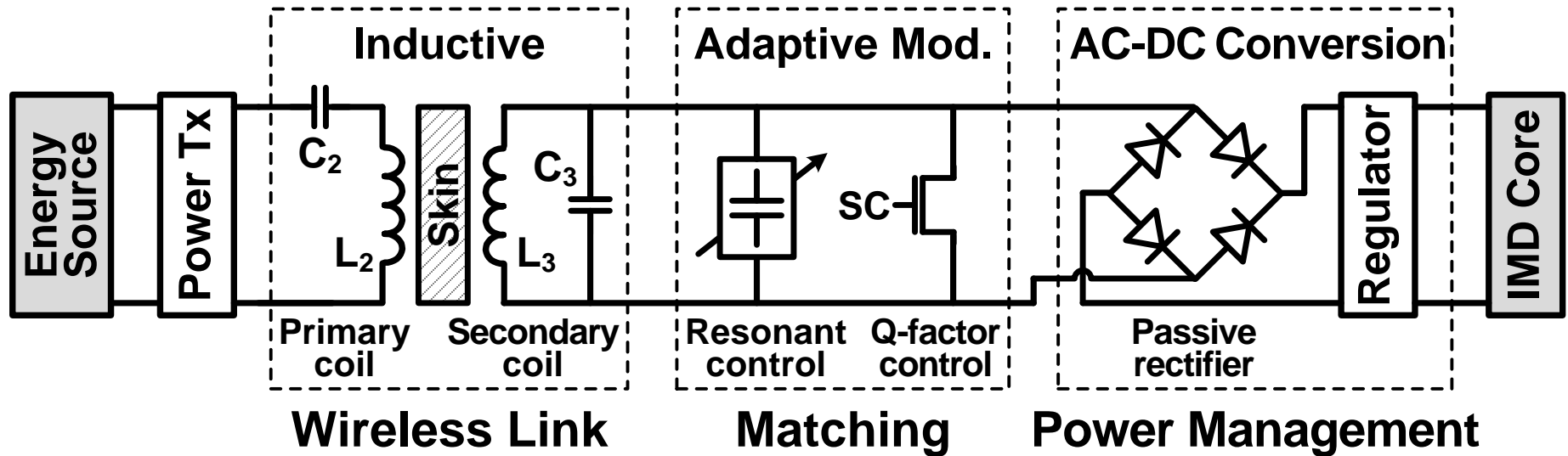

Various WPT techniques in every stage of power flow:

- Wireless power transmission link (across the skin)
- Matching and adaptive Q-modulation (inside the body)
- Power management units (inside the body)

Outline


- **Optimized Wireless Power Transfer Links**
- **Power Conversion and Management Circuits**
- **Low-Power Wireless Data Telemetry**
- **Conclusions**

Outline

- **Optimized Wireless Power Transfer Links**
 - **Conventional 2-Coil Inductive Links**
 - **Multi-Coil (3-Coil) Inductive Links**
 - **Q-Modulation Concept**
 - **Q-Modulation Power Management (QMPM)**
- **Power Conversion and Management Circuits**
- **Low-Power Wireless Data Telemetry**
- **Conclusion**

Power Transfer Efficiency (PTE) in 2-Coil Inductive Links

- The 2-coil power transfer efficiency (PTE):
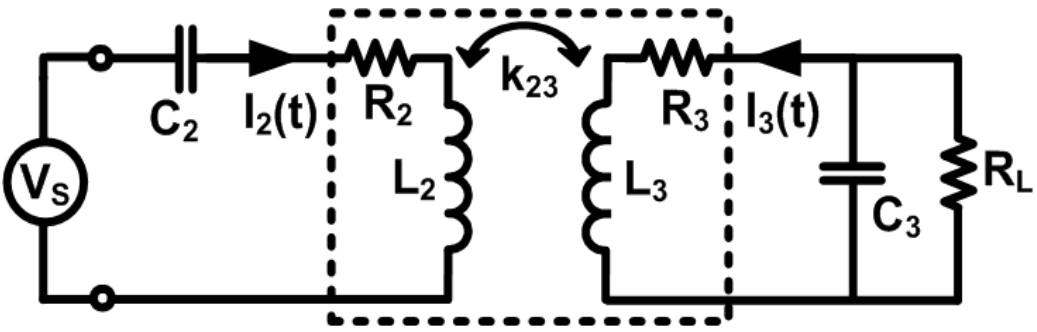
$$\eta_{2-coil} = \frac{k_{23}^2 Q_2 Q_{3L}}{1 + k_{23}^2 Q_2 Q_{3L}} \cdot \frac{Q_{3L}}{Q_L}$$


Primary Loop Secondary Loop

- PTE is highly dependent on: k_{23} , Q_2 , Q_3 , Q_L (load Q)


$$Q_{3L} = Q_3 Q_L / (Q_3 + Q_L)$$

$$Q_L = R_L / \omega_0 L$$

- Large R_L (Q_L): Low efficiency in the **secondary** loop
- Small R_L (Q_L): Low efficiency in the **primary** loop

Maximizing PTE and PDL in 2-Coil Link


Parameter		Sym	Sim
L_1	Inductance (μH)	L_1	1.2
	Outer diameter (cm)	D_{o1}	27
	Fill factor	Φ_1	0.28
	Num. of turns	n_1	2
	Line width (mm)	w_1	12
	Line spacing (mm)	s_1	35
	Quality factor	Q_1	196
L_2	Inductance (μH)	L_2	0.058
	Coil diameter (cm)	D_{o2}	4
	Wire diameter (mm)	w_2	5.68
	Num. of turns	n_2	1
	Line spacing (μm)	s_2	100
Quality factor		Q_2	151.5
coupling distance (mm)		d_{12}	50
coupling coefficient		k_{12}	0.032
Power transfer efficiency (%)		PTE	72.0
Power delivered to load (mW)		PDL	215.3

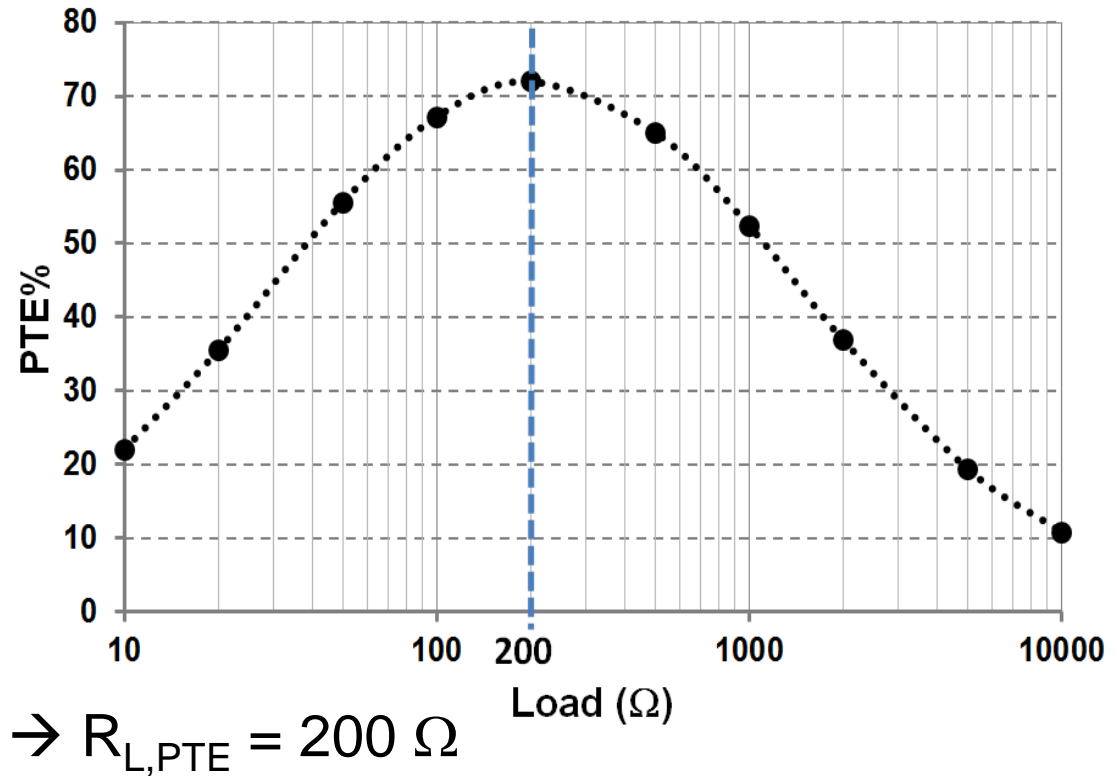

- PTE and PDL are highly dependent on R_L
 - R_L is often predefined
- Impedance Transformation
- 1) Matching circuits 2) Multiple coils

Maximizing PTE in 2-Coil Inductive Links
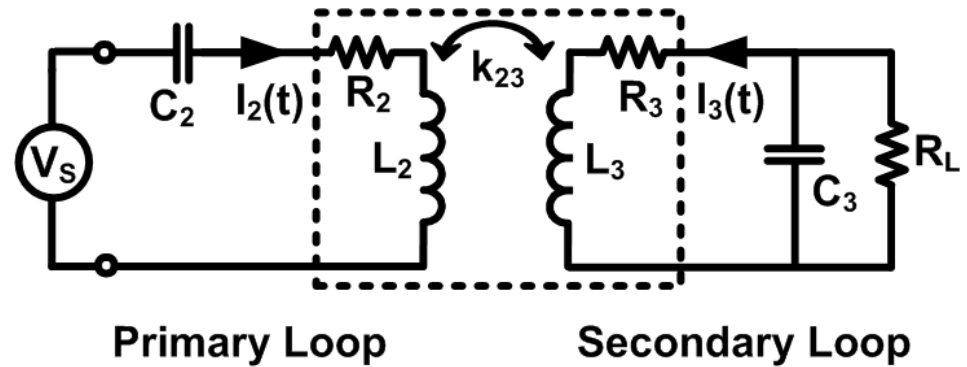
$$\eta_{2-coil} = \frac{k_{23}^2 Q_2 Q_{3L}}{1 + k_{23}^2 Q_2 Q_{3L}} \cdot \frac{Q_{3L}}{Q_L}$$



- An **optimal load**, $R_{L,PTE}$, to maximize the PTE

$$Q_{L,PTE} = \frac{R_{L,PTE}}{\omega_0 L_3} = \frac{Q_3}{(1 + k_{23}^2 Q_2 Q_3)^{1/2}}$$

- R_L is often defined by the application  **Impedance Transformation**

1) Matching circuits



- More lossy (multiple L & C with $Q < 100$)
- Smaller size and tunable



2) **Multiple coils**



- More efficient ($Q > 200$)
- Easy to match the load
- Larger size & not tunable




3-Coil Inductive Links for Load Matching

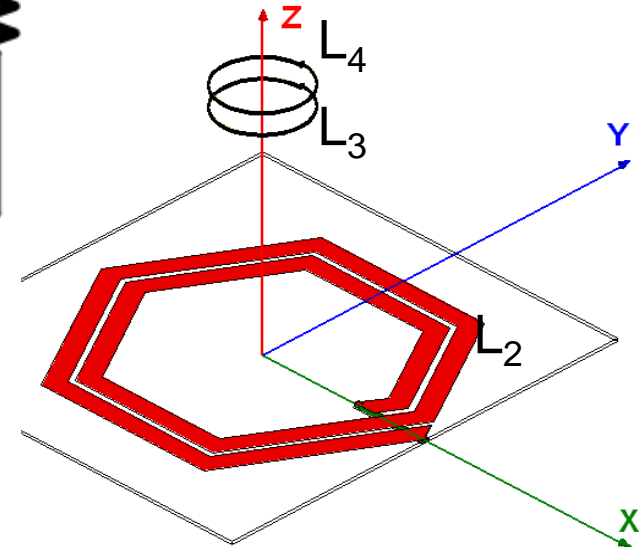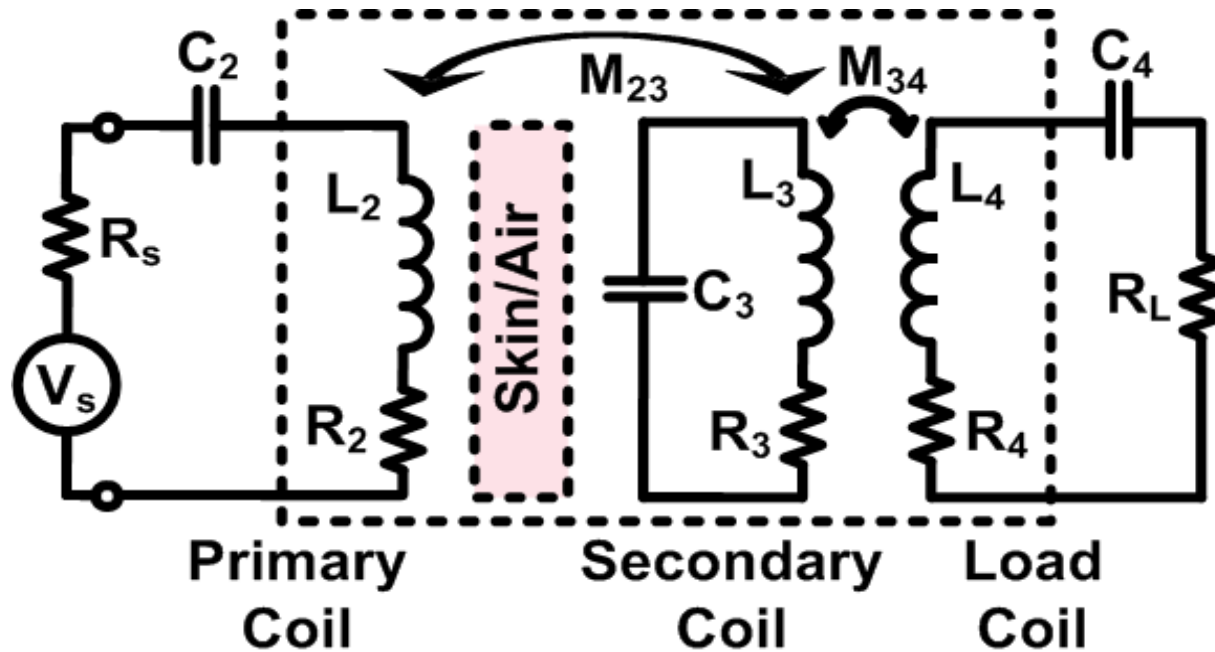


$$\eta_{3-coil} = \eta_{23}\eta_{34} = \frac{(k_{23}^2 Q_2 Q_3)(k_{34}^2 Q_3 Q_{4L})}{[(1 + k_{23}^2 Q_2 Q_3 + k_{34}^2 Q_3 Q_{4L})(1 + k_{34}^2 Q_3 Q_{4L})]} \cdot \frac{Q_{4L}}{Q_L}$$

Maximizing PTE in 3-Coil Link


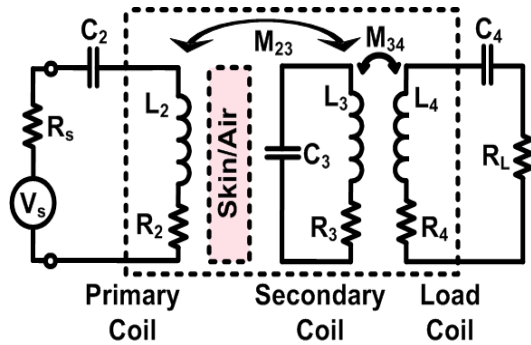


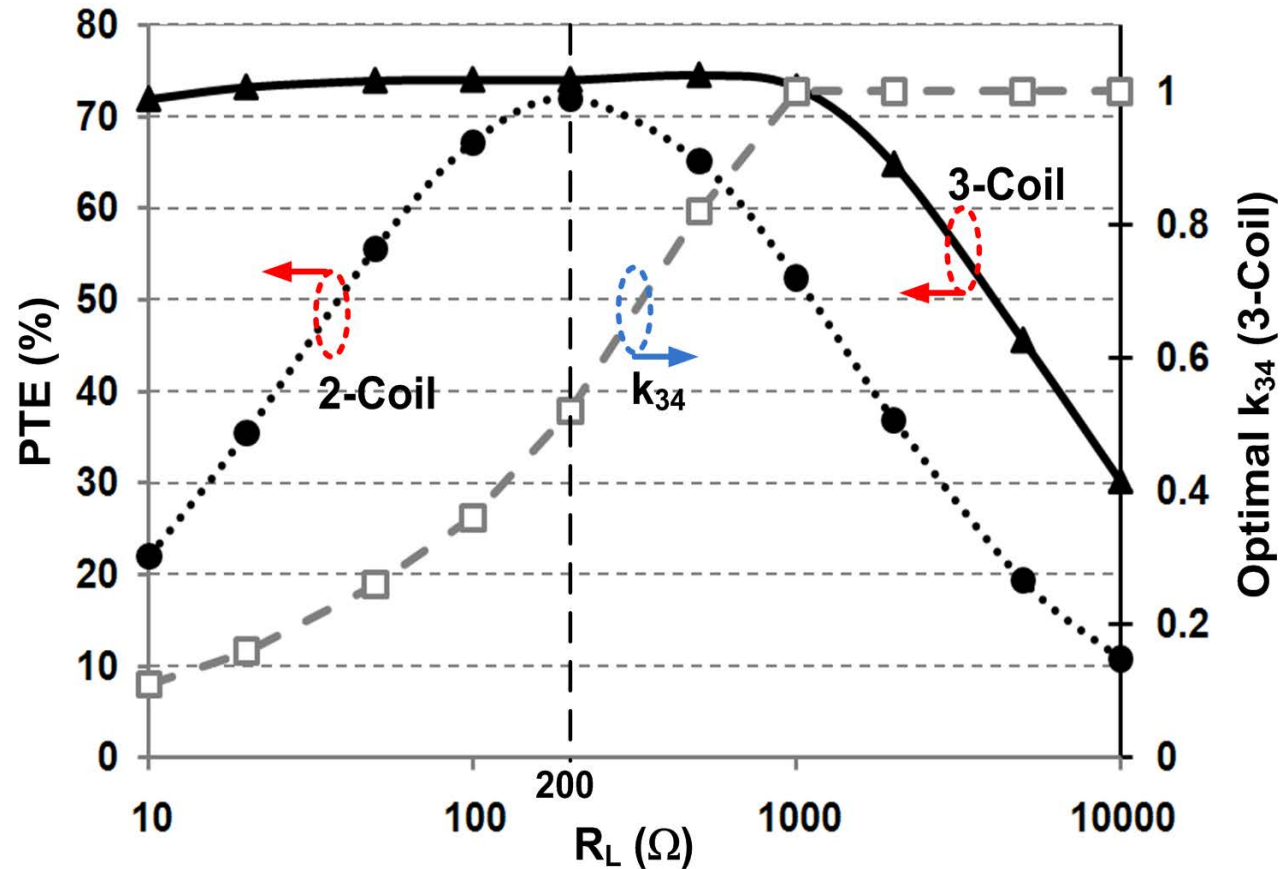By changing k_{34} (and $R_{\text{ref},3}$), the 3-coil PTE can be kept at maximum for a wide range of R_L .



A 2-coil link does not provide this flexibility, and PTE maximizes only for a specific R_L value.


3-Coil Inductive Links for Load Matching

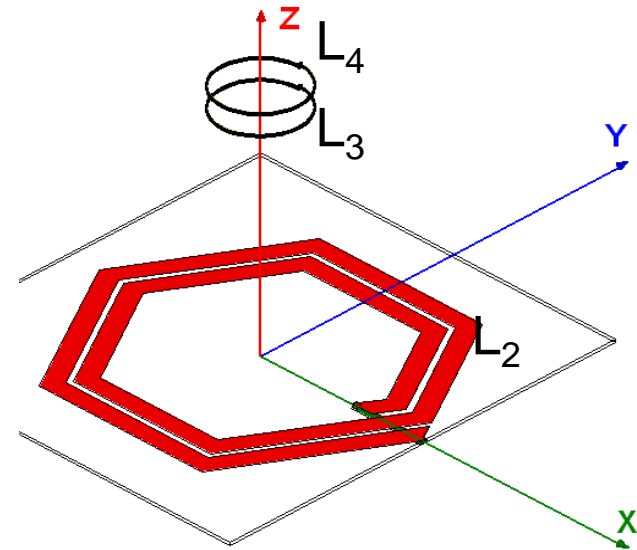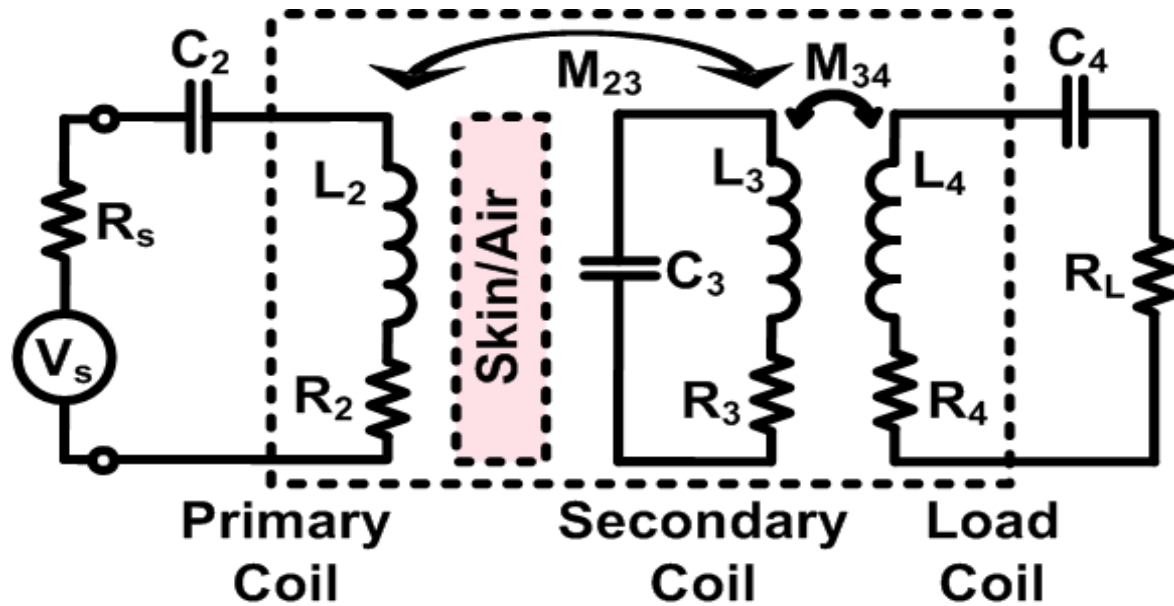



$$\eta_{3\text{-coil}} = \eta_{23}\eta_{34} = \frac{(k_{23}^2 Q_2 Q_3)(k_{34}^2 Q_3 Q_{4L})}{[(1 + k_{23}^2 Q_2 Q_3 + k_{34}^2 Q_3 Q_{4L})(1 + k_{34}^2 Q_3 Q_{4L})]} \cdot \frac{Q_{4L}}{Q_L}$$

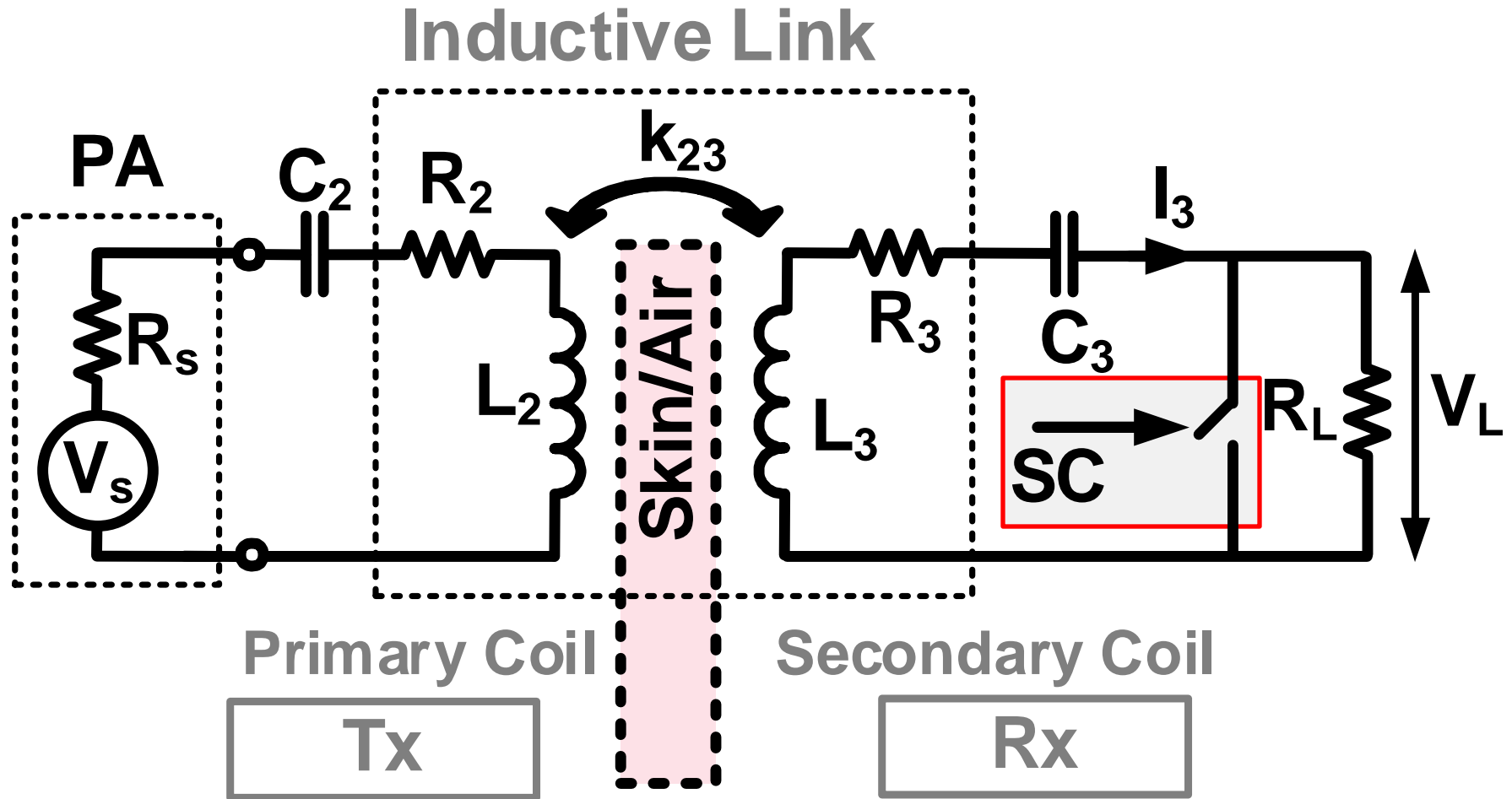Problem: k_{23} and R_L change but k_{34} is not adjustable during operation!

A Q-Modulation Based Inductive Power Transmission Link



Q-Modulation Inductive Link

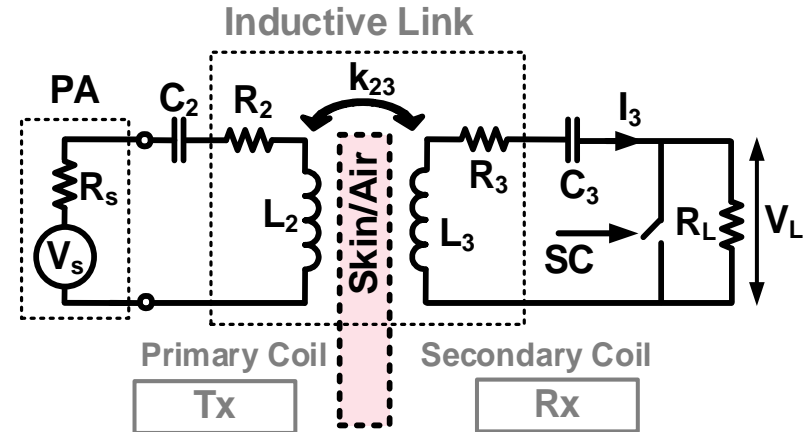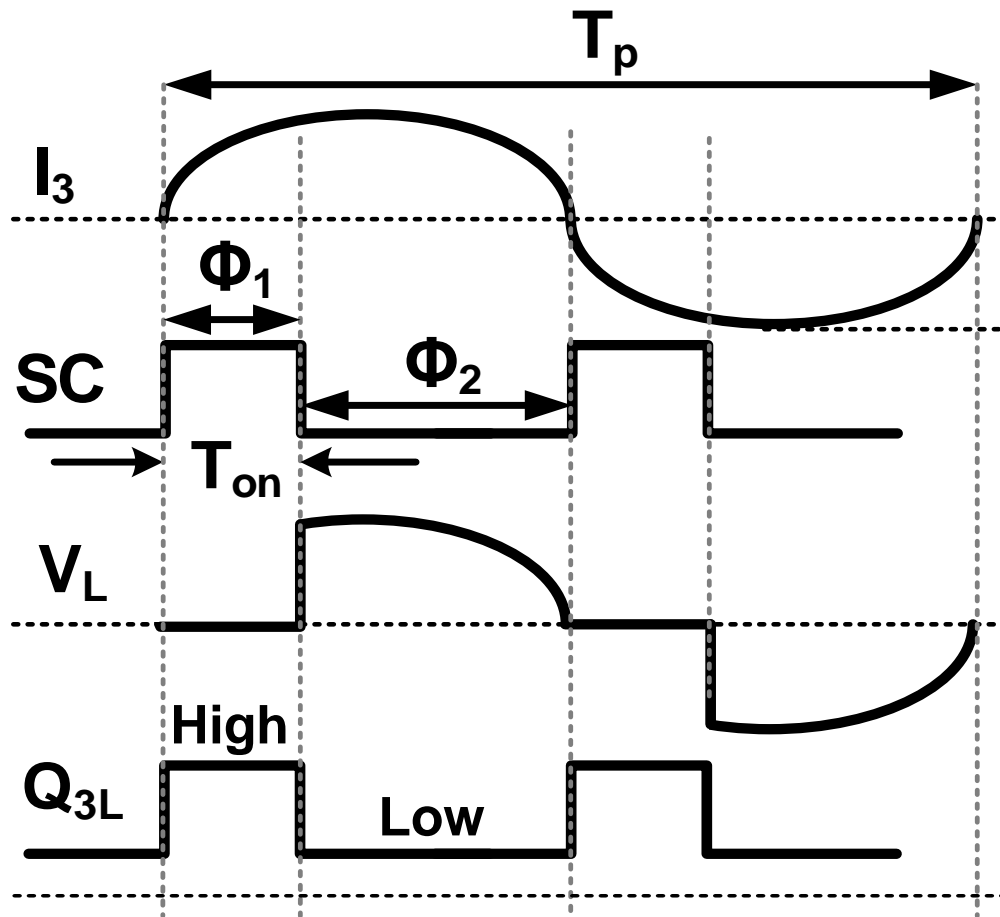


Q-Modulation Parameters


- $T_p/2$ and T_{on}
- Duty cycle: $D = 2T_{on}/T_p$
- Switching at time zero crossing of I_3
- Switch resistance: R_{sw}

$$Q_{3L,eq} = \omega_p \frac{0.5L_3 |I_m|^2}{P_{Rsw} + P_{R3} + P_{RL}} = \frac{\omega_p L_3}{R_3 + R_{sw} \left(D - \frac{1}{2\pi} \sin(2\pi D)\right) + R_L \left(1 - D + \frac{1}{2\pi} \sin(2\pi D)\right)}$$

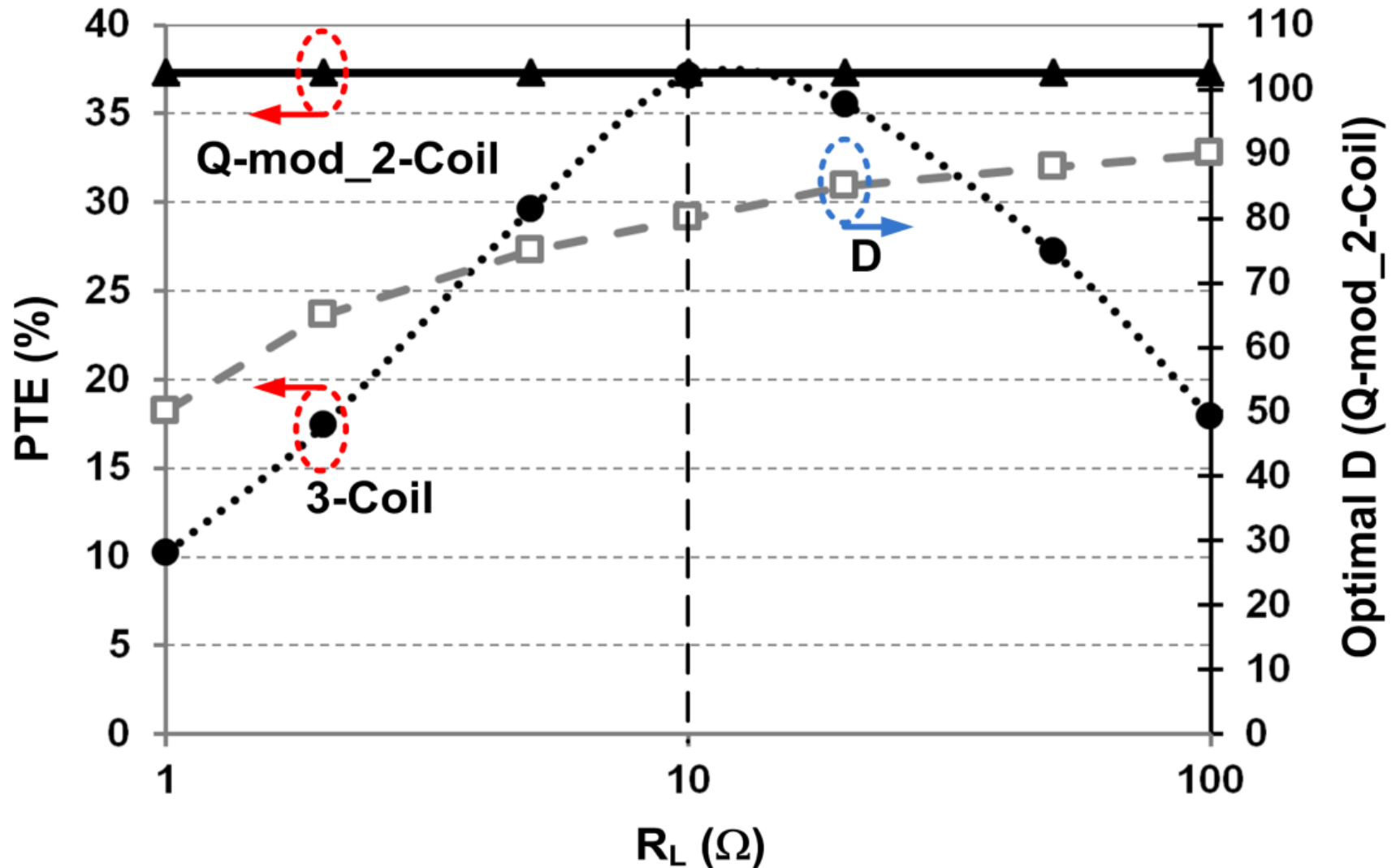
PTE Comparison between 3-Coil and Q-Modulation Inductive WPT Links



Q-Modulation Power Management (QMPM)

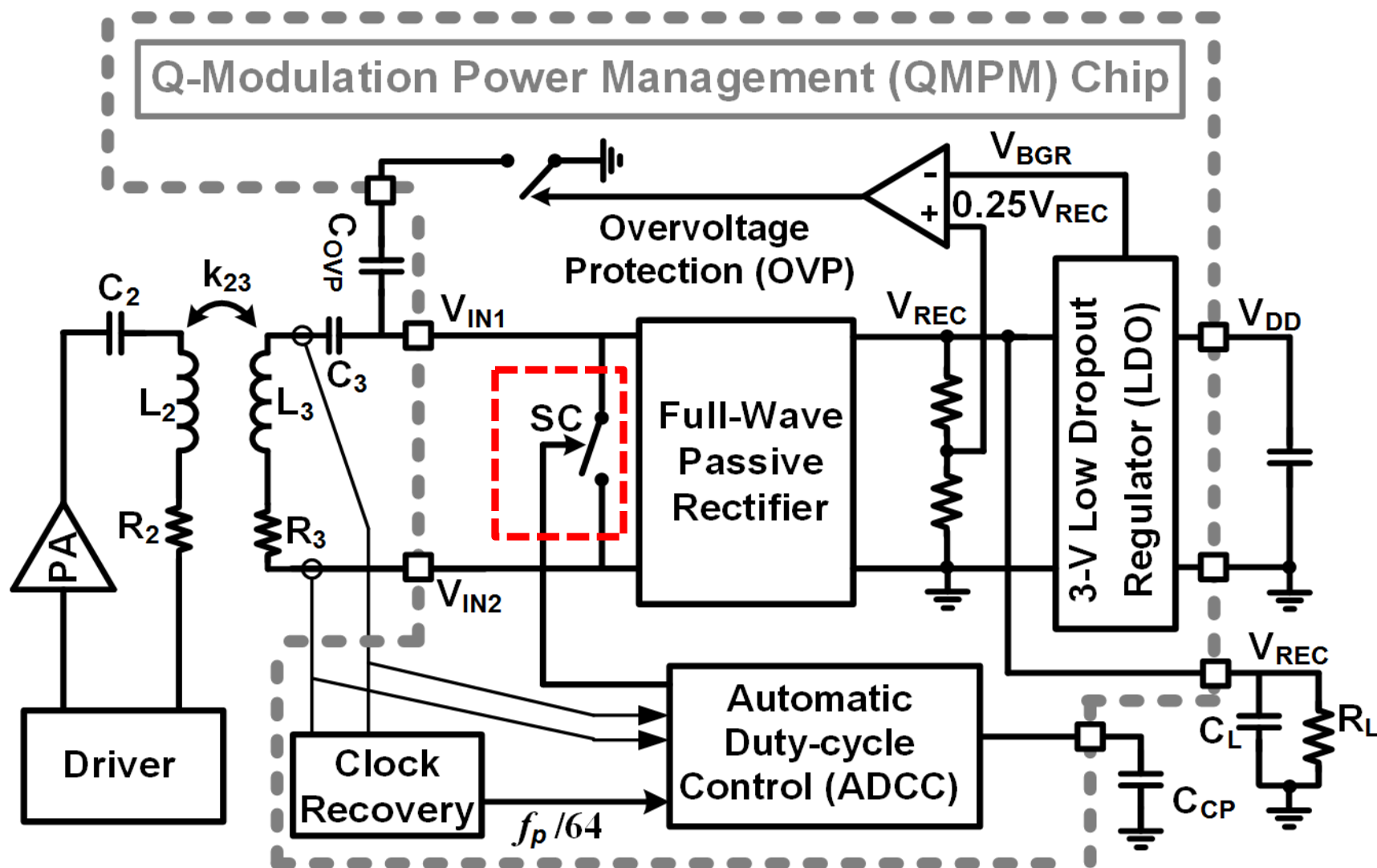


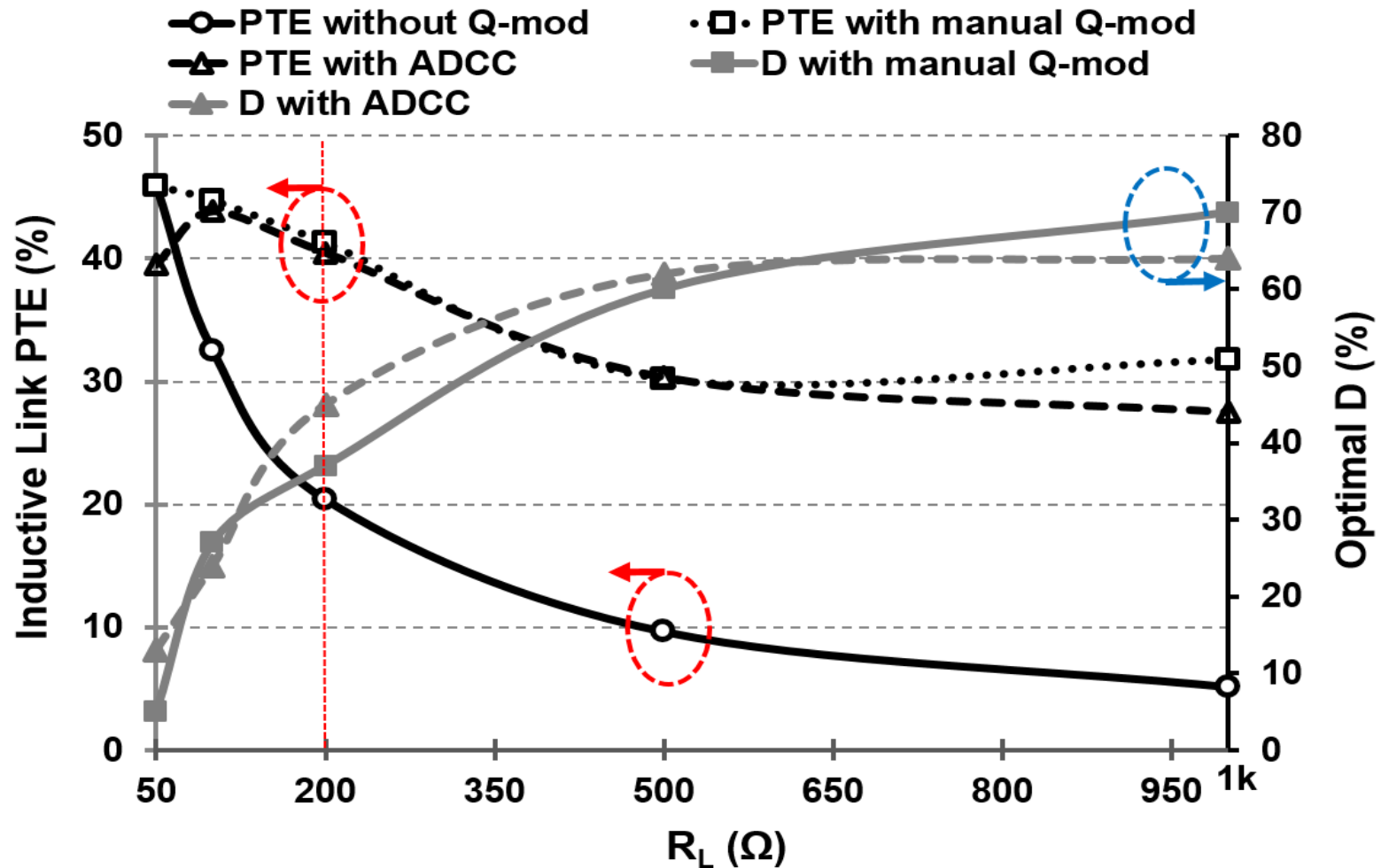Q-Modulation Measurement Results: Load Variation



With Q-modulation, PTE increases by **2x** at $R_L = 200 \Omega$!

QMPM Die Micrograph & Benchmarking

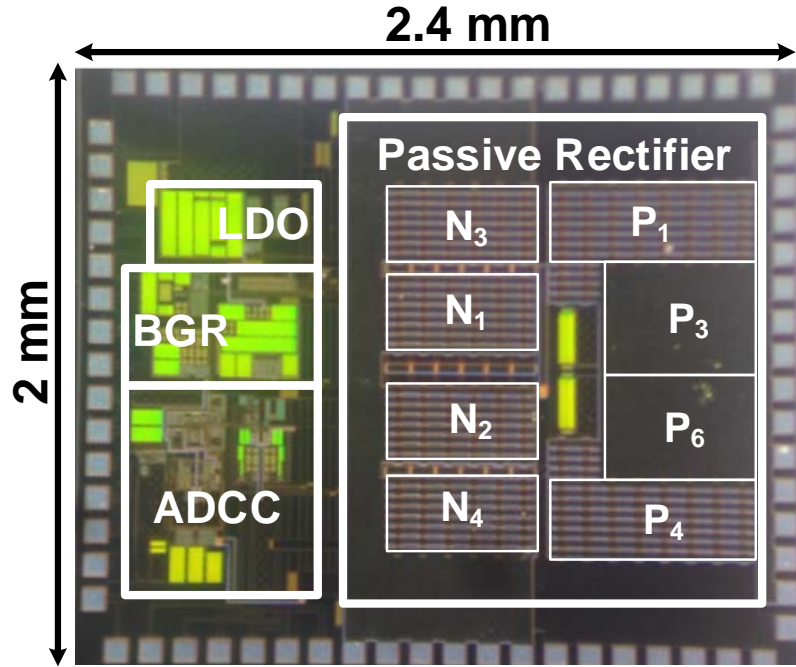


CMOS Technology		0.35 μ m 4M2P
Nominal Load		15 Ω
Rectifier Cap (C_L)		50 μ F
Die Area		4.8 mm ²
Tx/Rx Coils	Diameter	9 / 4 cm
	# of Turns	5 / 14
	Inductance	4.1 / 17.1 μ H

Publication	Choi, ISSCC13	Lee, ISSCC12	Lu, ISSCC13	This Work
Freq (MHz)	6.78	13.56	13.56	2
V_{REC} (V)	5	3.1	4	4.5
Max Power (W)	6	0.037	0.032	1.45
Meas. PCE (%)	86	77	84	75
Load Matching	NO	NO	NO	YES

Outline


- Optimized Wireless Power Transfer Links
- **Power Conversion and Management Circuits**
 - **Active AC-DC Converter**
 - **Reconfigurable AC-DC converter**
 - **Adaptive Regulating Rectifier**
 - **Wireless Capacitor Charger**
- Low-Power Wireless Data Telemetry
- Conclusion

Inductively-Powered IMD Structure

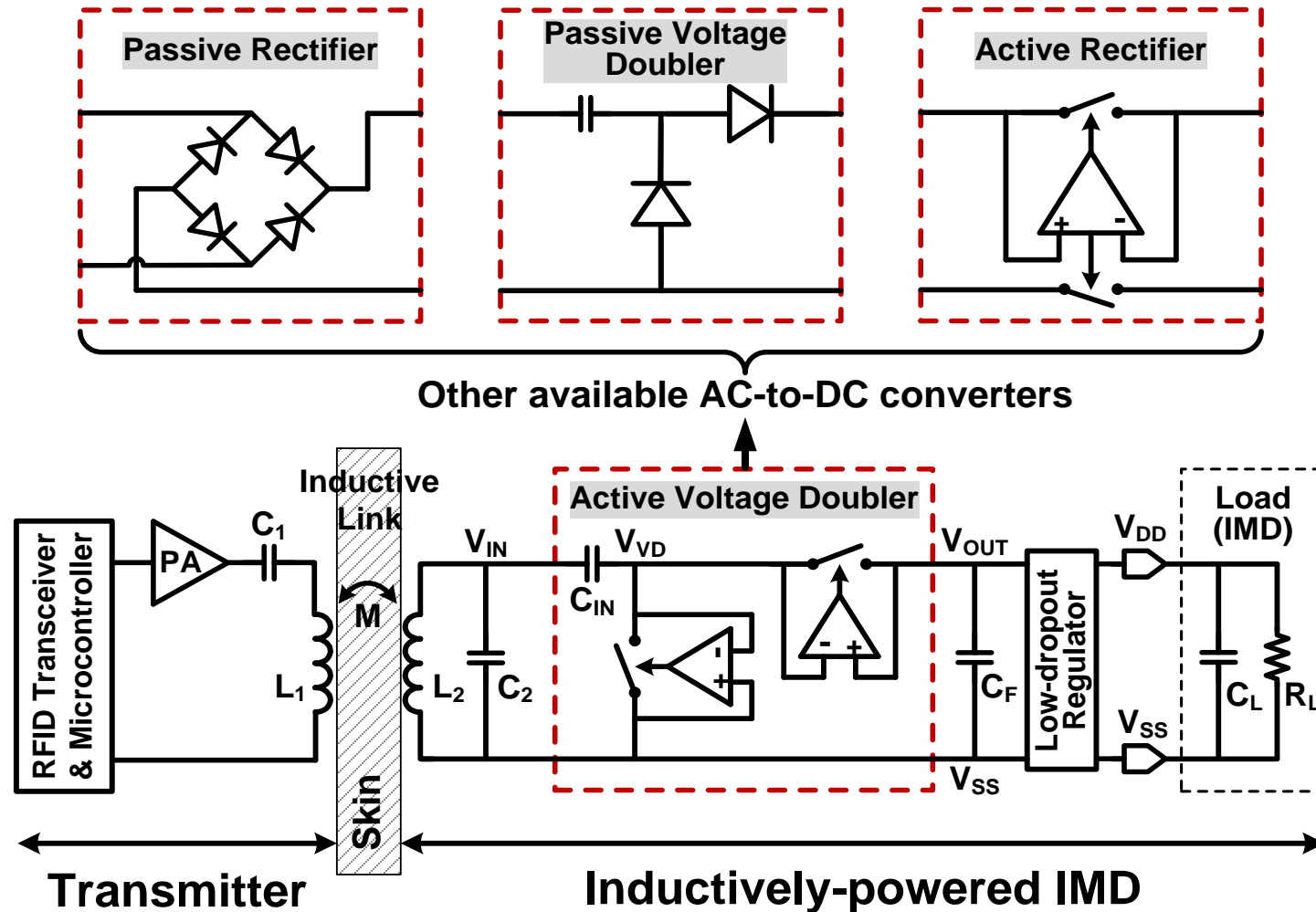


- **Comparator-based Active AC-DC converters** enable high power conversion efficiency (PCE) and low dropout voltage.

Full-Wave Active Rectifier

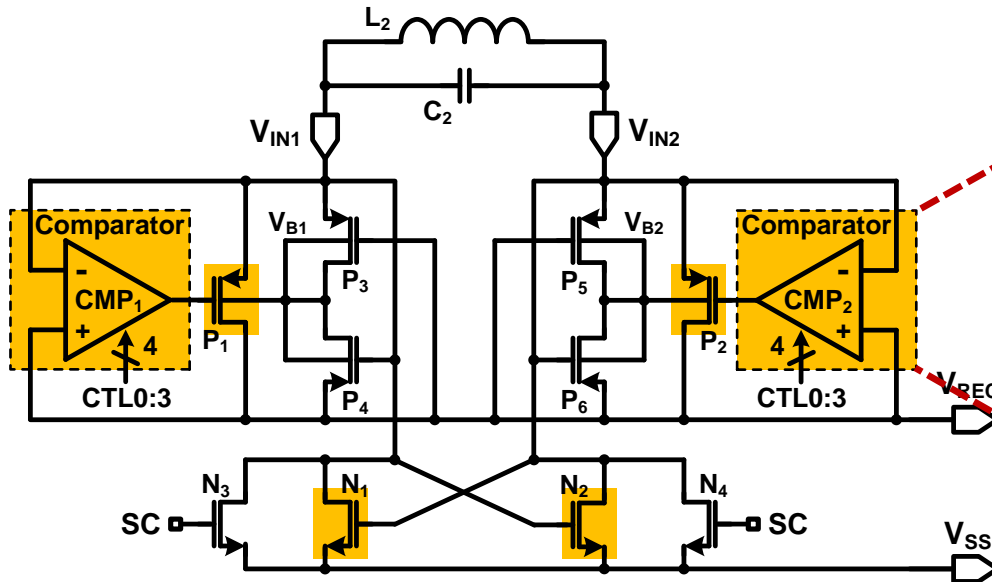


[Full-wave active rectifier]

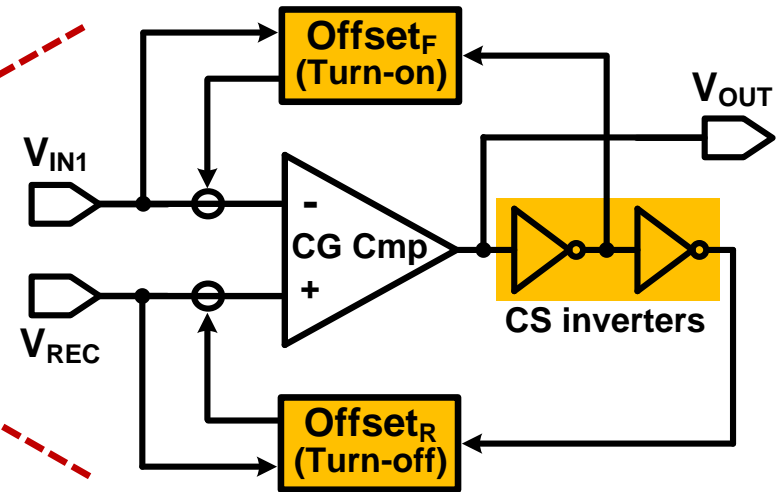

[Offset-controlled comparator]


- Rectifying switches are driven by **offset-controlled high-speed comparators** at 13.56MHz ISM band.
- Offset-control blocks inject offset currents to compensate for both turn-on and turn-off delays.
- High measured PCE of **80.2%** with 3.12V DC for 0.5kΩ load.

High-Speed Active Voltage Doubler

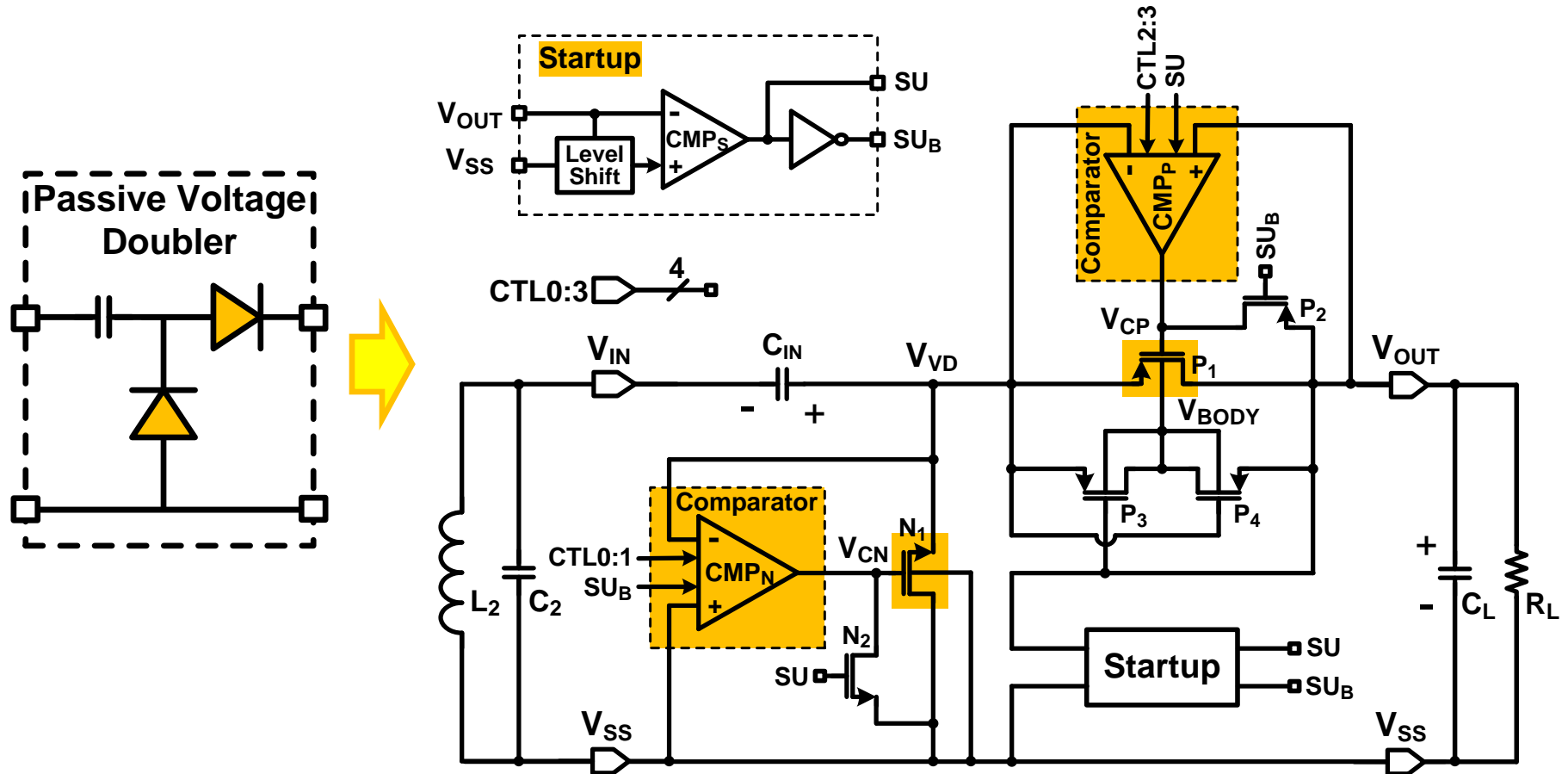

- Comparator-based active voltage doubler for high output voltage and high PCE @ 13.56MHz.
- **PCE = 79%** with 2.4V DC for 1k Ω load from 1.46V AC input.


Reconfigurable AC-DC Converter

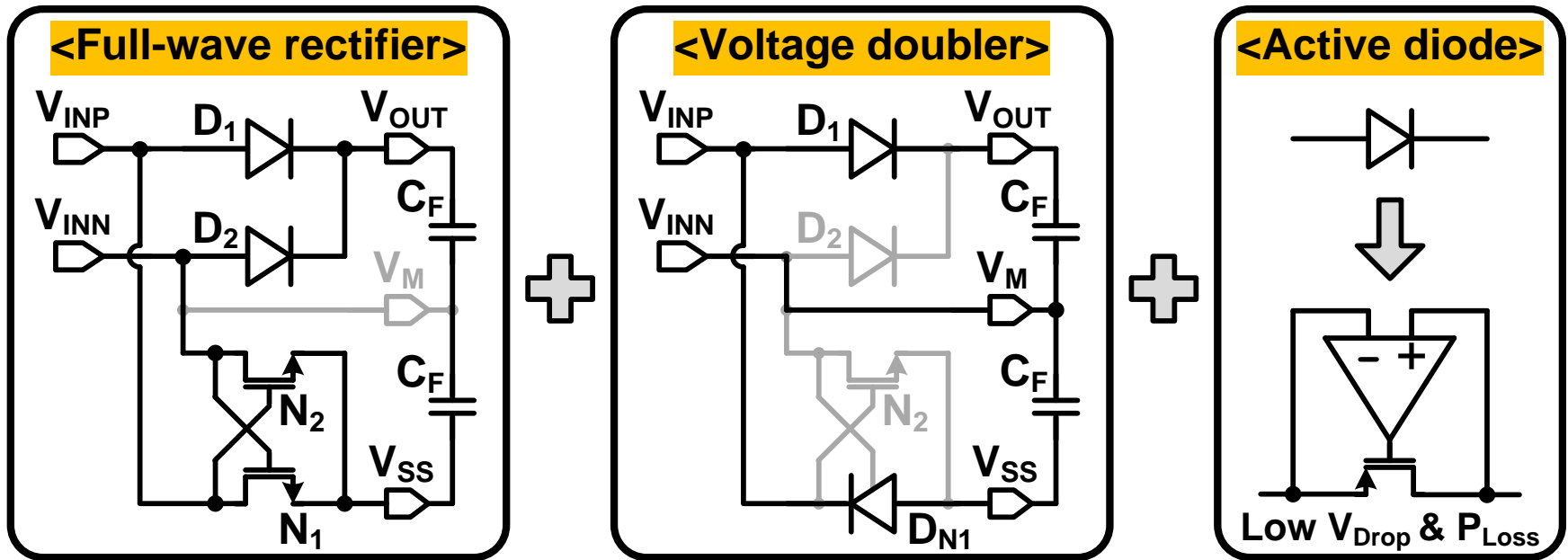

Combining two AC-DC mechanisms into a single circuit:

- VD/REC combines two AC-to-DC converters, i.e. a **full-wave rectifier** and a **voltage doubler**, into a single circuit.
- **Active diodes** driven by high-speed comparators lead to low dropout and high PCE in both VD and REC.





Adaptive Reconfigurable VD/REC

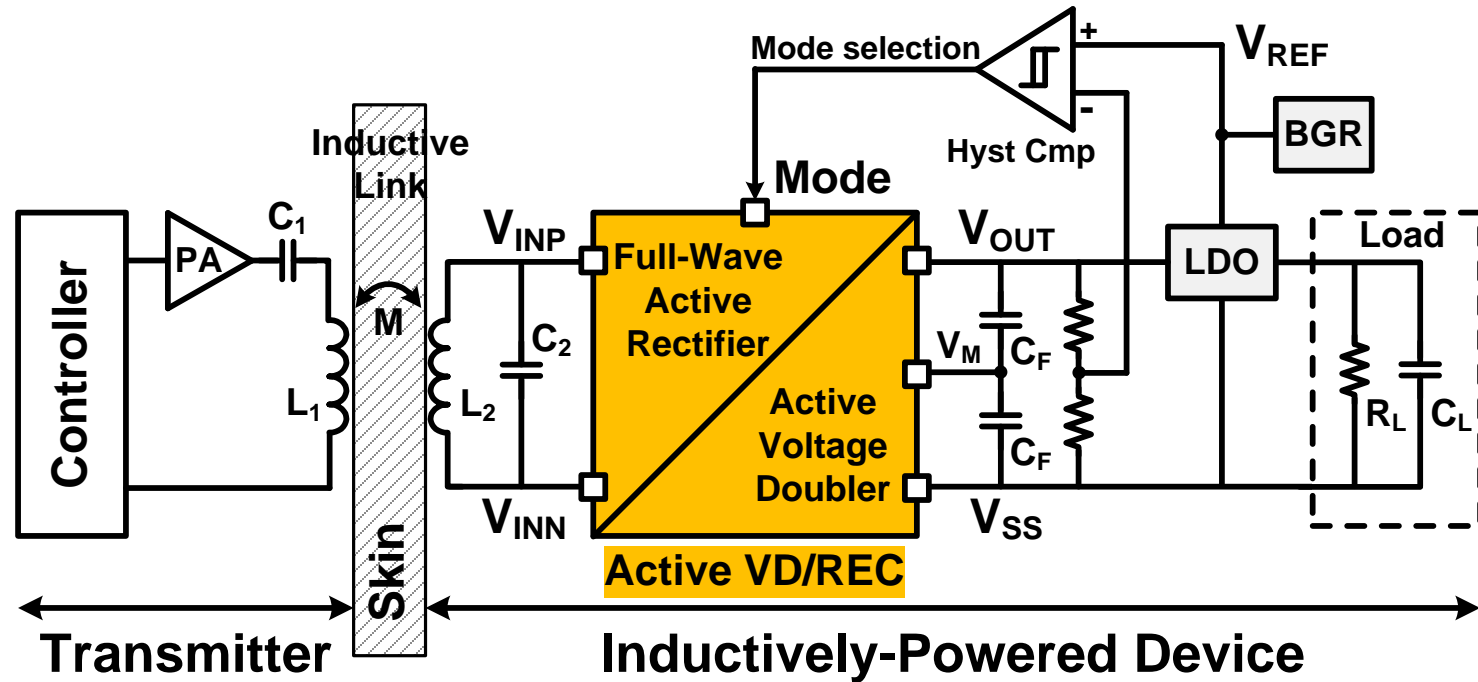

Condition	Mode	Operation	Key Feature
$V_{OUT} > V_{REF(Hyst)}$	0	Full-wave rectifier	High power efficiency (PCE)
$V_{OUT} < V_{REF(Hyst)}$	1	Voltage doubler	High output voltage (V_{OUT})


- Adaptive mode control for rectification or voltage doubling
- Extended-range inductive power transmission
- High PCE (70% VD / 77% REC) with active diodes

Power Transmission Range

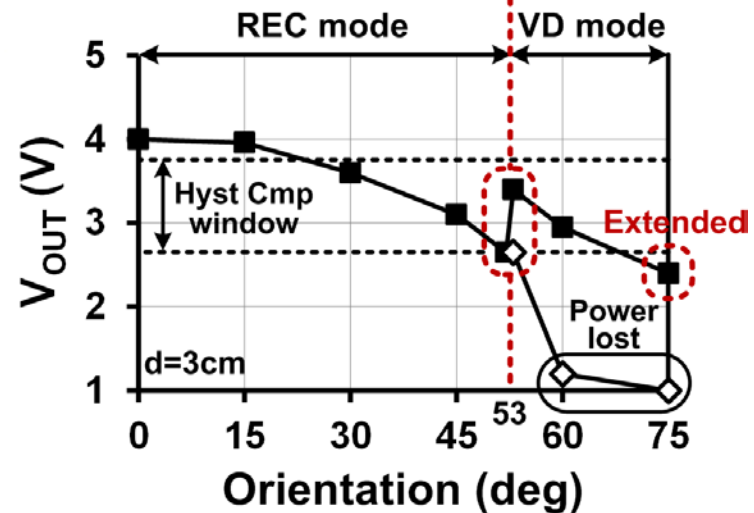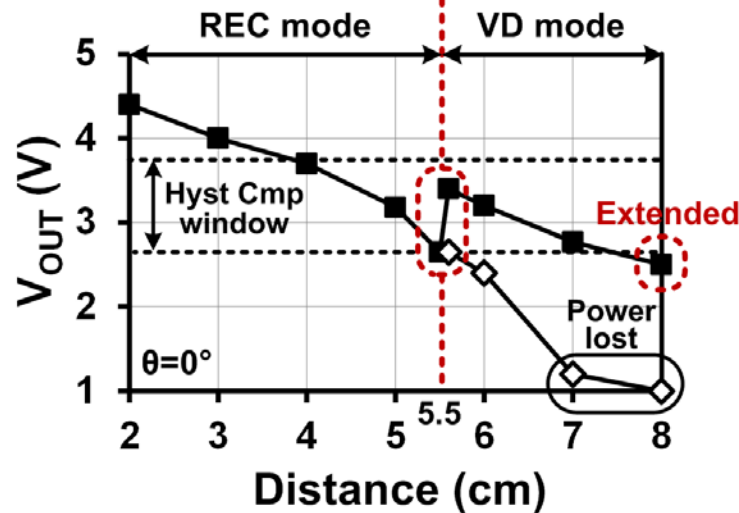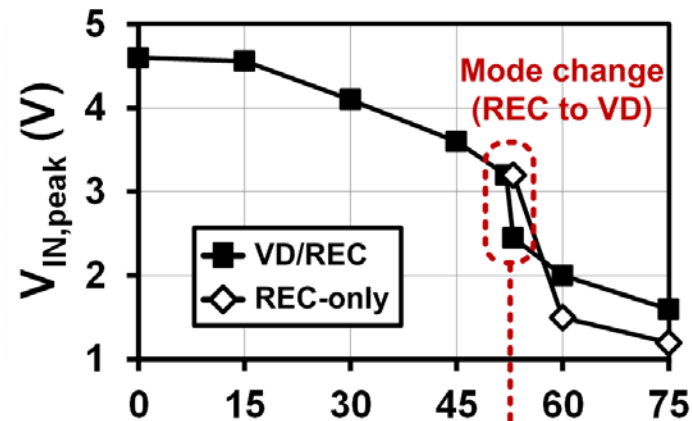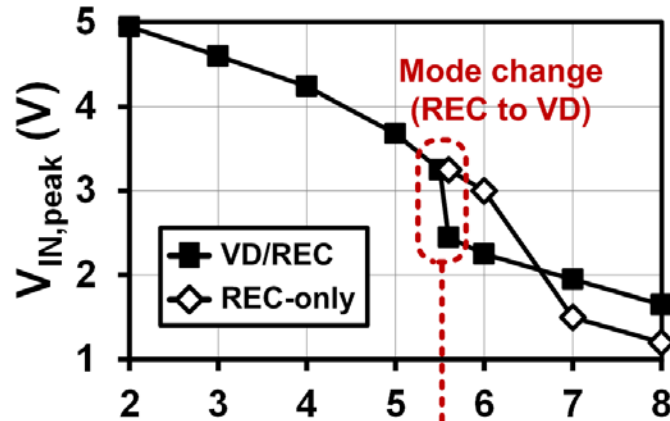

- VD/REC extends power transmission range by 33% (6cm to 8cm) in coil distance and 41.5% (53° to 75°) in coil orientation, compared to using the rectifier only.



Adaptive Regulating Rectifier

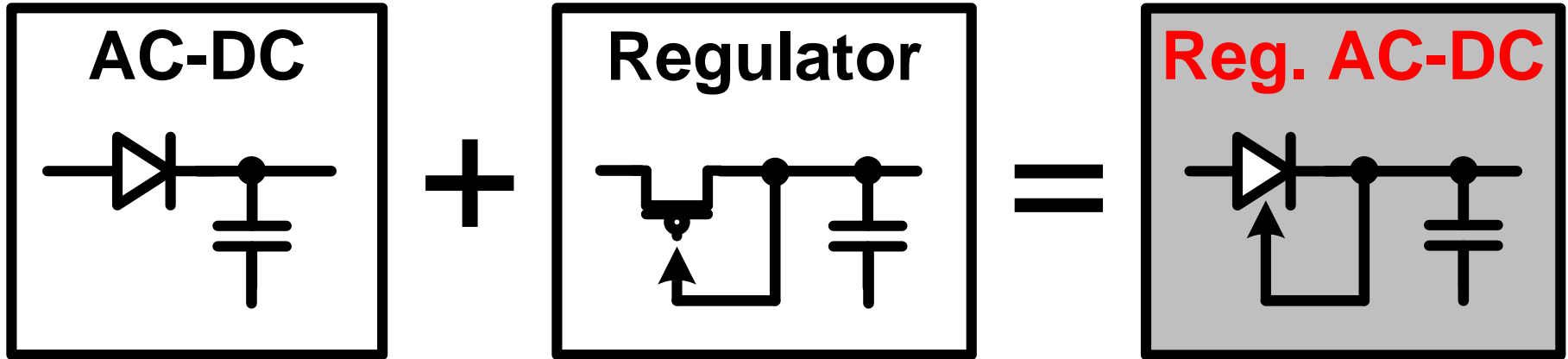

Combining AC-DC conversion and DC regulation into a single structure:

- Adaptive regulating rectifier combines an AC-DC converter and a regulator into a single structure
- Area & power-efficiency one-step power conversion/regulation
- Overall PCE up to 87% at 2MHz without using regulators

Adaptive Regulating Rectifier Concept

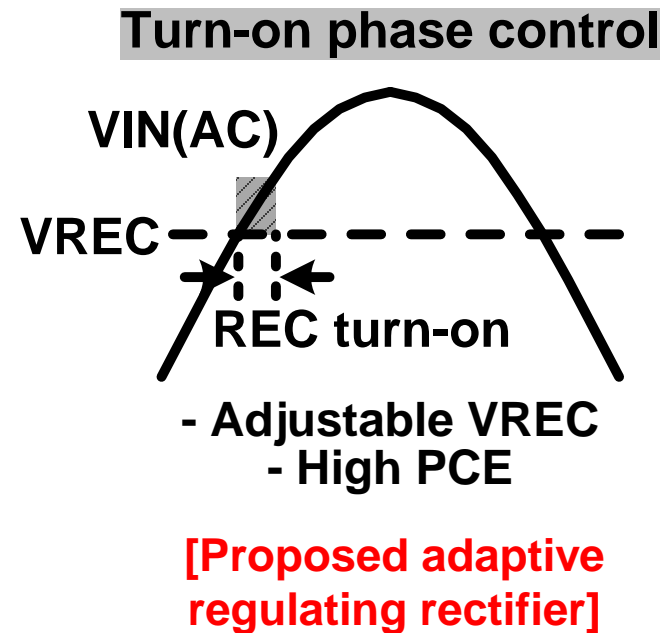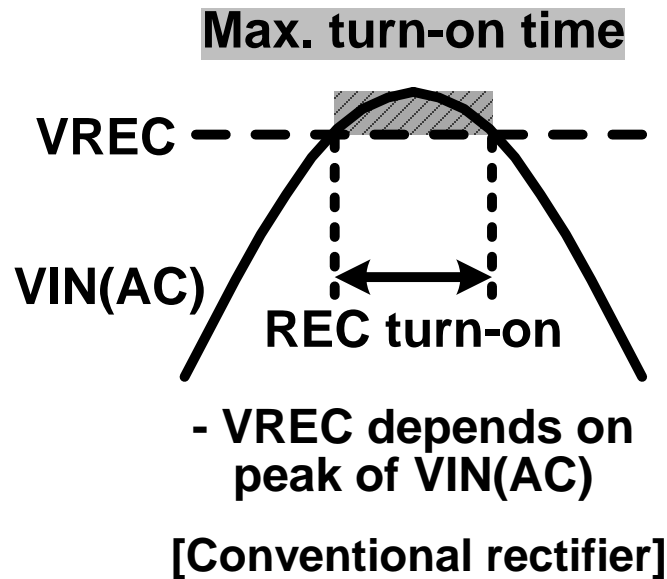


■ Conventional rectifier:

- V_{REC} depends on peak of $V_{IN(AC)}$ → V_{REC} is not adjustable.


■ Proposed adaptive regulating rectifier:

- Turn-off timing control → V_{REC} is adjustable.
- High PCE with small voltage drop between V_{REC} and $V_{IN(AC)}$.

Rectifier Phase Control Feedback

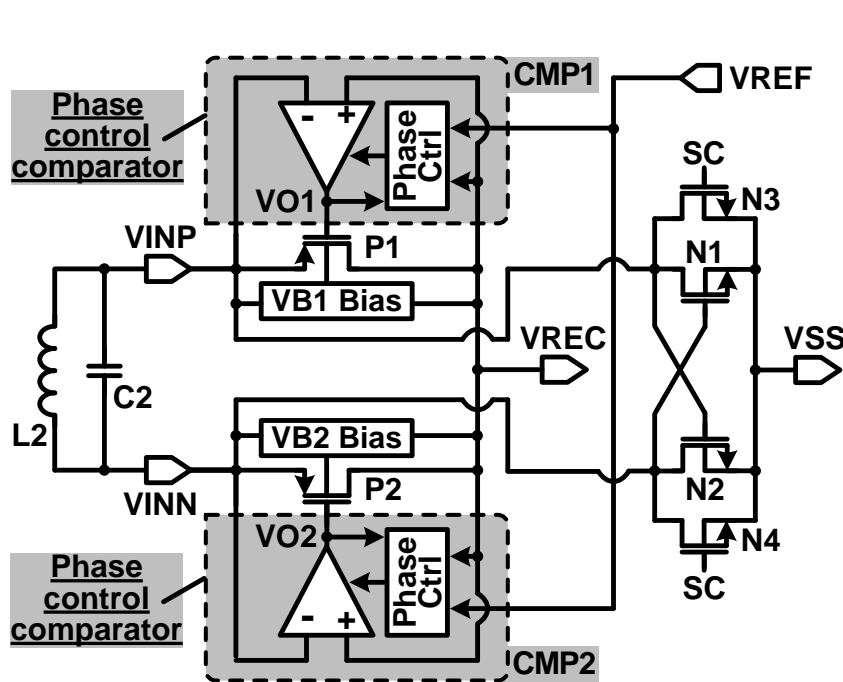


[Adaptive regulating rectifier]

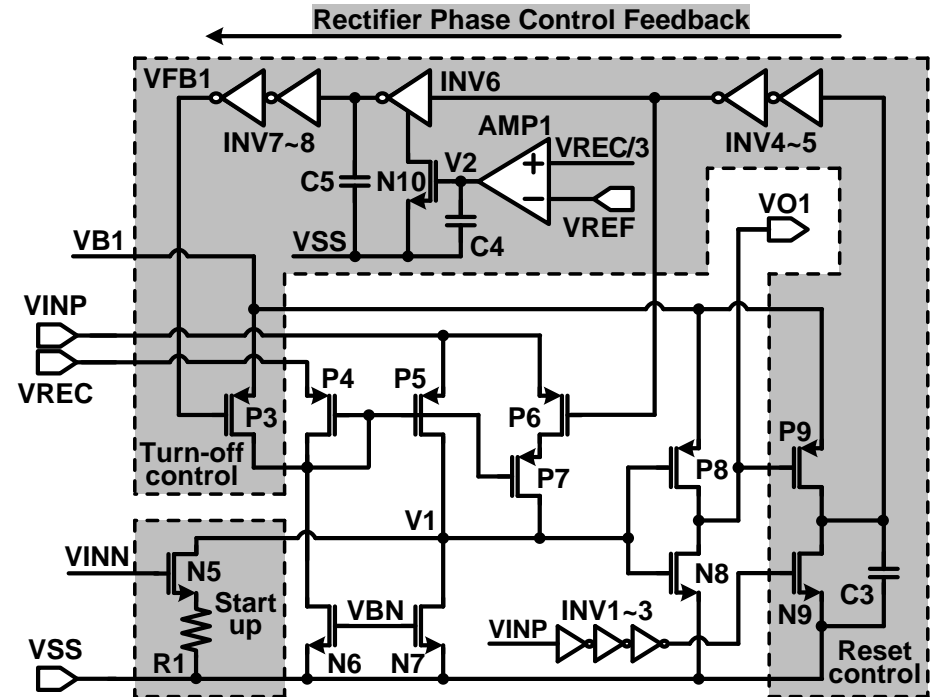

[Phase control comparator]

- Phase control feedback can be added to the conventional comparator to control the rectifier turn-off time.
- Phase control feedback turns off the rectifier after a variable time delay to adjust V_{REC} for a target output voltage.


Regulating Rectifier Waveforms & PCE

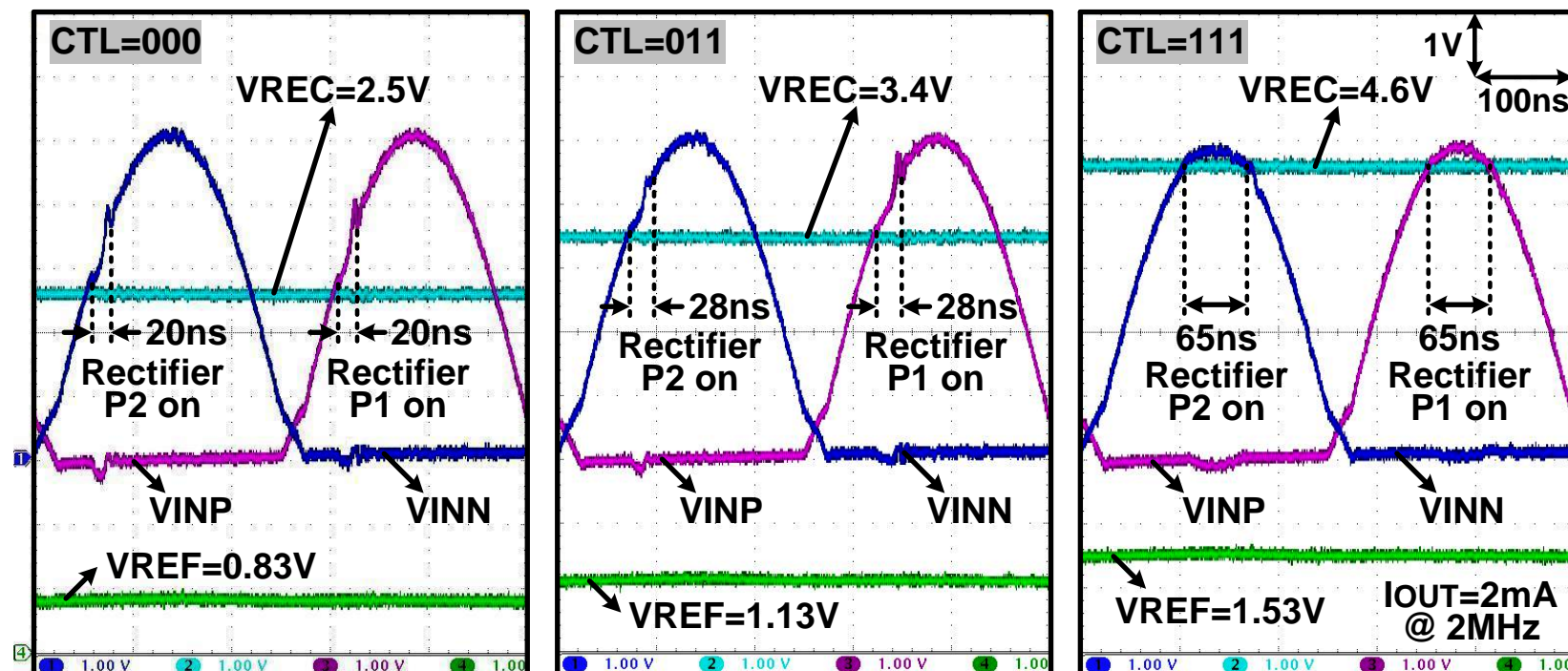

When the peak input voltage is constant at 5V:


- The regulating rectifier generates adjustable V_{REC} from 2.5V to 4.6V (3-bit) by adjusting the rectifier turn-on phase.
- The regulating rectifier still achieves high PCE of 72~87% at 2MHz when $V_{REC} = 2.5\sim 4.6\text{V}$ and $I_{OUT} = 2.8\text{mA}$.

Efficient Wireless Capacitor Charger

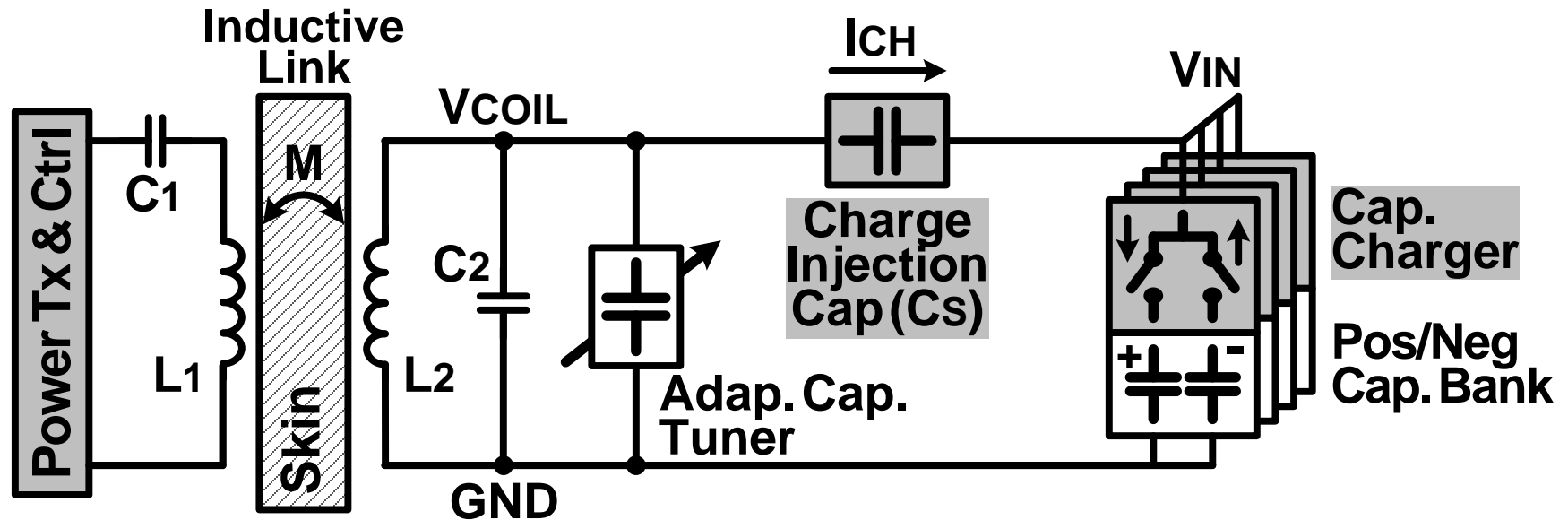


- Direct pos/neg capacitor charging from AC coil voltage (V_{COIL})
- A charge injection capacitor (C_s) & a capacitor charger switch generate a fixed amount of charging current (I_{CH}).
- Fixed I_{CH} reduces switching loss, while C_s does not dissipate power, maximizing capacitor charging efficiency (82% @ $\pm 2V$).

Wireless Capacitor Charger Operation

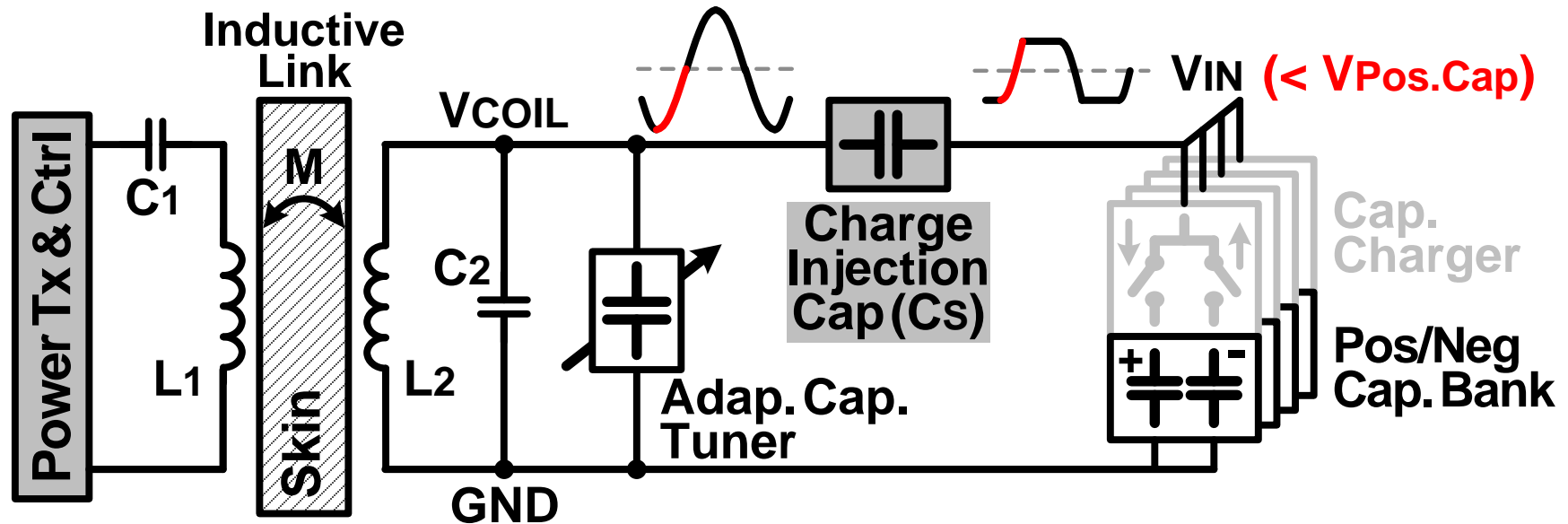


- Direct pos/neg capacitor charging from AC coil voltage (V_{COIL})
- A charge injection capacitor (C_s) & a capacitor charger switch generate a fixed amount of charging current (I_{CH}).
- Fixed I_{CH} reduces switching loss, while C_s does not dissipate power, maximizing capacitor charging efficiency (82% @ $\pm 2V$).

Wireless Capacitor Charger Operation

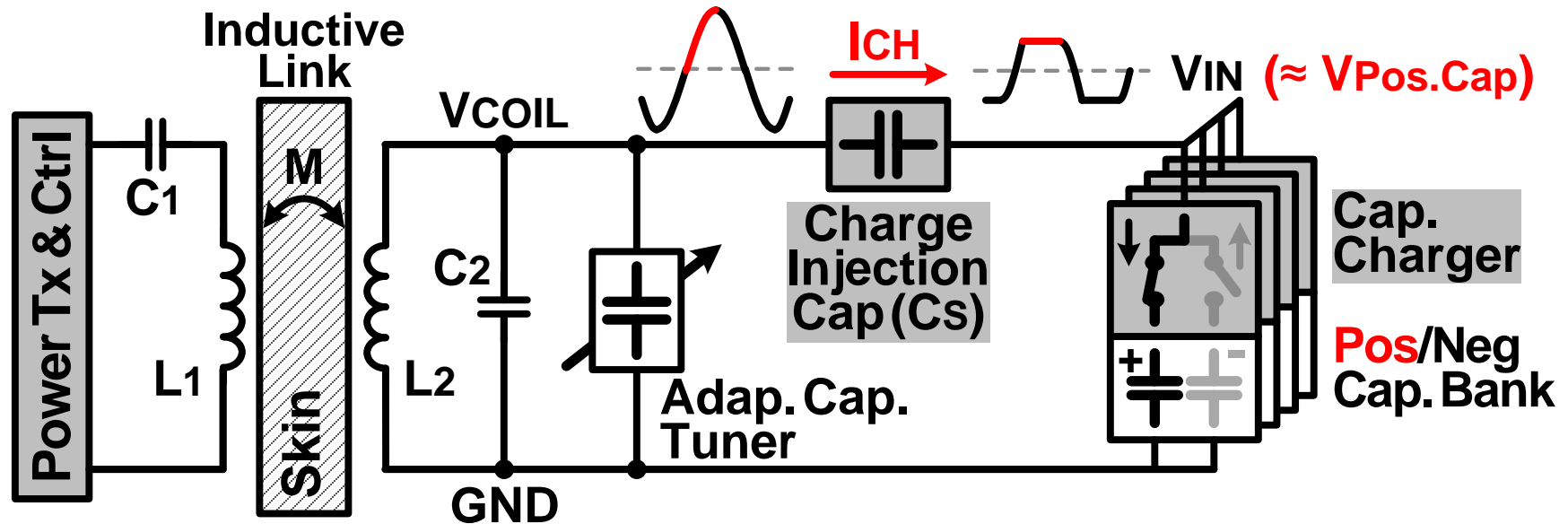


- Direct pos/neg capacitor charging from AC coil voltage (V_{COIL})
- A charge injection capacitor (C_s) & a capacitor charger switch generate a fixed amount of charging current (I_{CH}).
- Fixed I_{CH} reduces switching loss, while C_s does not dissipate power, maximizing capacitor charging efficiency (82% @ $\pm 2V$).

Wireless Capacitor Charger Operation

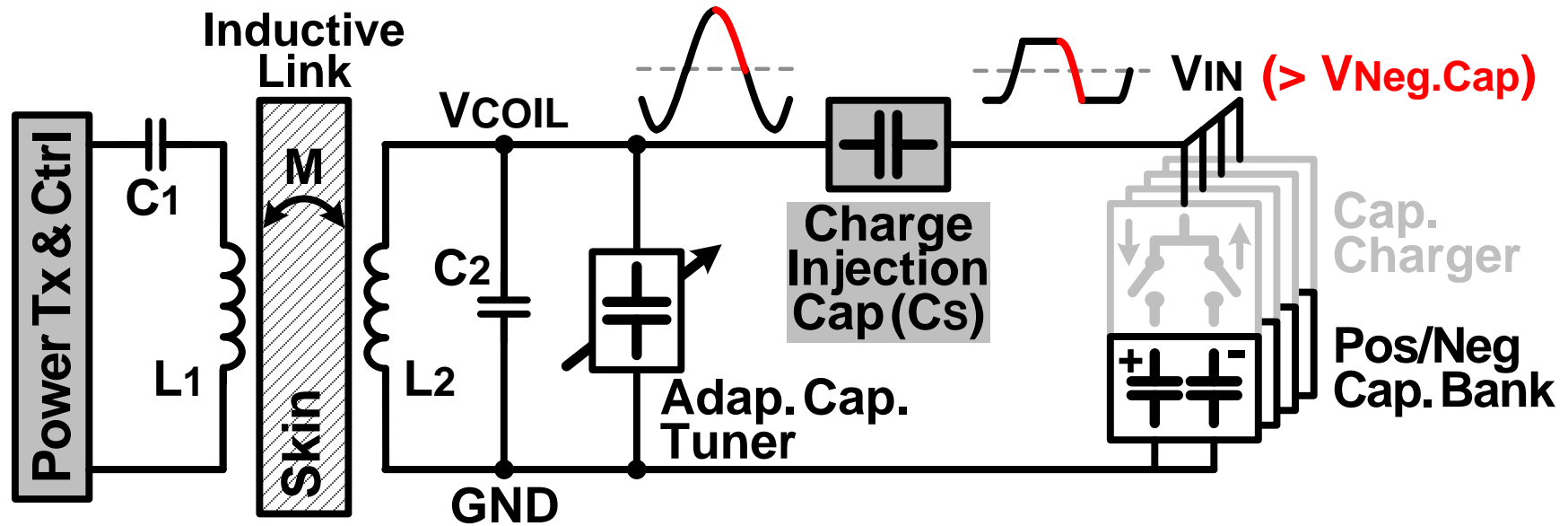


- Direct pos/neg capacitor charging from AC coil voltage (V_{COIL})
- A charge injection capacitor (C_s) & a capacitor charger switch generate a fixed amount of charging current (I_{CH}).
- Fixed I_{CH} reduces switching loss, while C_s does not dissipate power, maximizing capacitor charging efficiency (82% @ $\pm 2V$).

Wireless Capacitor Charger Operation

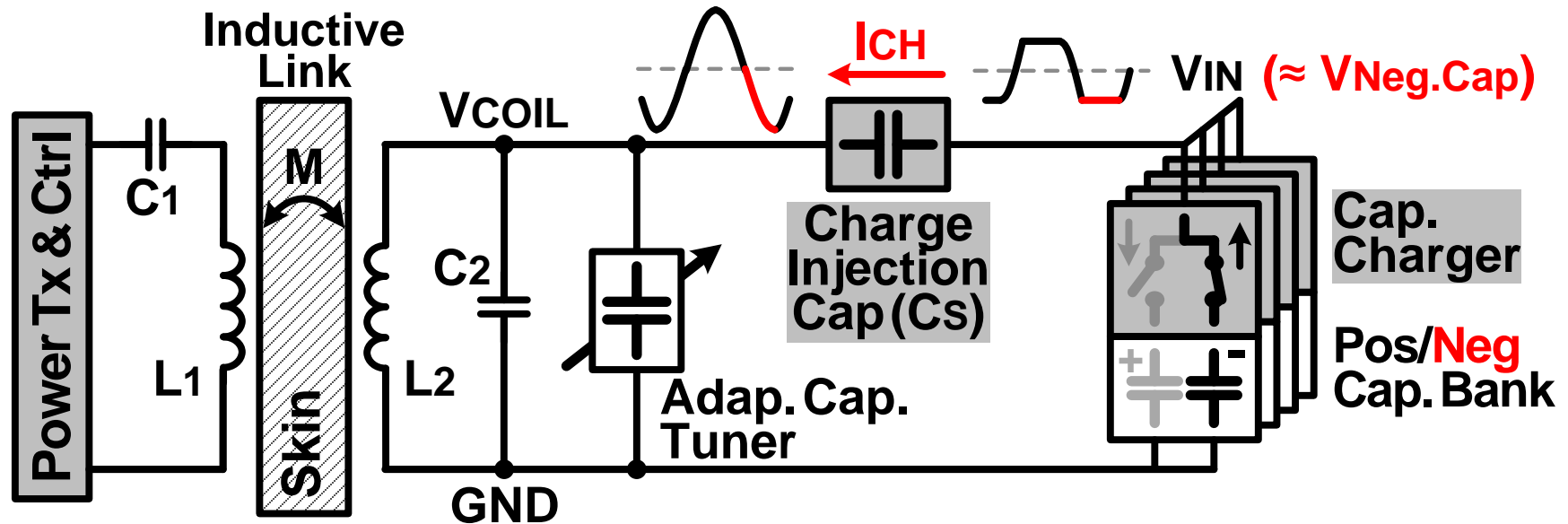


- Direct pos/neg capacitor charging from AC coil voltage (V_{COIL})
- A charge injection capacitor (C_s) & a capacitor charger switch generate a fixed amount of charging current (I_{CH}).
- Fixed I_{CH} reduces switching loss, while C_s does not dissipate power, maximizing capacitor charging efficiency (82% @ $\pm 2V$).

Dual-Control Wireless Capacitor Charger

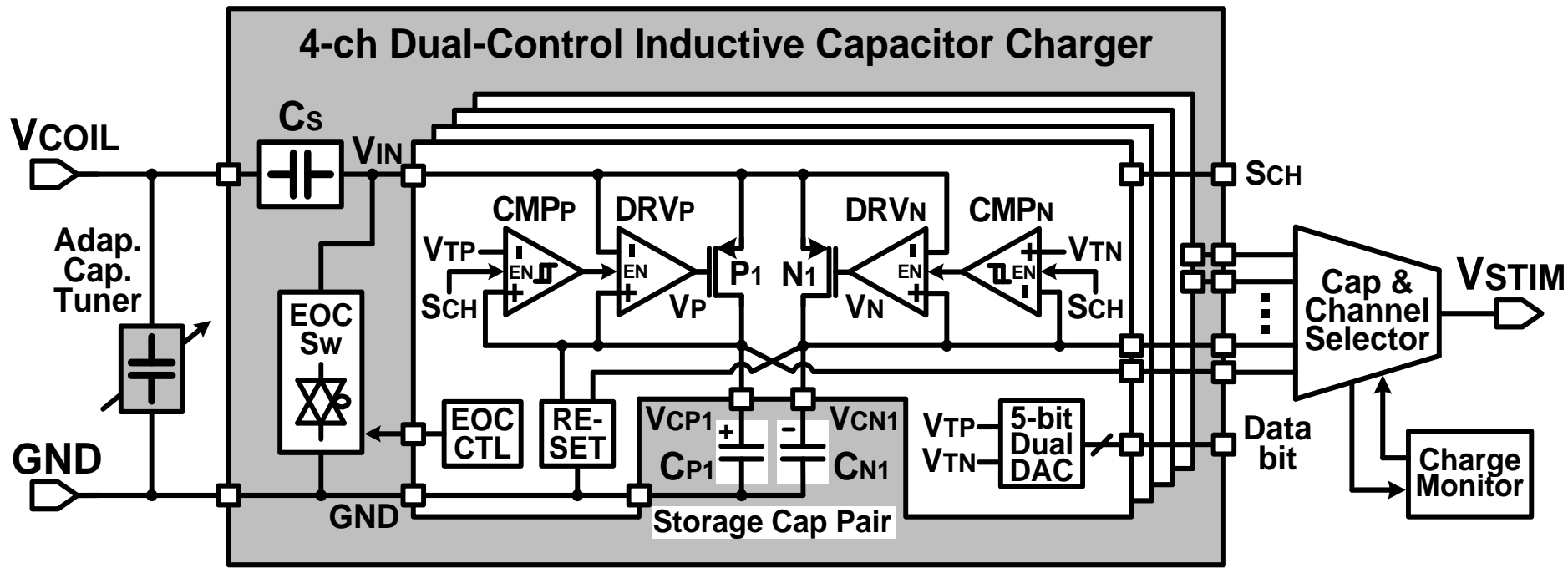


- Dual-voltage control capability for separately charging pos/neg capacitors to their designated target voltages
- Capacitor reset function
- Adaptive capacitor tuning

Adaptive Resonant Capacitor Tuner

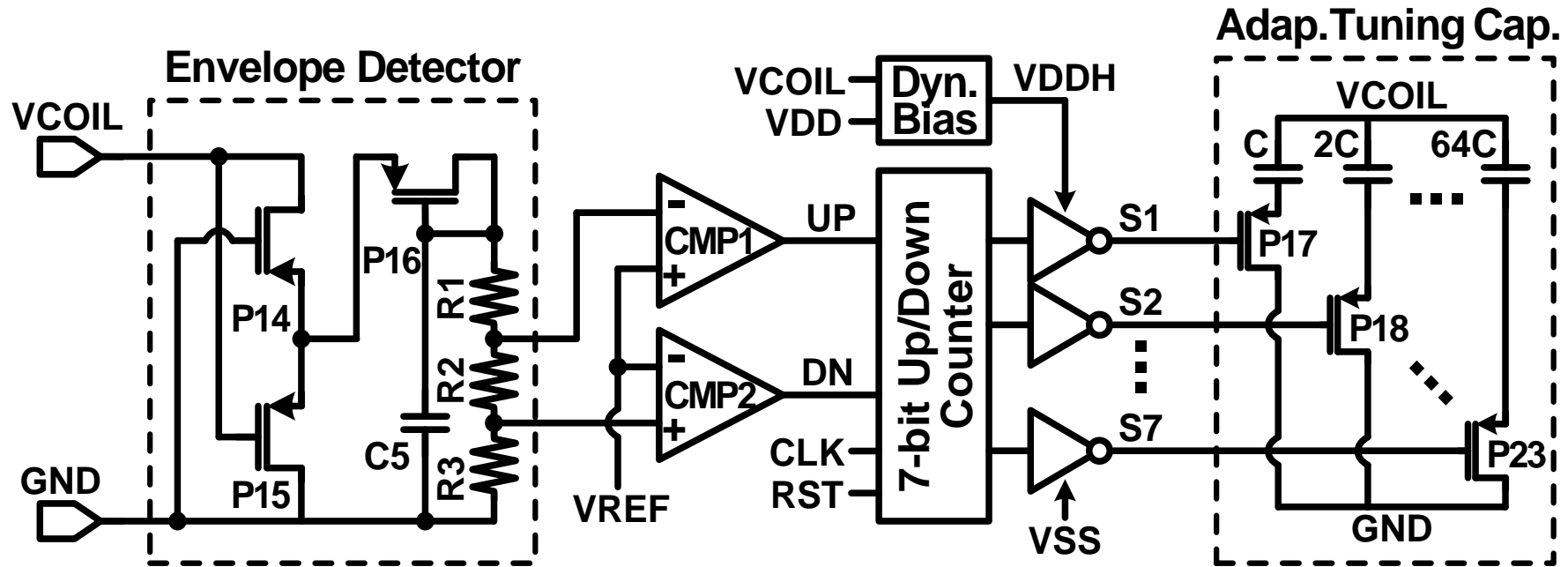


- Effective resonance capacitance varies during charging.
- Coil amplitude detection & comparison
- Adaptive 7-bit tuning capacitors

Adaptive Capacitor Tuner Waveforms

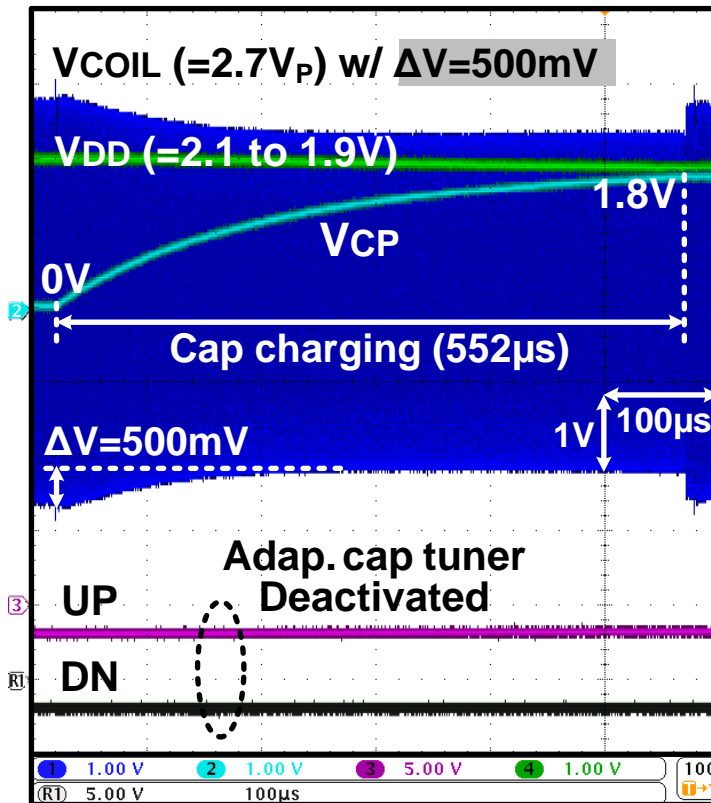


[Adaptive cap. tuner deactivated]

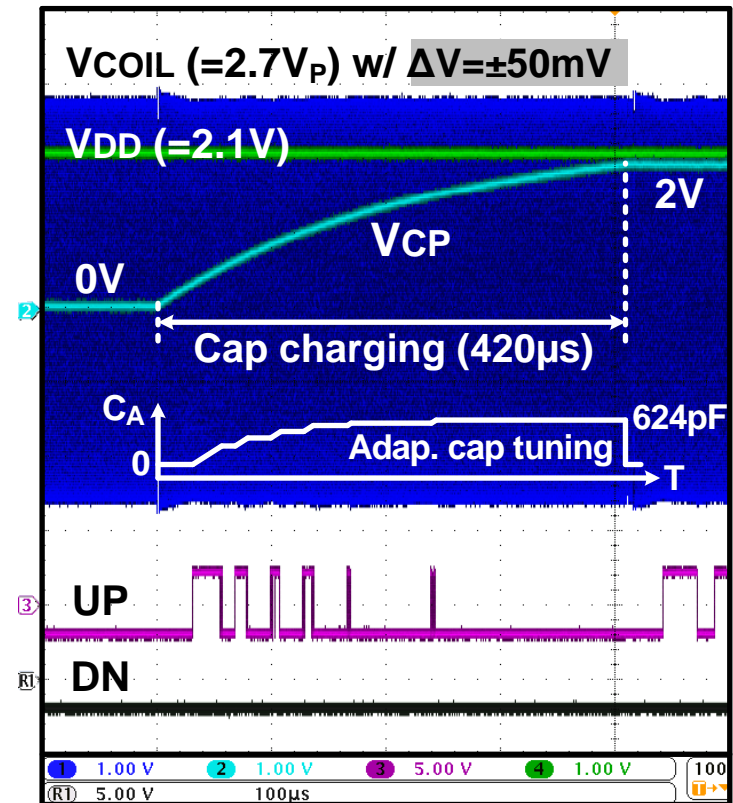

[Adaptive cap. tuner activated]

- During charging, resonant capacitance variation decreases the V_{COIL} amplitude, limiting the proper charging operation.
- An adaptive capacitor tuner keeps V_{COIL} amplitude constant.

Capacitor Charging Efficiency & Time

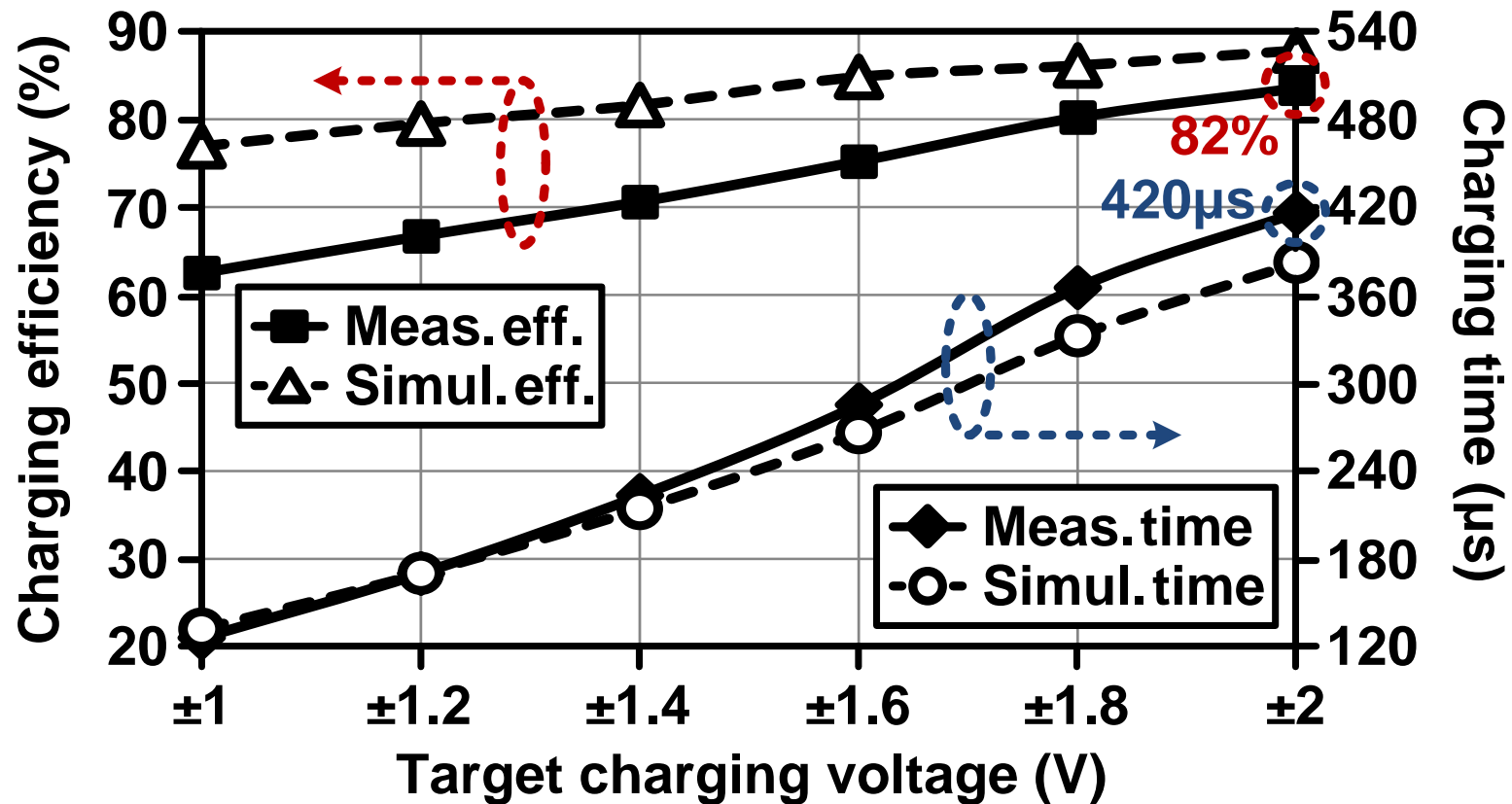


- With 2.7V peak AC input at 2MHz, a pair of $1\mu\text{F}$ capacitor can be charged up to $\pm 2\text{V}$ in $420\mu\text{s}$, achieving high measured charging efficiency of 82%.

Outline

- Optimized Wireless Power Transfer Links
- Power Conversion and Management Circuits
- **Low-Power Wireless Data Telemetry**
 - **Pulse Delay Modulation (PDM)**
 - **PDM Transceiver**
 - **PDM Measurement Results**
- Conclusion

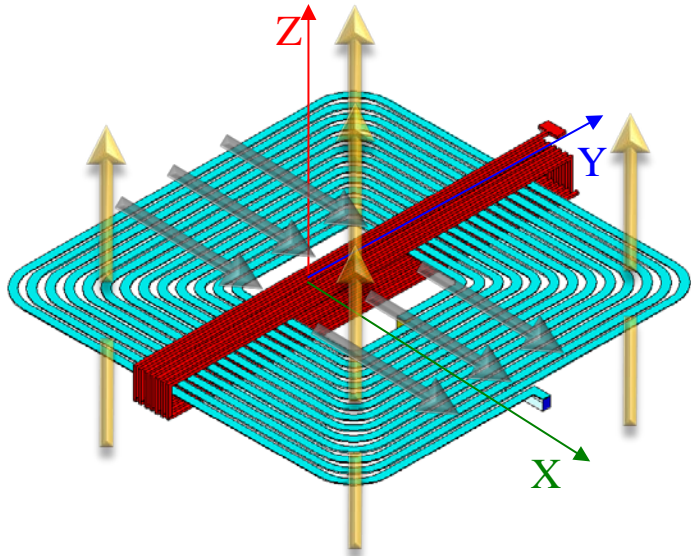Dual-Band Data/Power Transmission Using Two Pairs of Coils



Vertical coils



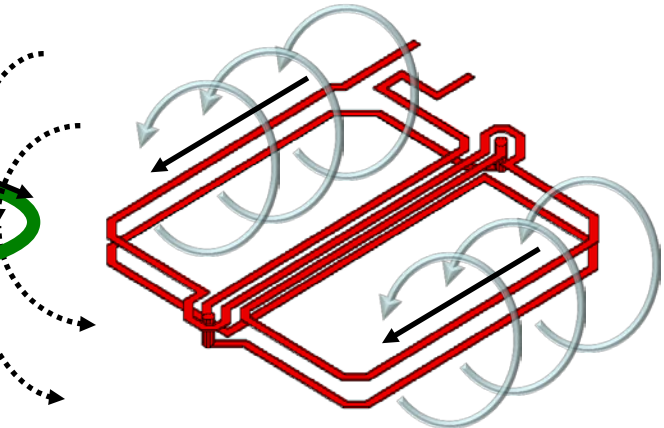
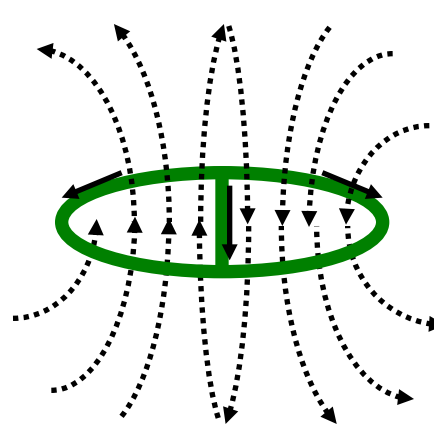
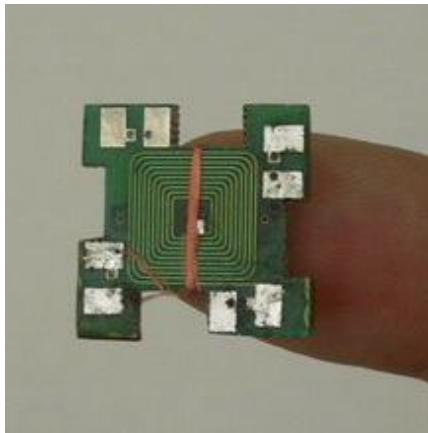


Figure-8 coils

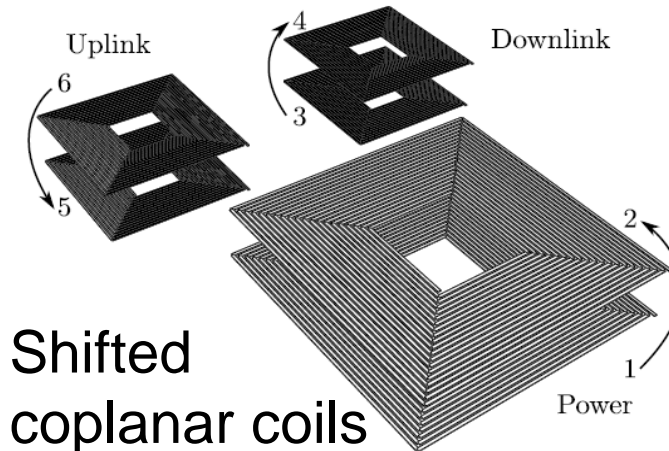

Shifted
coplanar coils

Simard and Sawan

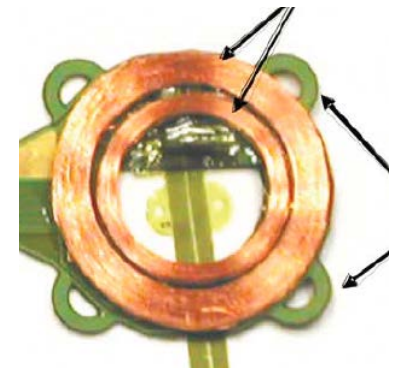


Coaxial coils


S. Kelly et al. and W. Liu et al.

Pulse Delay Modulation (PDM) using a Dual-Band Power/Data Link

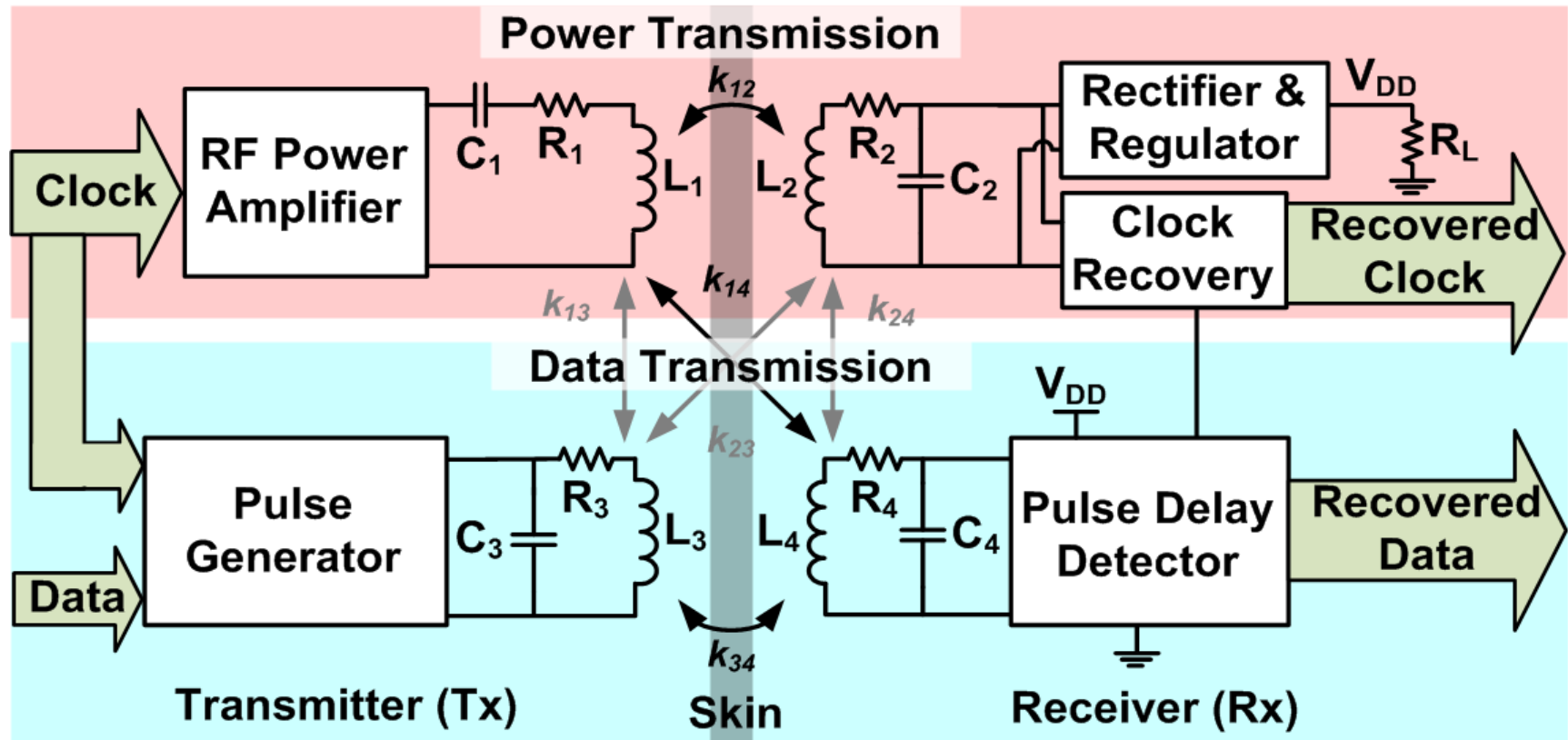- Pulse-Based data transmission using a **separate** data link by modulating the **zero-crossings** of the undesired power carrier interference across L_4C_4 -tank with short decaying ringing.




PDM Simulation in MATLAB


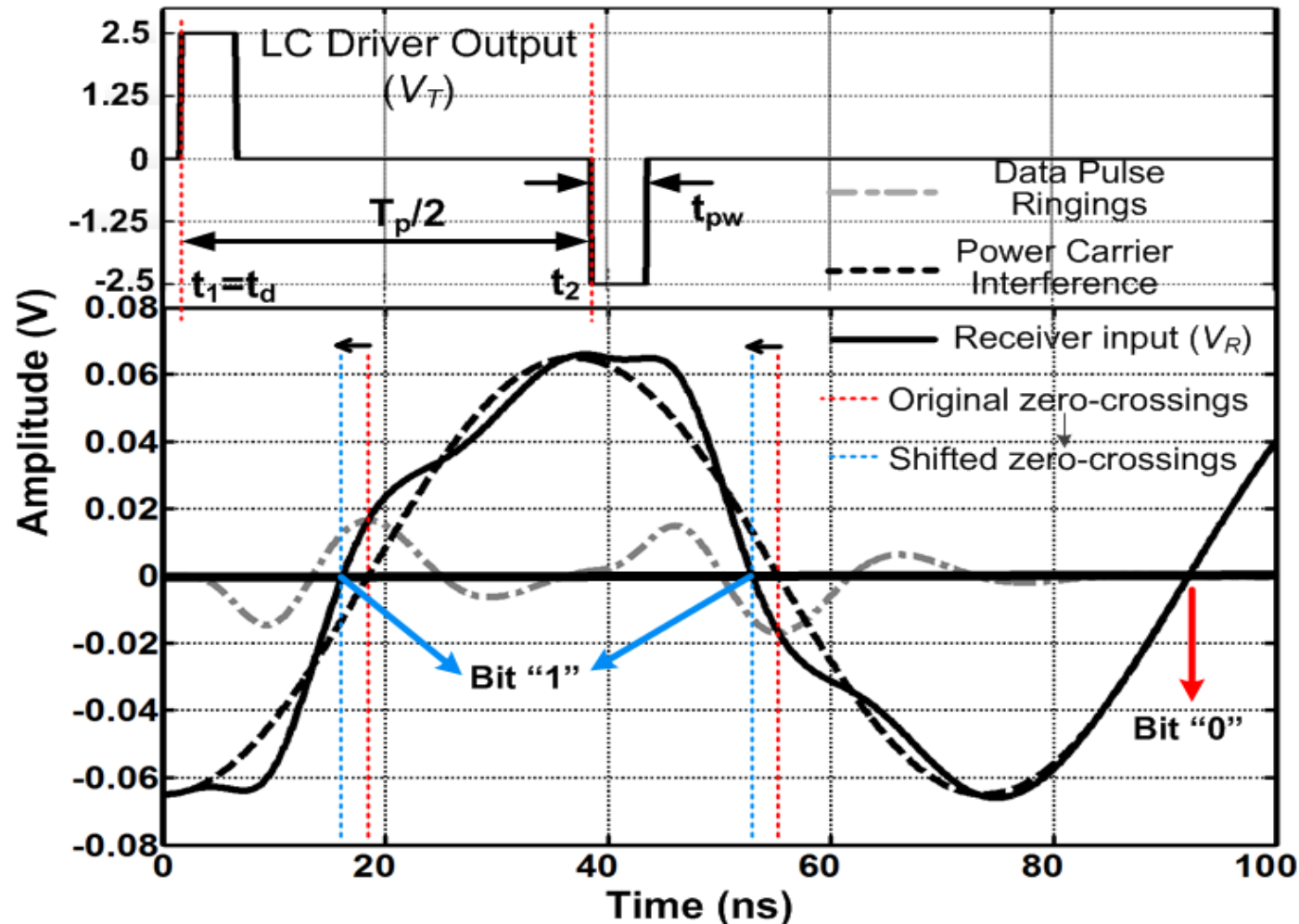


- Zero-crossing timing shift = 2.5 ns
- Signal-to-Interference Ratio (SIR) = -18.5 dB

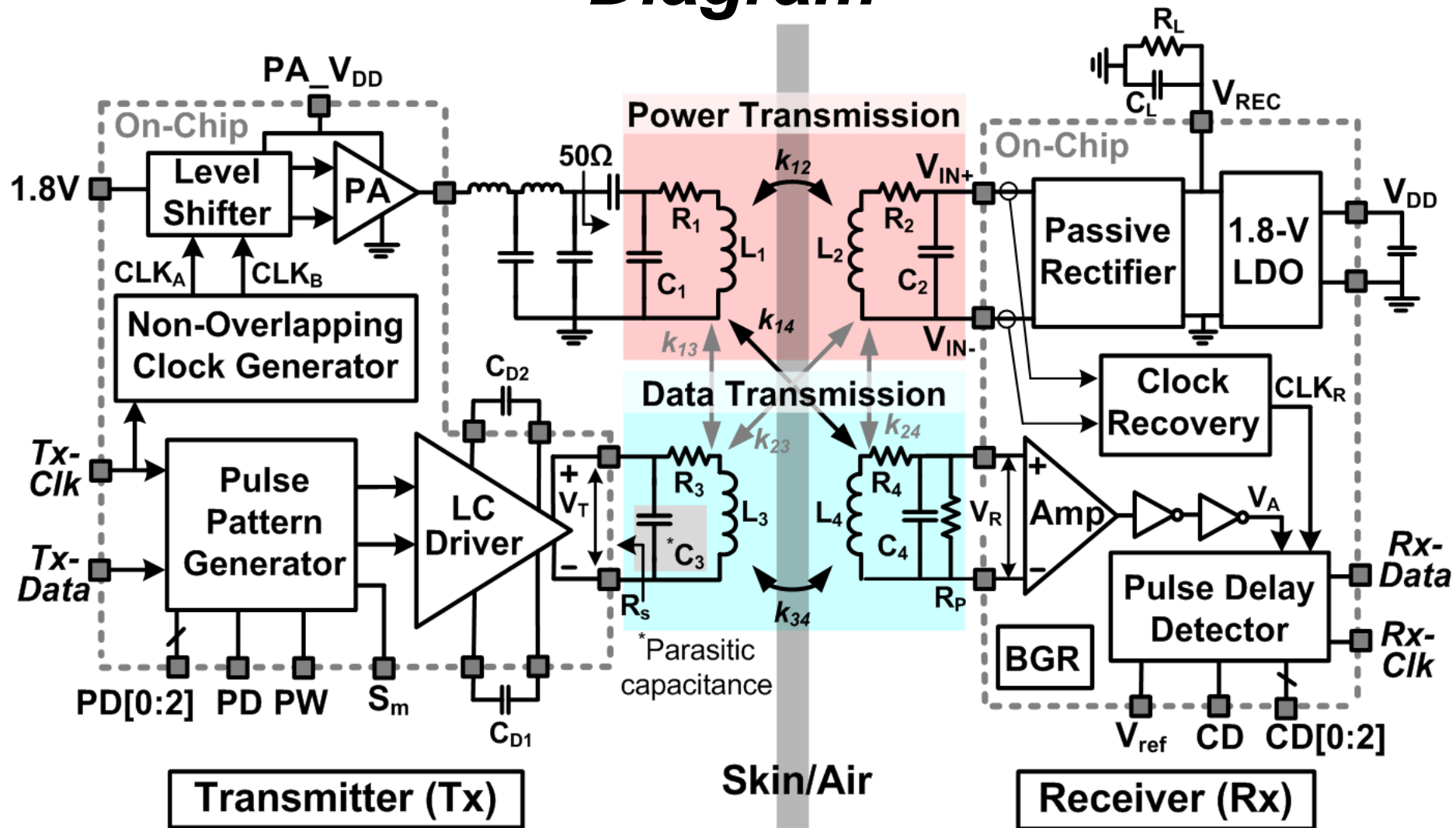Fully-integrated PDM-based Transceiver Diagram




PDM Implementation and Test Setup

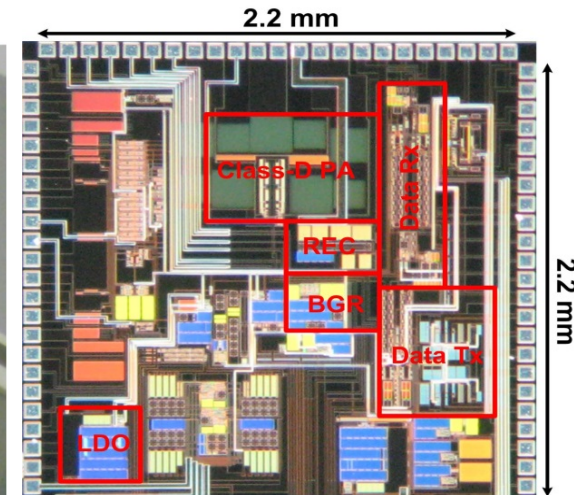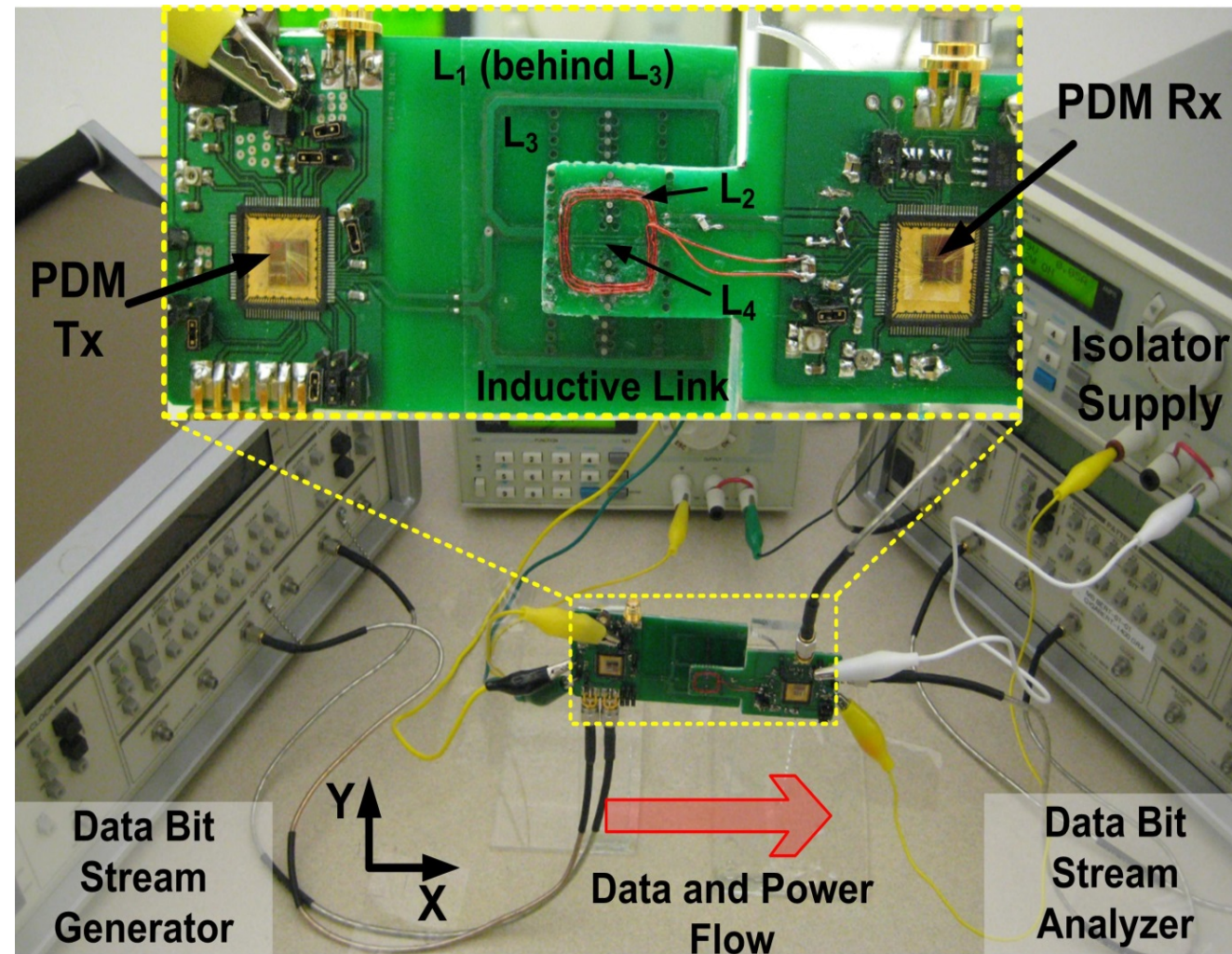


- Std. CMOS
TSMC 0.35- μ m
- Supply volt. =
1.8 V
- Operating freq.
= 13.56 MHz

PDM Measurement Results

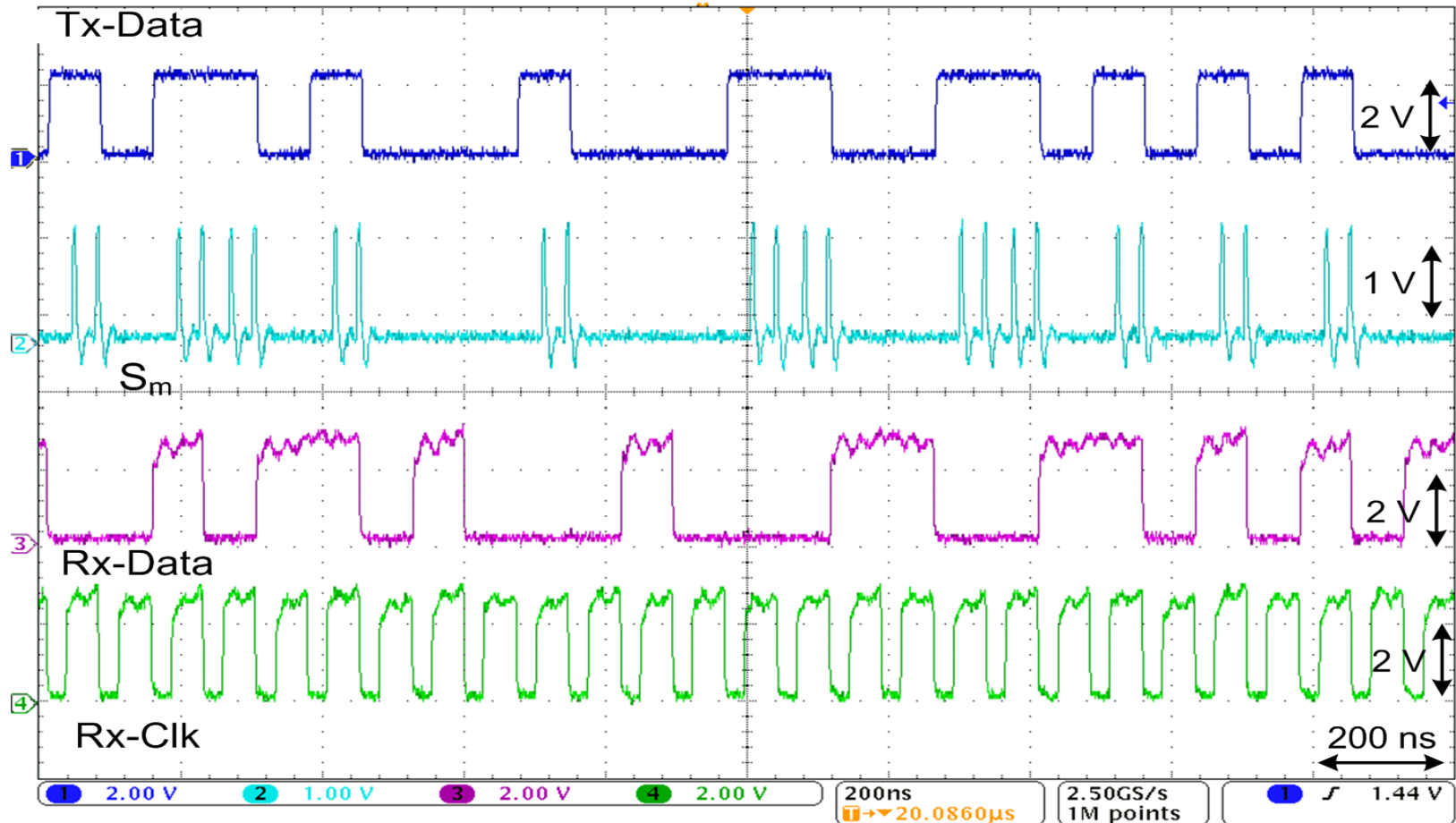

- Data rate = 13.56 Mbps
- Distance = 10 mm
- Power carrier = 13.56 MHz
- SIR = -18.5 dB
- Delivered power = 42 mW
- Bit error rate (BER) = 4.3×10^{-7}

PDM Measurement Results

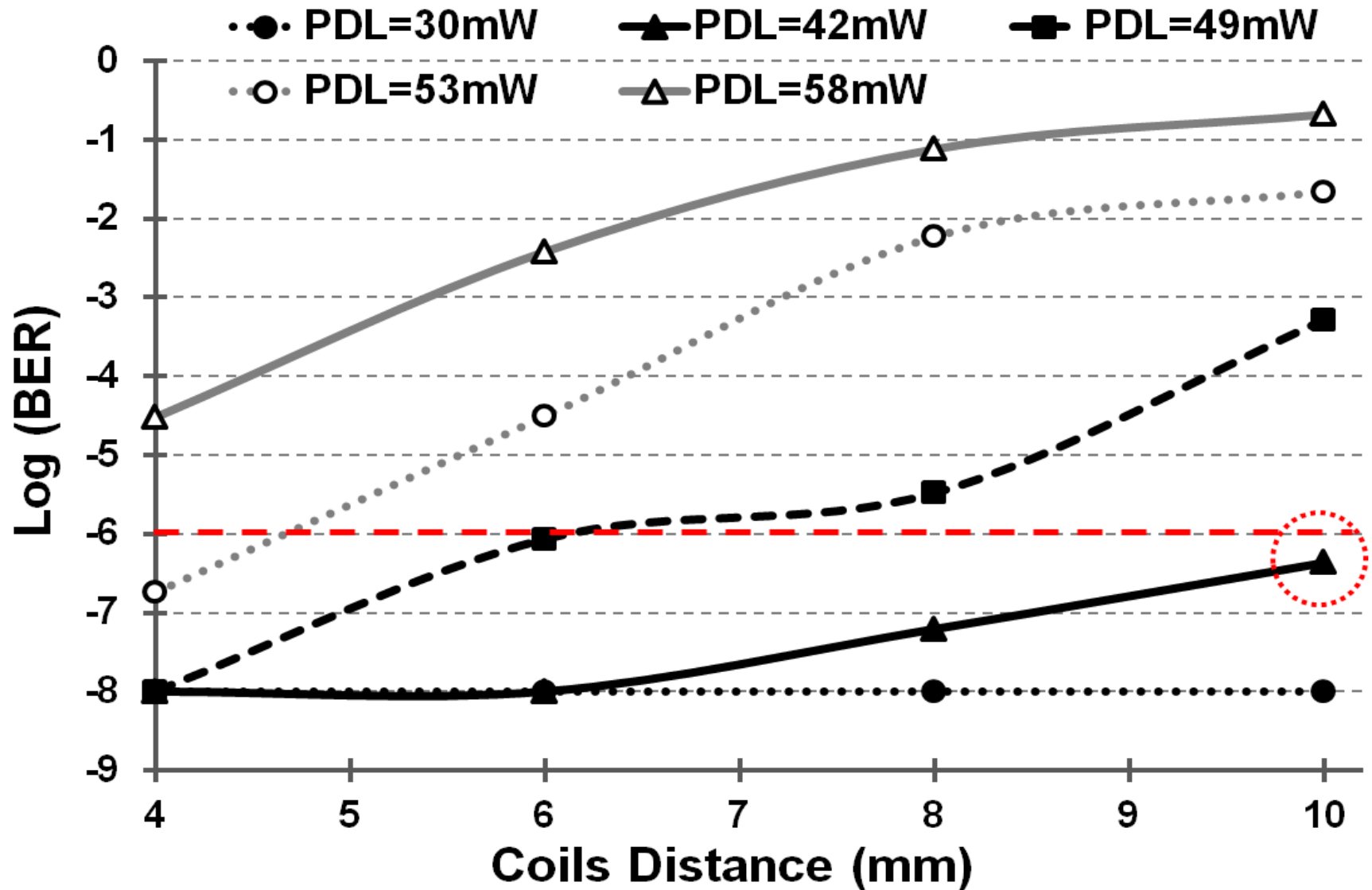

PDM Benchmarking

- **PDM advantages:**
 - Low-power consumption of data transceiver
 - Robustness against power carrier interference
 - First inductively-powered pulse-based transceiver

Reference	Mod.	d (mm)	Data Carrier (MHz)	Power Carrier (MHz)	Data Rate (Mbps)	Tx/Rx Power (pJ/bit)	CMOS Tech. (μm)	SIR (dB)	Die Area (mm^2) (Data Tx/Rx)	V_{DD} (V)	BER
Ghovanloo, 2004	pcFSK	5	5/10	5/10	2.5	-/152	1.5	-	-/0.29	5	10^{-5}
Hu, 2005	BPSK	15	10	10	1.12	-/625	0.18	-	-/0.2	1.8	10^{-5}
Mandal, 2008	LSK ⁺⁺	20	25	25	2.8	35.7/1250	0.5	-	2.2/2.2 ^{**}	2.8	10^{-6}
Rush, 2012	FSK	20	-/5	5	1.25	-	0.8	-	-	2.7	-
Rush, 2012	BPSK	20	48	5	3	1962/-	0.8	-	2.3 ^{**}	2.7	2×10^{-4}
Simard, 2010	QPSK	5	13.56	1	4.16	-	-	-	-	-	2×10^{-6}
Zhou, 2008	BPSK	15	20	2	2	-/3100	0.35	-12 [*]	-/4.4	4.5	10^{-7}
Chen, 2013 ⁺	DPSK	-	20	2	2	-	0.18	-	-	1.8	10^{-7}
This Work	PDM	10	50	13.56	13.56	960/162	0.35	-18.5	0.34/0.37	1.8	4.3×10^{-7}

* A 1st-order off-chip filter was used to improve SIR to -6 dB. ** Including pads.

⁺ Second-order filter was used to improve SIR. ⁺⁺ LSK is only used for uplink.

Conclusions

- Various wireless power and data transfer techniques can be utilized to **power up and communicate with IMDs**.
- The **wireless power transfer** consists of several stages, such as the power Tx, inductive link, matching circuit, power conversion and management units.
- Every stage offers the designer with several degrees of freedom and design parameters, which need to be **optimally combined by considering designated specifications**.
- **Low-power wireless data telemetry** with simultaneous power interference are important in **information-heavy IMDs**, in which high performance is desired despite limited received power.

GT- Bionics Lab Members



Acknowledgements

- Funding provided by:

- National Science Foundation
- National Institutes of Health
- Army Research Office (ARO)
- ON Semiconductor



National Institutes
of Health

- Collaborators:

- Dr. Ravi Bellamkonda, Georgia Tech, Atlanta, GA
- Dr. Ann Laumann, Northwestern University, Chicago, IL
- Dr. Joseph Manns, Emory University, Atlanta, GA
- Dr. Elliot Roth, Rehab. Institute of Chicago, Chicago, IL
- Dr. Donald Rainnie, Emory University, Atlanta, GA
- Dr. Wen Li, Michigan State University, Lansing, MI
- Dr. Kimberly Wilson, University of Western Georgia, Carrollton, GA
- Dr. Rupal Patel, Northeastern University, Boston, MA
- Dr. Alan Sokoloff, Emory University, Atlanta, GA

