

# Sub-Sampling PLL Techniques

**Xiang Gao, Eric Klumperink\***  
**Bram Nauta\***

**Marvell, Santa Clara, CA**

**\*University of Twente, Enschede, The Netherlands**

# Outline


---

- **Classical CP PLL and PLL FOM**
- **Sub-Sampling(SS) PLL**
- **SSPLL Power Reduction Techniques**
- **SSPLL Spur Reduction Techniques**
- **Recent SSPLL Development and Discussion**


# The Need For High Performance PLL
 
## ■ Low noise/jitter/power PLL applications

- Radio transceivers
- Wireline and optical data links
- Analog to Digital converters




# Classical PLL And Noise

 

- Loop noise low pass filtered, dominant in-band
- VCO noise high pass filtered, dominates out-band
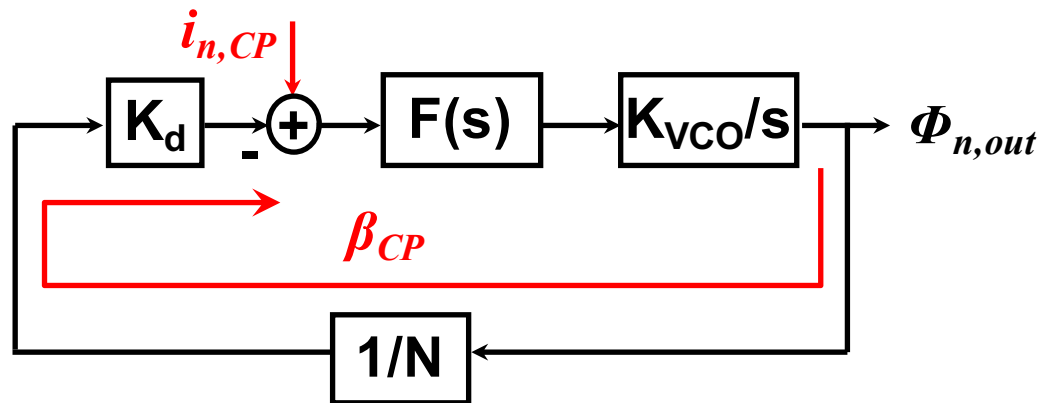
# CP Noise

- PD/CP usually major loop noise source in classical PLL





- Define CP feedback gain as:  $\beta_{CP} = \frac{\Delta I_{out}}{\Delta \phi_{out}}$
- Inside bandwidth, loop gain is large


$$\mathcal{L}_{CP,in-band} \approx \frac{S_{iCP,n}}{2\beta_{CP}^2}$$

**CP noise suppressed by  $(\beta_{CP})^2$ , Large  $\beta_{CP}$  desired**

# Classical 3-state PFD/CP PLL

 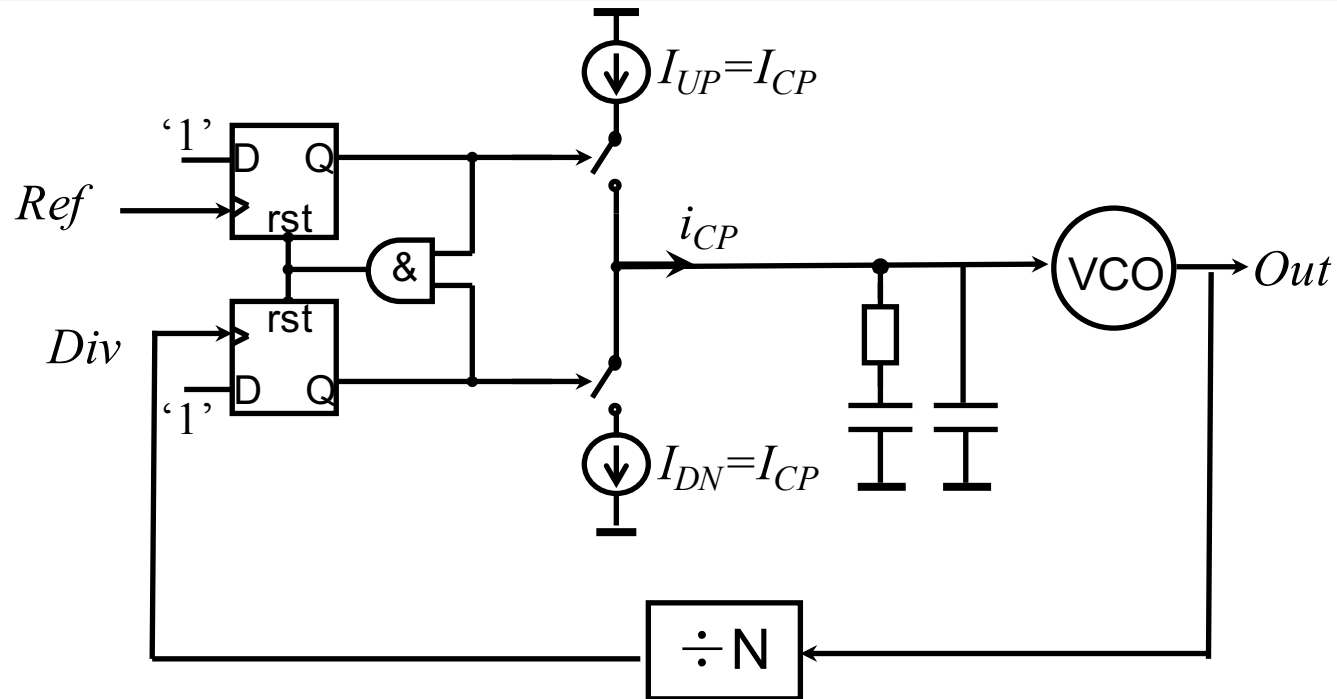

# Classical CP Feedback Gain

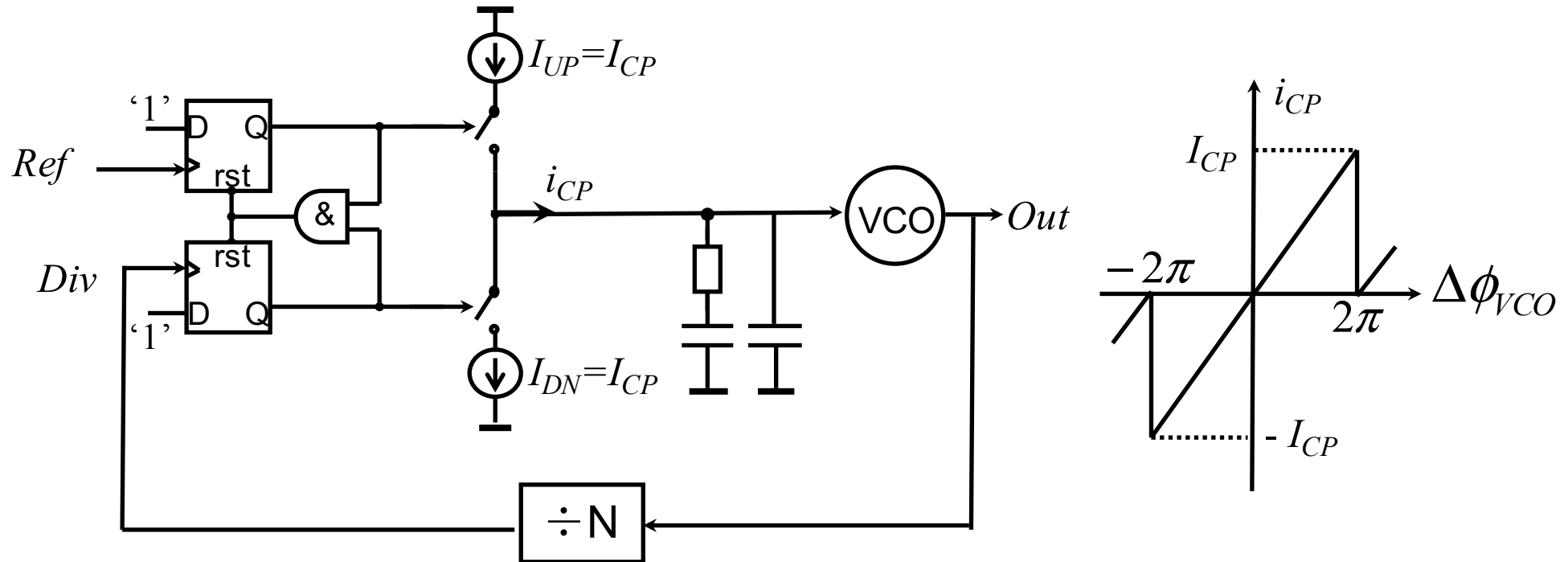

■ CP feedback gain  $\beta_{CP,3state} = \frac{1}{N} \times \frac{I_{CP}}{2\pi}$

-  $\beta_{CP}$  reduced by  $N$ , thus CP noise amplified by  $N^2$

# Figure of Merit (FOM)

---

- **Figure of Merit (FOM) useful in comparing relative merits and helping designers to approach fundamental limits**
- **Widely used VCO FOM takes into account fundamental tradeoff between various parameters**

$$\text{FOM}_{\text{VCO}} = 10 \log \mathfrak{L}(f_m) + 10 \log \left( \frac{f_m^2}{f_{\text{VCO}}^2} \frac{P_{\text{VCO}}}{1 \text{mW}} \right)$$

- **PLL performance involves more parameters:  $f_{\text{ref}}$ ,  $f_{\text{out}}$ , loop bandwidth, in-band/out-band noise, jitter, power...**



# PLL Loop FOM

---

■ Assuming all the fundamentally required power for loop component (PD/CP, divider, ref buffer) is dynamic and neglecting  $1/f$  noise, [1] showed that:

$$\mathcal{L}_{loop,in-band} \propto N^2 \cdot f_{ref} \cdot \frac{f_{ref}}{P_{loop}} = \frac{f_{out}^2}{P_{loop}}$$

■ A FOM for PLL loop design is thus defined as:

$$FOM_{loop} = 10 \log \mathcal{L}_{loop,in-band} + 10 \log \left[ \left( \frac{1\text{Hz}}{f_{out}} \right)^2 \cdot \frac{P_{loop}}{1\text{mW}} \right]$$

- Independent on  $f_{ref}$ : larger  $f_{ref}$  reduces loop noise but also increases dynamic power

# PLL FOM

---

■ In optimized PLL, Loop/VCO contributes equally to both jitter and power, the minimum achievable jitter is [1]:

$$\sigma_{t,PLL,\min}^2 = \frac{1}{(1\text{Hz})^2} \cdot \frac{1\text{mW}}{P_{PLL}} \cdot \frac{1}{\pi} \cdot 10^{\frac{FOM_{loop} + FOM_{VCO}}{20}}$$

■ A PLL FOM is thus defined as:


$$FOM_{PLL} = 10 \log \left[ \left( \frac{\sigma_{t,PLL}}{1\text{s}} \right)^2 \cdot \frac{P_{PLL}}{1\text{mW}} \right].$$

- or: 
$$FOM_{PLL} = \frac{FOM_{loop} + FOM_{VCO}}{2} + 10 \log \frac{1}{\pi}.$$

- Design quality (FOM) of the loop and VCO are equally important in achieving good PLL FOM
 
# State-of-Art PLLs

■ This PLL FOM has been widely adopted recently. The FOM generally improves over the years. The SSPLLs currently hold best FOM for both int-N and frac-N PLLs.




# Outline

---

- Classical CP PLL and PLL FOM
- **Sub-Sampling(SS) PLL**
- SSPLL Power Reduction Techniques
- SSPLL Spur Reduction Techniques
- Recent SSPLL Development and Discussion

# Sub-Sampling Phase Detector (SSPD)


## ■ Sub-Sampling PD for Integer-N PLL

 

- VCO sub-sampled by Ref without going through divider
- Phase/Timing error converted into voltage error
- High phase detection gain due to high VCO  $dv/dt$

[2] X. Gao, E. Klumperink, M. Bohsali and B. Nauta, "A Low Noise Sub-Sampling PLL in Which Divider Noise is Eliminated and PD/CP Noise is not Multiplied by  $N^2$ ," *IEEE J. Solid-State Circuits*, vol. 44, no.12, pp. 3253-3263, Dec. 2009.

# Sub-Sampling PD/CP (SSPD/CP)

 

- Voltage controlled CP


- Ideal characteristic

■ Detection characteristic is fairly linear once in lock

$$\beta_{CP} = K_d = \frac{\Delta I_{out}}{\Delta\phi_{VCO}} = \frac{g_m \cdot A_{VCO} \sin(\Delta\phi_{VCO})}{\Delta\phi_{VCO}} \approx g_m A_{VCO}$$

**There is no N factor !**


# SSPLL And Modeling

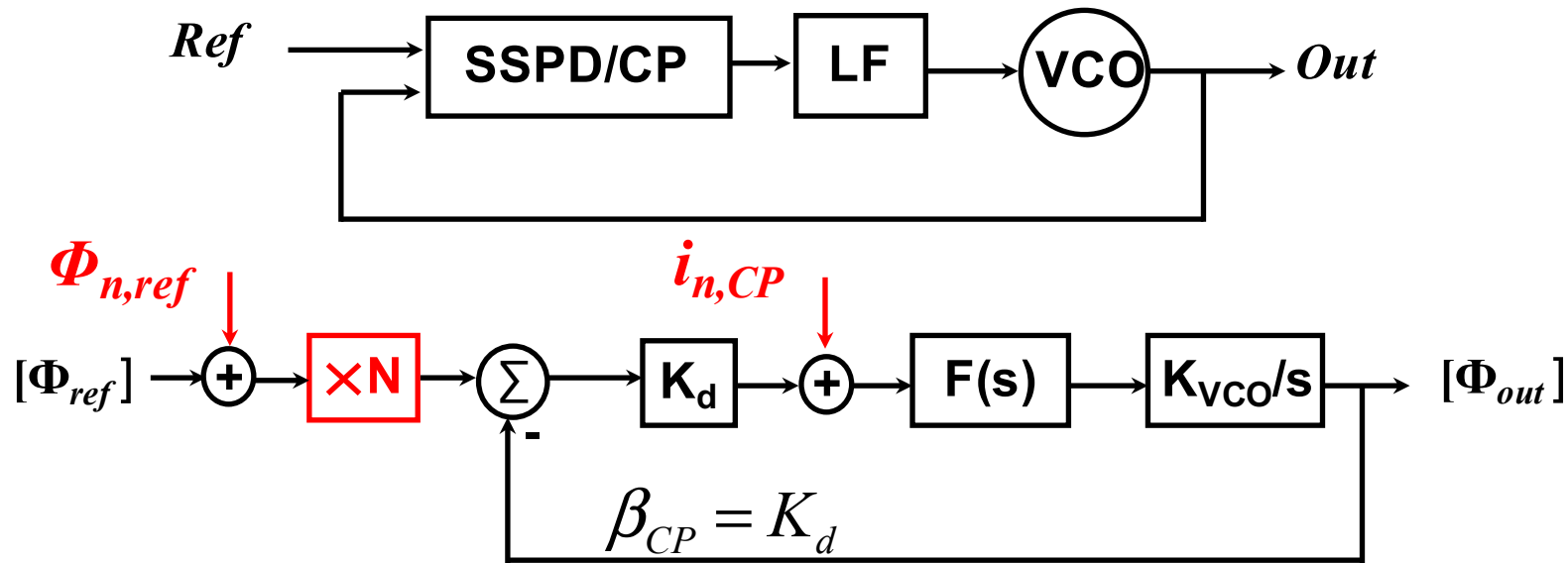
 
## ■ No Divider but a virtual Multiplier

- Sub-sampling process

$$f_{alias} = f_{VCO} - N \cdot f_{ref}$$




- Ref noise multiplied by N, same as in classical PLL

**CP noise *NOT* multiplied by N !!**
 
# N Factor On CP Noise: Another Angle

■ PLL is a loop back transceiver: VCO transmits 'signal' (VCO noise), the Loop receive/process it and feed it back to cancel/suppress the VCO noise



■ Classical PLL is analogous to a superheterodyne receiver


- Divider: 1<sup>st</sup> down-converter, to low IF
- PFD: 2<sup>nd</sup> down-converter, to DC
- CP/LPF: Base Band (TIA/LPF)

■ Divider as down-converter has  $1/N$  attenuation and  $20\log N$  noise figure, PFD/CP noise thus amplified by  $N^2$



# Why no N Factor In SSPLL

---

 

- SSPLL is analogous to a direct conversion receiver
- SSPD down-converter has no attenuation but a gain of 1, thus better NF and no amplification for PD/CP noise

# SSPLL VS Classical PLL

---

- SSPLL ideally has no divider noise
- SSPLL CP noise greatly suppressed by large  $\beta_{CP}$ 
  - Comparing  $\beta_{CP}$  with 3-state PFD/CP assuming same  $I_{CP}$

$$\frac{\beta_{CP,SSPD}}{\beta_{CP,3state}} = 4\pi \cdot N \cdot \frac{A_{VCO}}{2I_{CP} / g_m} = 4\pi \cdot N \cdot \frac{A_{VCO}}{V_{gs,eff}} \gg 1$$

$$\text{e.g.} \quad = 4\pi \times 40 \times \frac{0.4V}{0.2V} \approx 1000$$

**SSPLL has much larger  $\beta_{CP}$ , thus more CP noise suppression**

# SSPD Noise

---

## ■ In-band Phase Noise due to SSPD

$$L_{in-band,SSPD} = \frac{kT}{C_{sam} \cdot f_{ref} \cdot A_{VCO}^2}$$


$$\text{e.g.} = \frac{4 \times 10^{-21}}{10f \times 40M \times 0.4^2} \approx -132dBc/Hz$$

**$C_{sam}$  as small as 10fF enough for very low phase noise**
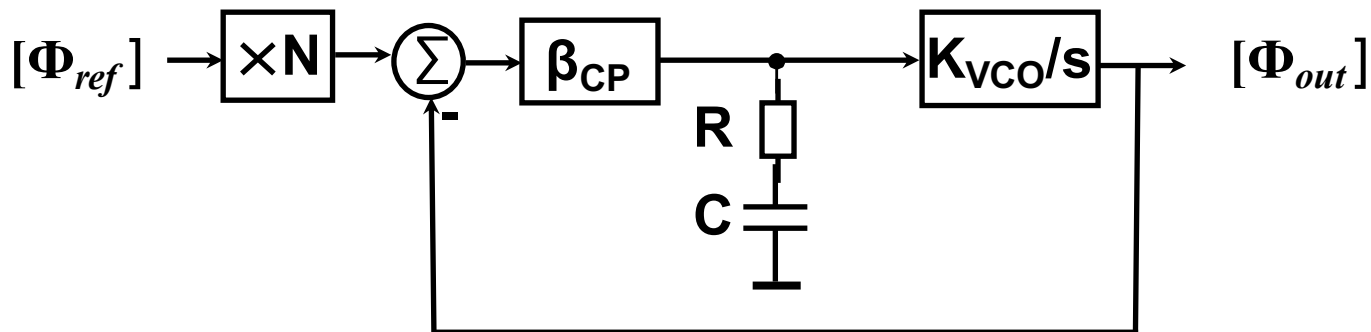
# SSPLL Design Challenges


---

- SSPLL has no divider
  - May lock to any integer N
- SSPD/CP has very Large  $\beta_{CP}$ 
  - May need Big Cap for stabilization



- For given phase margin and  $K_{VCO}$ : 
$$C \propto \frac{\beta_{CP}}{f_c^2}$$


# $\beta_{CP}$ and Filter Cap Area

 

- Once CP noise is negligible, further Larger  $\beta_{CP}$  only wastes chip area (Big Cap)

$\beta_{CP}$  control is desired for full integration


# SSPD/CP with Gain Control

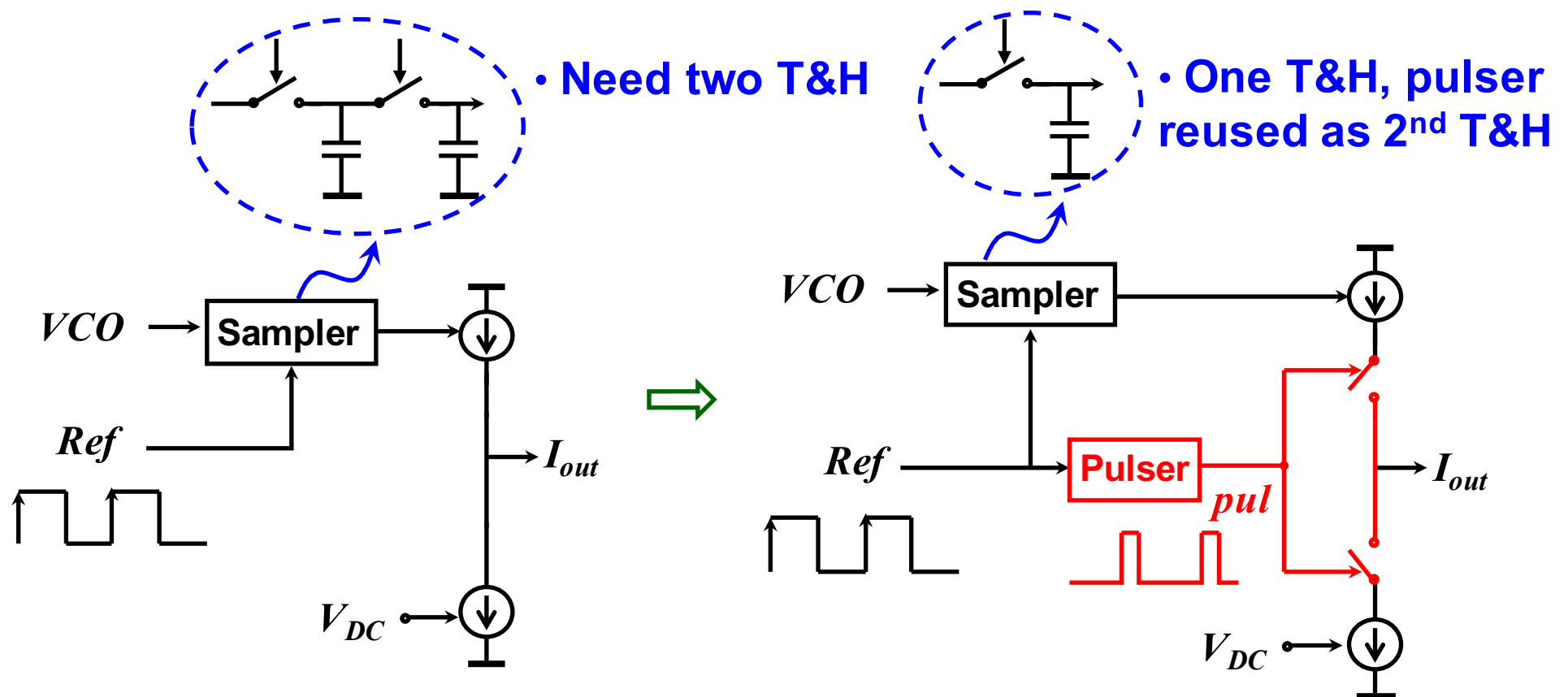


$$\beta_{CP} = A_{VCO} \cdot g_m \cdot DR_{pul}$$

**A proper choice of  $DR_{pul}$  reduces Cap area while still keeps CP noise negligible**


# Differential Sampling

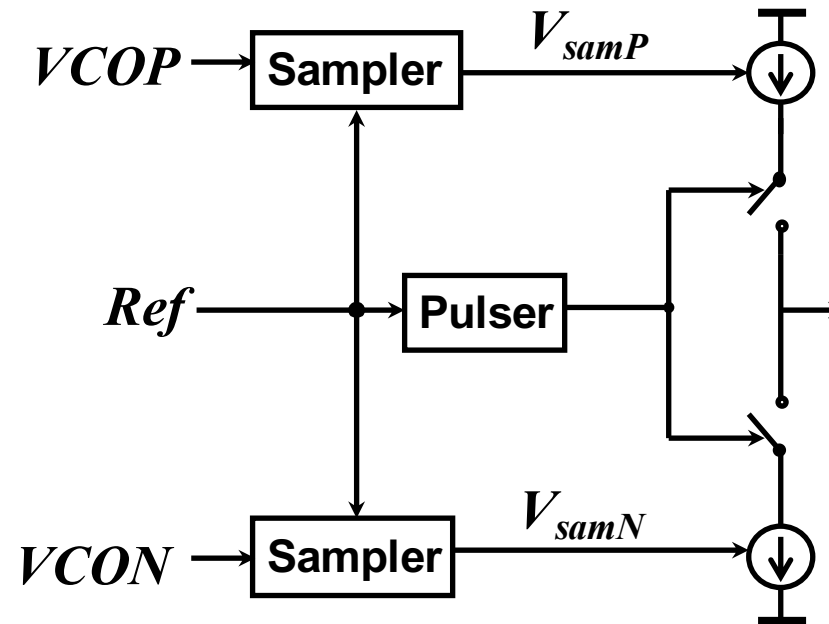

 - Cancels clock feed-through & charge injection
- VCO crossing (most linear point) is locking point




# SSPLL With Frequency Locking Loop

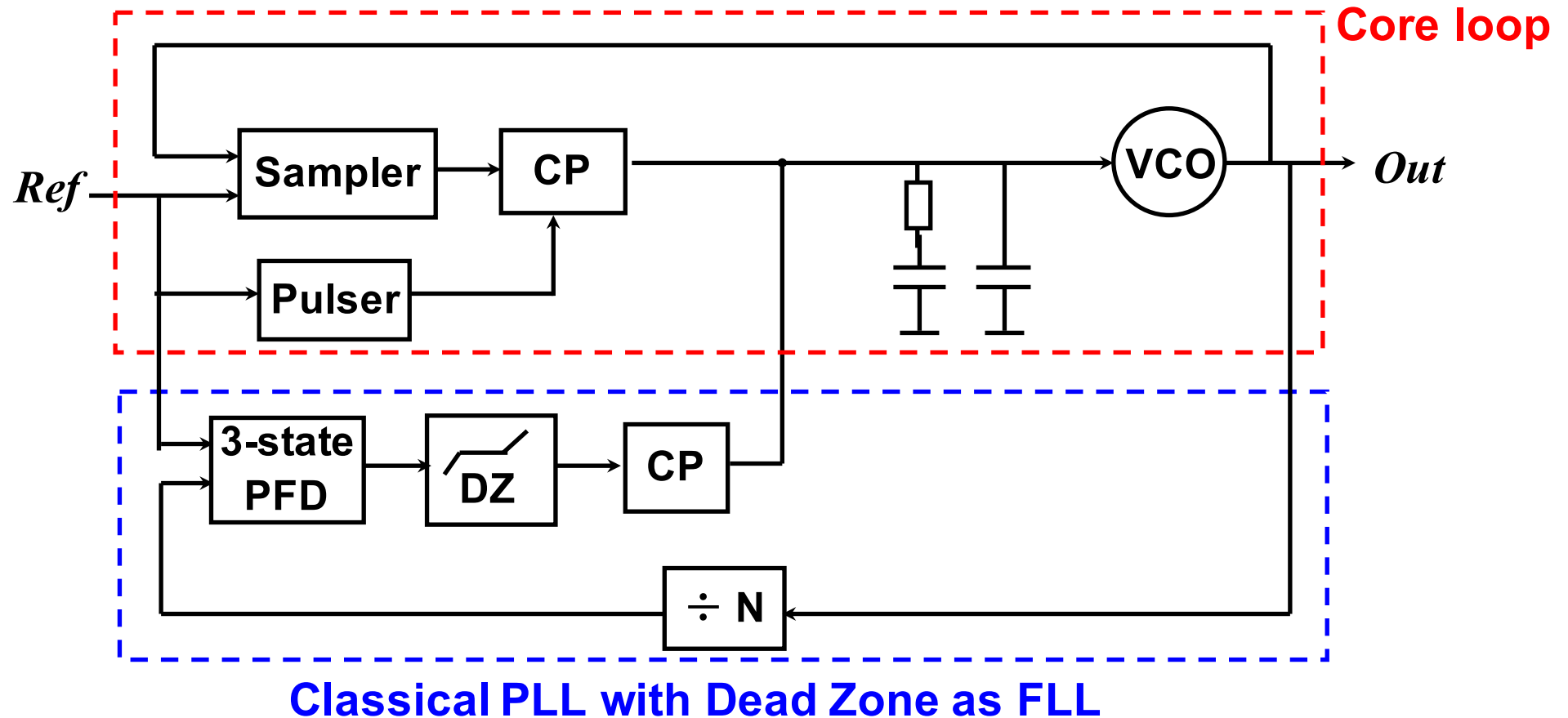

- During locking,  $\Delta\Phi > DZ$ , FLL has large gain, brings loop to lock
- Close to locking,  $\Delta\Phi < DZ$ , FLL has zero gain, not injecting noise
- FLL can also be disabled after locking to save power




# Dead Zone Creator Example

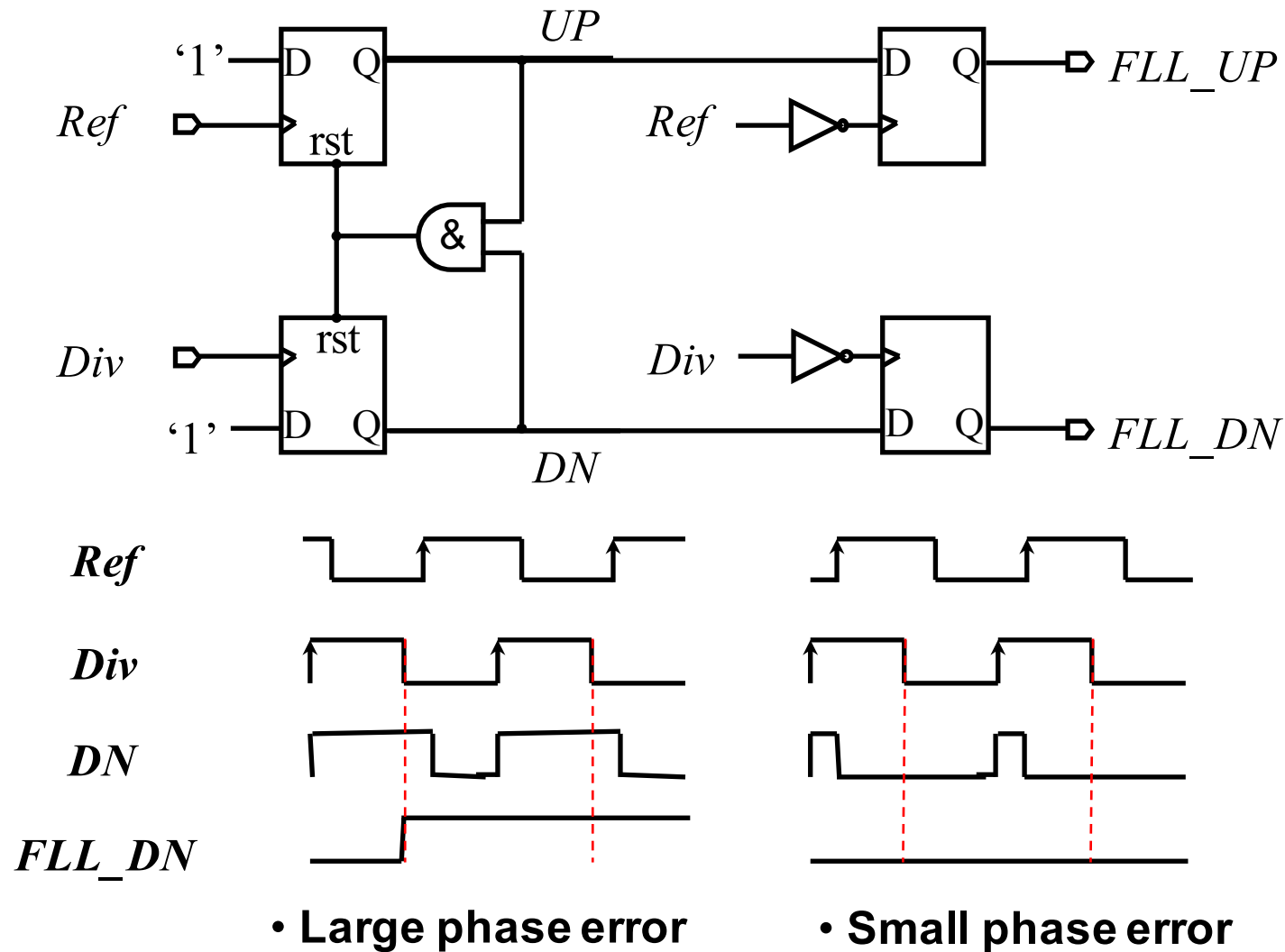

■ With 50% *Ref* and *Div* duty ratio, Dead zone is  $(-\pi, +\pi)$

# It Also Works Without Dead Zone

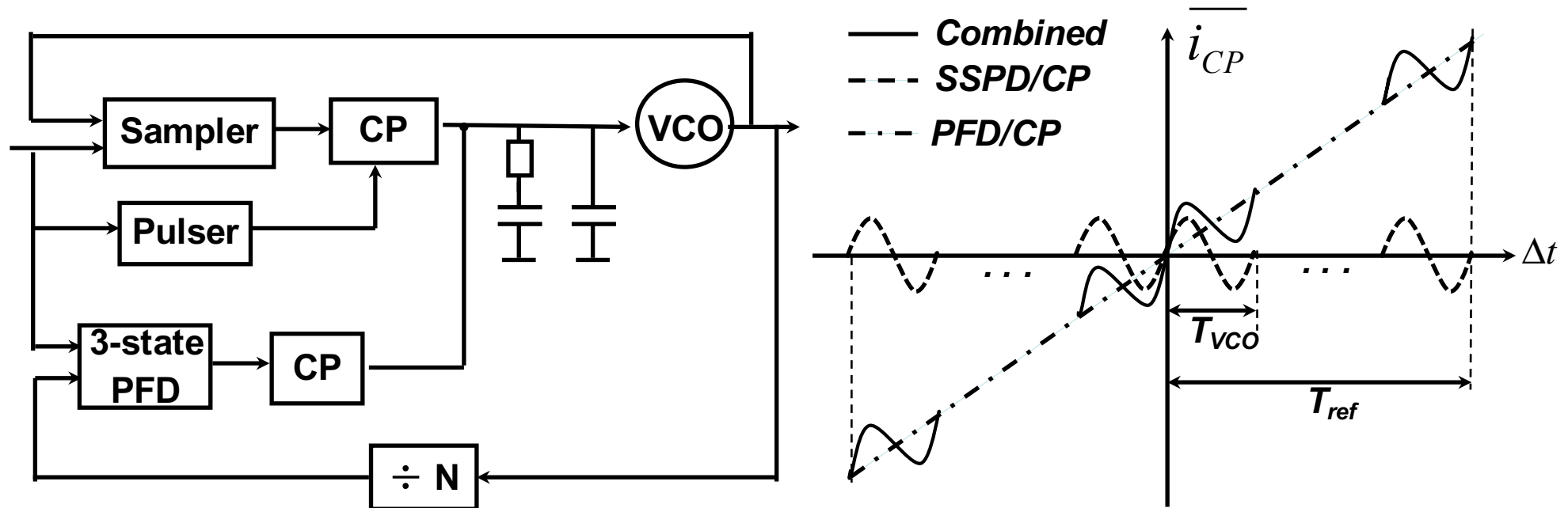

- FLL keeps running, more robust against disturbances
- Overall characteristic SSPD/CP and PFD/CP combined
- FLL PFD/CP injects noise but is attenuated by  $(\beta_{CP,SS} + \beta_{CP,PFD})^2$

[3] C.-W. Hsu, K. Tripurari, S.-A. Yu and P. R. Kinget, "A Sub-Sampling-Assisted Phase-Frequency Detector for Low-Noise PLLs With Robust Operation Under Supply Interference," IEEE Trans. Circuits Syst. I, vol.62, no.1, pp.90-99, Jan. 2015.


# Outline

---

- Classical CP PLL and PLL FOM
- Sub-Sampling(SS) PLL
- **SSPLL Power Reduction Techniques**
- SSPLL Spur Reduction Techniques
- Recent SSPLL Development and Discussion
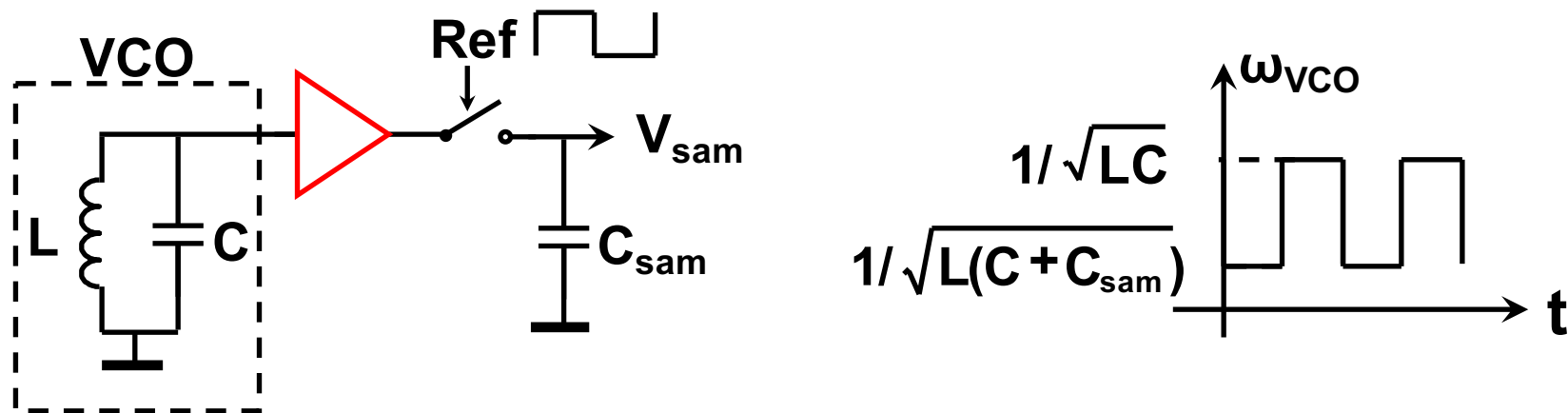
# VCO-Sampler Buffer

- VCO buffer is power consuming, can we remove it?





- VCO load and  $f_{VCO}$  changes, BFSK effect causes spur

$$SP = 20 \log \left[ \sin(\pi \cdot D_{ref}) \cdot \frac{N}{2\pi} \cdot \frac{C_{sam}}{C} \right]$$

# Direct Sampling with Dummy Sampler

  
## ■ Complementary switched dummy sampler



## - Spur due to BFSK effect with mismatch


$$SP = 20 \log \left[ \sin(\pi \cdot D_{ref}) \cdot \frac{N}{2\pi} \cdot \frac{A_C \sqrt{2C_{sam}}}{C} \right]$$

# Direct VCO Sampling Design Example

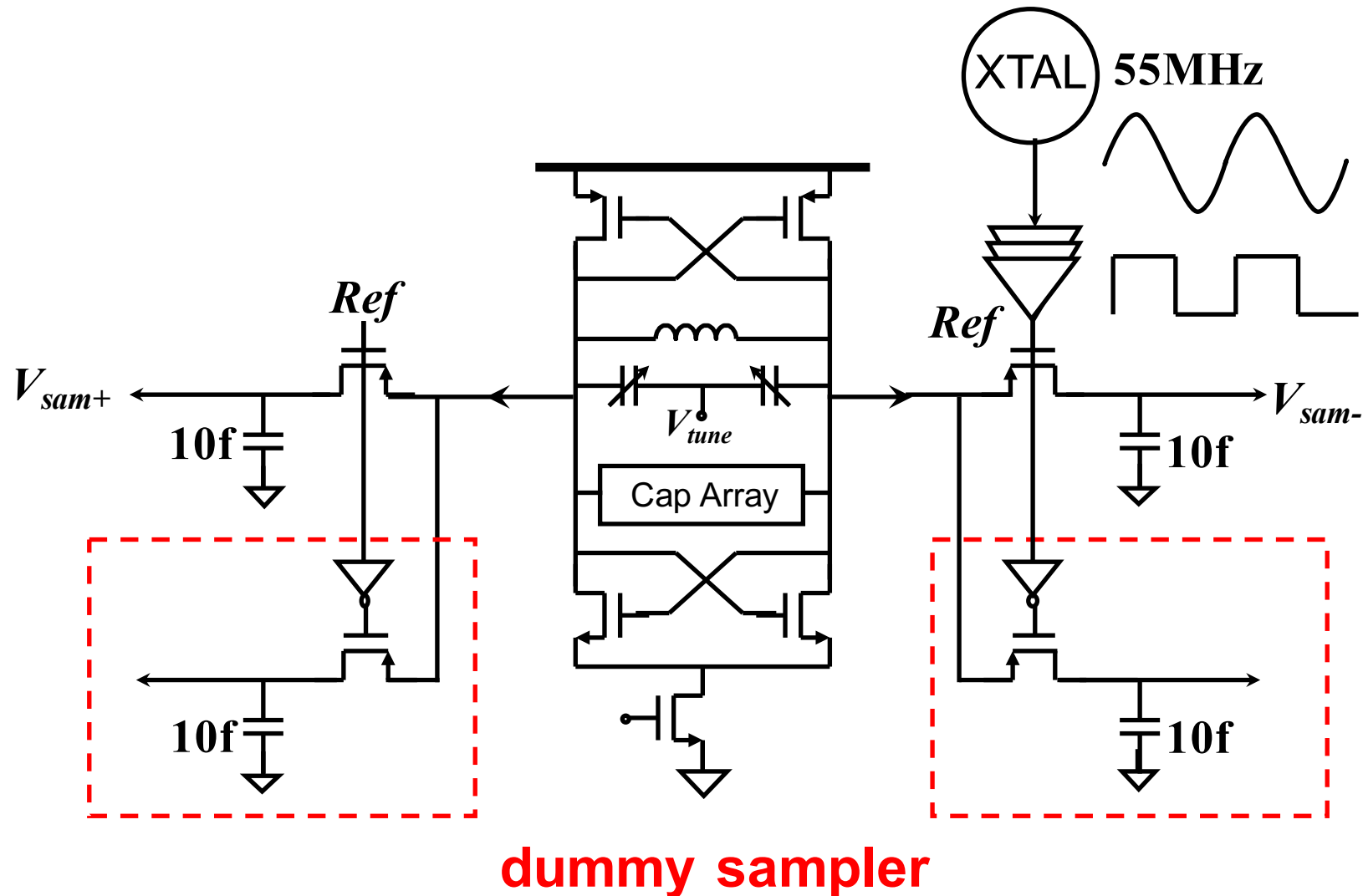


[4] X. Gao, E. Klumperink, G. Socci, M. Bohsali and B. Nauta, "A 2.2GHz Sub-Sampling PLL with 0.16ps<sub>rms</sub> Jitter and -125dBc/Hz In-band Phase Noise at 700μW Loop-Components Power," *IEEE Symposium on VLSI Circuits*, pp. 139-140, Jun. 2010.

# CP Design

 

dummy CP

 


$V \rightarrow I$

- Due to superior CP noise suppression of SSPLL, a small  $I_{CP}$  of  $30\mu A$  is enough to achieve very low phase noise
 
# Inverter Ref Buffer

- XTAL outputs sine-wave, SSPD needs square-wave Ref




- Big size for low Ref noise
  - Slow sine-wave input, N1 and P1 both on for long time
  - Short-circuit current could be  $>90\%$  of inverter power
- With so little  $I_{CP}$  and SSPD virtually consume no power, simple Ref buffer become major loop power dissipater



# How to Reduce Short-Circuit Current?


---

## ■ Practical sampler: track-and-hold

 

- Only the sampling edge (SE) is critical for noise
- The tracking edge (TE) can be noisy


# Low Power Sine-to-Square Ref Buffer

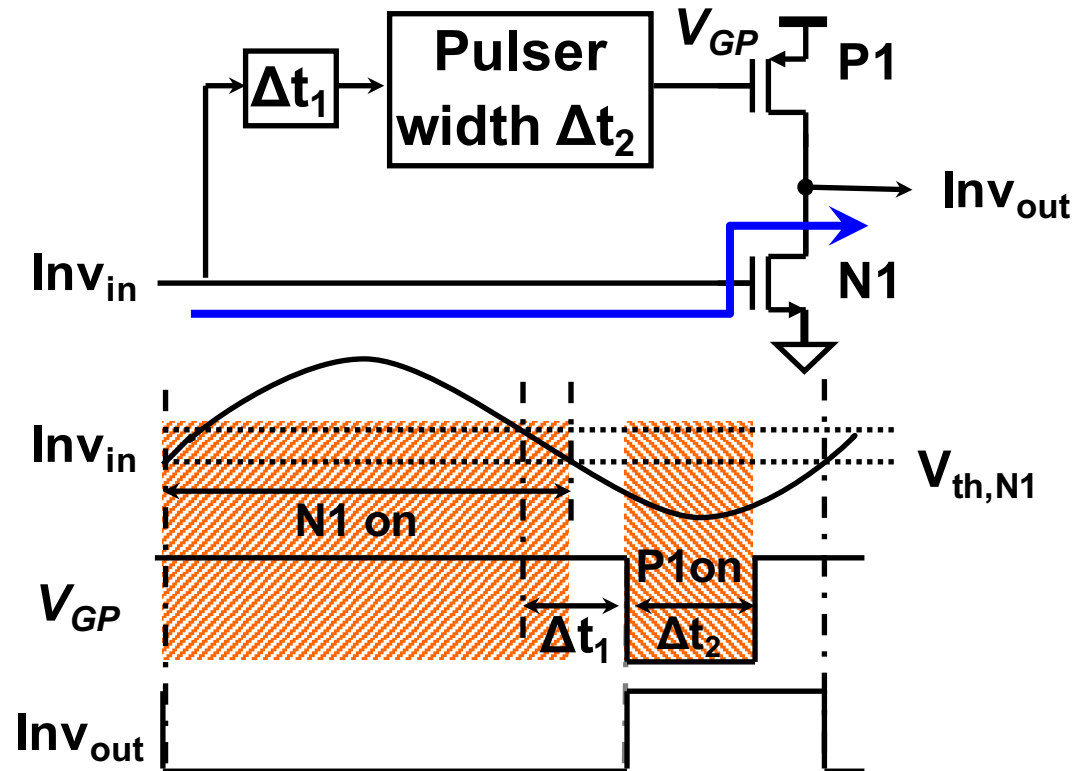

- N1 and P1 on-time guaranteed non-overlapping
- Critical path for **SE** is kept clean and short


**Short-circuit current eliminated**

# Low Power Ref Buffer Design Example

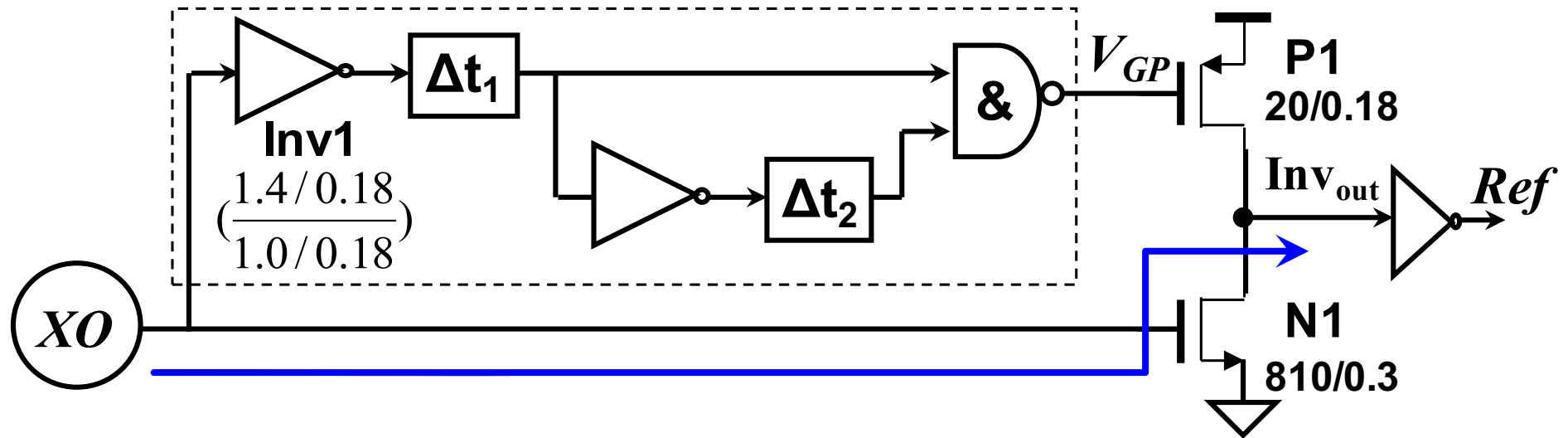


- Delays are implemented with shunt-C inverters
- Transistors in critical path are sized big, others are small to save power
- It draws 0.22mA (would be >2mA for simple inverter)

# Die Photograph

 

- 0.18 μm CMOS
- Active Area: 0.2 mm<sup>2</sup>
- 24-pin LLP package
- VDD: 1.8 V
- Power Consumption
  - VCO 1.0 mA
  - Loop 0.4 mA

# Measured Phase Noise

 


- 2.2GHz output with 55MHz XTAL
- In band noise -125.3dBc/Hz@200kHz
- Rms jitter 0.16ps [10k, 100M]
 
# Measured Spur


---

- Spur from 20 chips from spectrum analyzer


 
# PLL Utopia

- All PLL need Ref buffer. “PLL Utopia”: only the Ref path contributes to loop noise and power.
- Both SSPLL and injection locked PLL can approach “Utopia” and they hold the PLL FOM record



# SSPLL vs ILPLL

---

- **SSPLL is more like a traditional PLL with a phase detector and a feedback loop**
  - **More robust bandwidth/loop-dynamic control**
  - **Lower reference spur**
- **ILPLL can achieve larger filtering bandwidth for VCO noise and can be beneficial e.g. when ring oscillator is used**




# Outline

---


- Classical CP PLL and PLL FOM
- Sub-Sampling(SS) PLL
- SSPLL Power Reduction Techniques
- **SSPLL Spur Reduction Techniques**
- Recent SSPLL Development and Discussion

# Classical CP

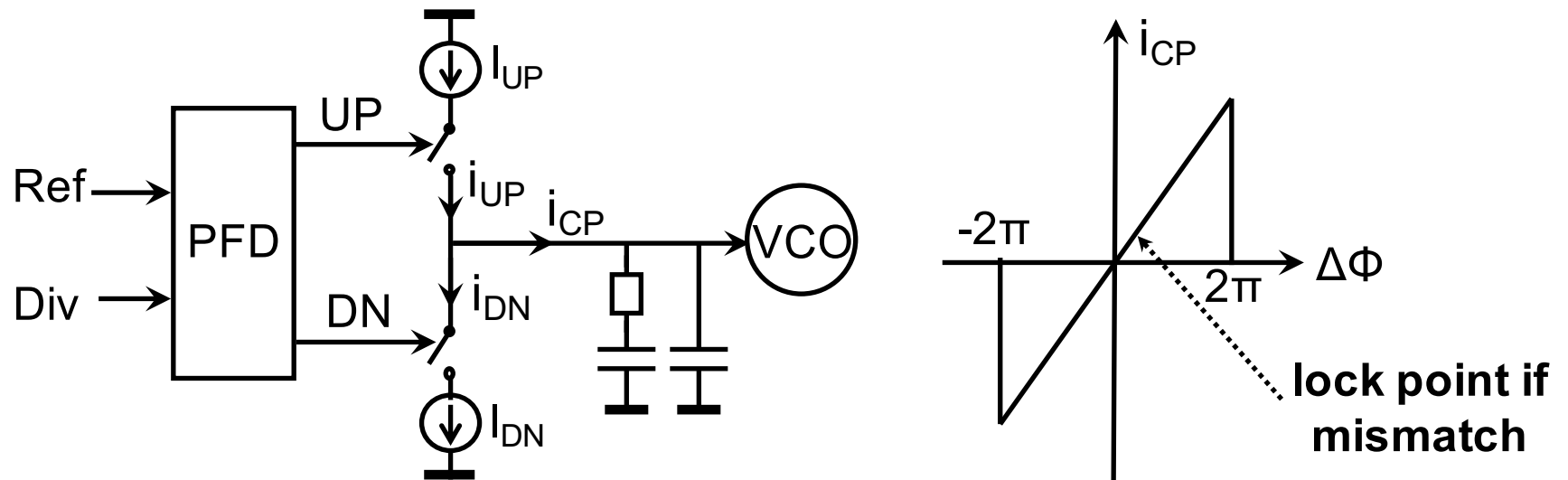
 
## ■ UP/DN constant amplitude, variable on-time

- Amplitude mismatch  $\rightarrow$  UP or DN on-time mismatch  $\rightarrow$  CP ripple




## ■ VCO Ref spur by CP ripple $\propto i_{CP, \text{fref}} \cdot \left(\frac{f_{BW}}{f_{\text{ref}}}\right)^2$

**Sensitive to mismatch, low spur high BW tradeoff**


# Classical Low Ripple CP Design

---

 

- Cascode transistors for high impedance, better matching
- Current steering, UGB for  $V_{dump}=V_{LF}$  to keep node voltages

# CP in SSPLL

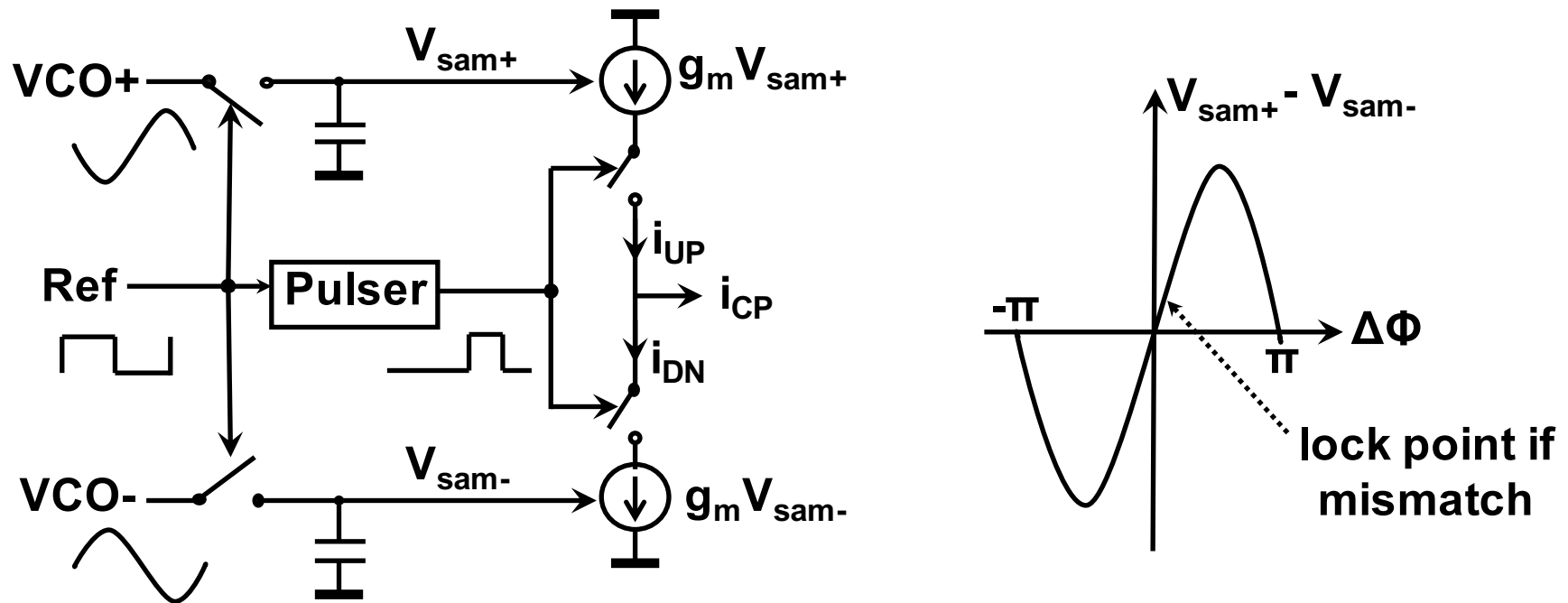

- Pulser is 2nd T&H and controls CP gain


■ UP/DN constant on-time, variable amplitude

- Amplitude mismatch → UP/DN still same on-time → no ripple




**UP/DN amplitude mismatch eliminated**

# Simple Low Ripple CP Design

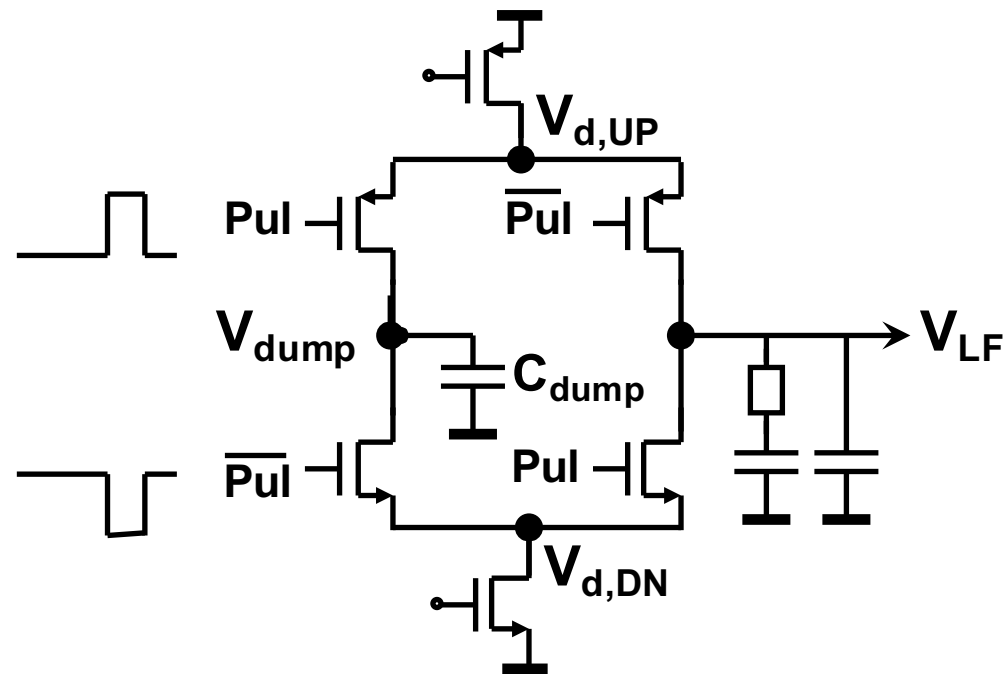

- No amplitude mismatch, single transistor enough
  - Achieves  $V_{\text{dump}} = V_{\text{LF}}$  without using UGB
    - Steer to filter:  $I_{\text{UP}} = I_{\text{DN}}$  at  $V_{\text{d,UP}} = V_{\text{d,DN}} = V_{\text{LF}}$
    - Steer to  $C_{\text{dump}}$ :  $I_{\text{UP}} = I_{\text{DN}}$  at  $V_{\text{d,UP}} = V_{\text{d,DN}} = V_{\text{dump}}$
- ⇒ Due to finite output impedance,  $V_{\text{dump}} = V_{\text{LF}}$

# SSPD Also Induces Spur

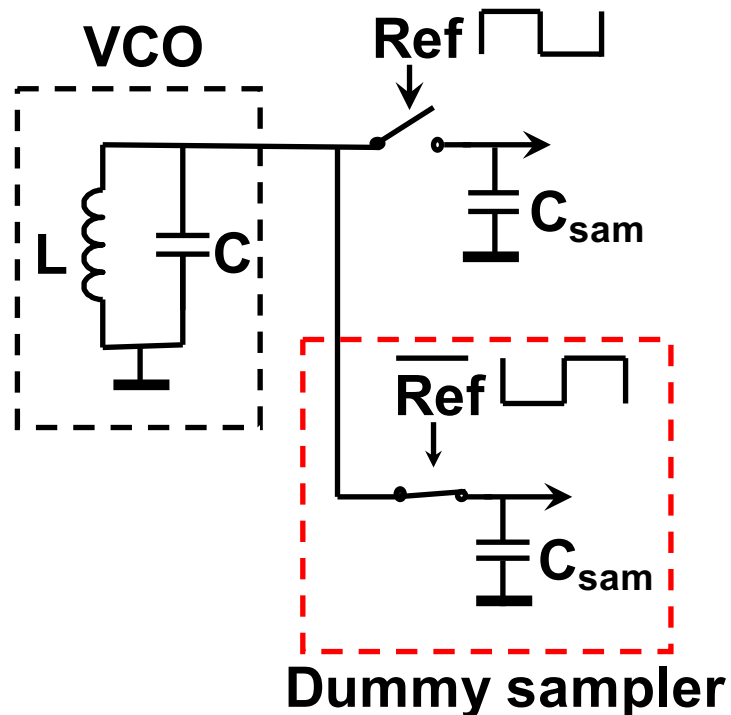


**compensated**


1. VCO load and  $f_{VCO}$  changes, BFSK
2. Charge injection from switch to VCO
3. Charge Sharing between  $C_{sam}$  and VCO

- All spur mechanisms doesn't go through loop filtering, so no spur/BW tradeoff
- Complementary sampling helps but not enough

# VCO/Csam Charge Sharing

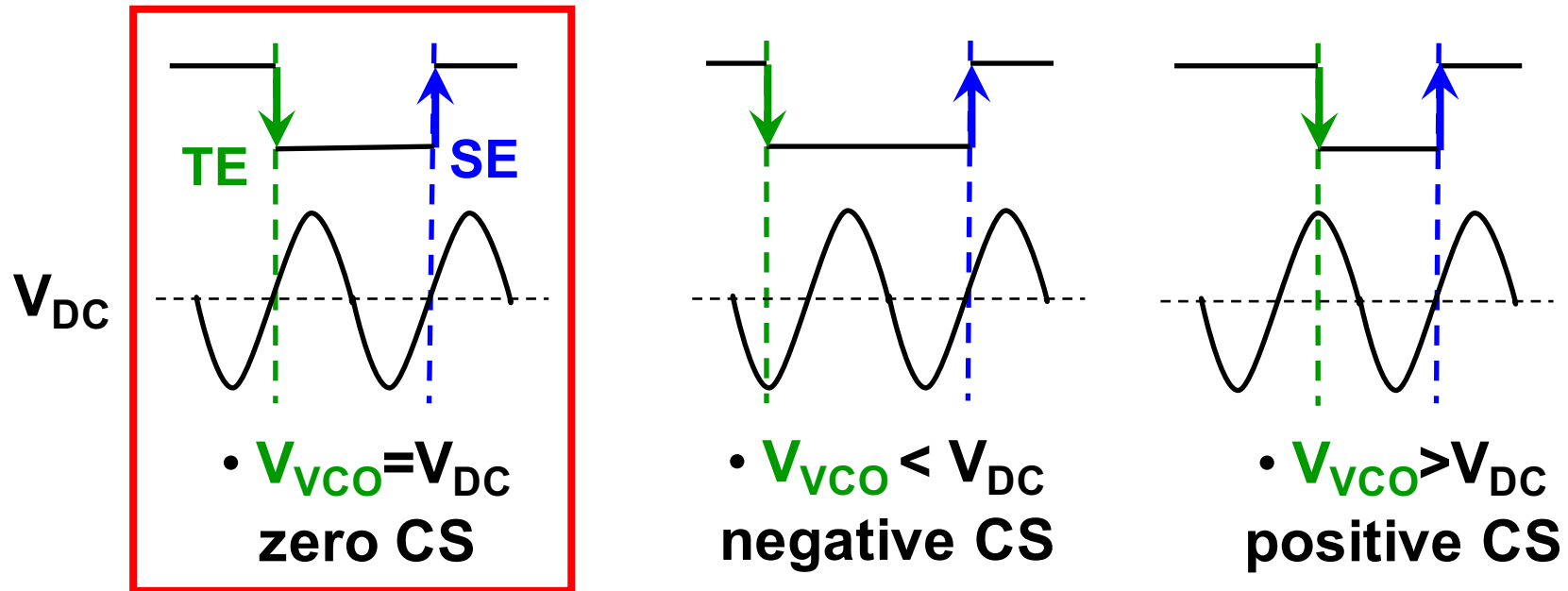

 ■  $\Delta q$  depends on Tracking Edge (TE) timing, has sign




No charge sharing by aligning TE to VCO zero-crossing

# Align Ref TE and VCO

## ■ Phase detector for Ref TE

- Use dummy sampler as it samples VCO with Ref TE


## ■ Ref TE tuning scheme

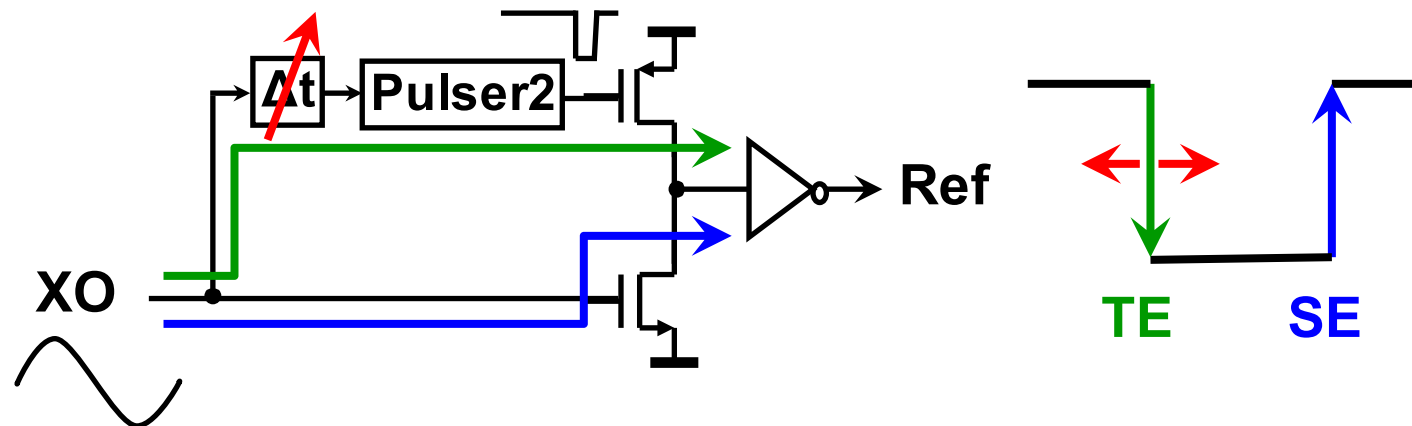

- Separate gate control for TE/SE
- Critical SE path kept short and un-affected
- No short circuit current if N/PMOS on time non-overlap




# Low Spur SSPLL Architecture

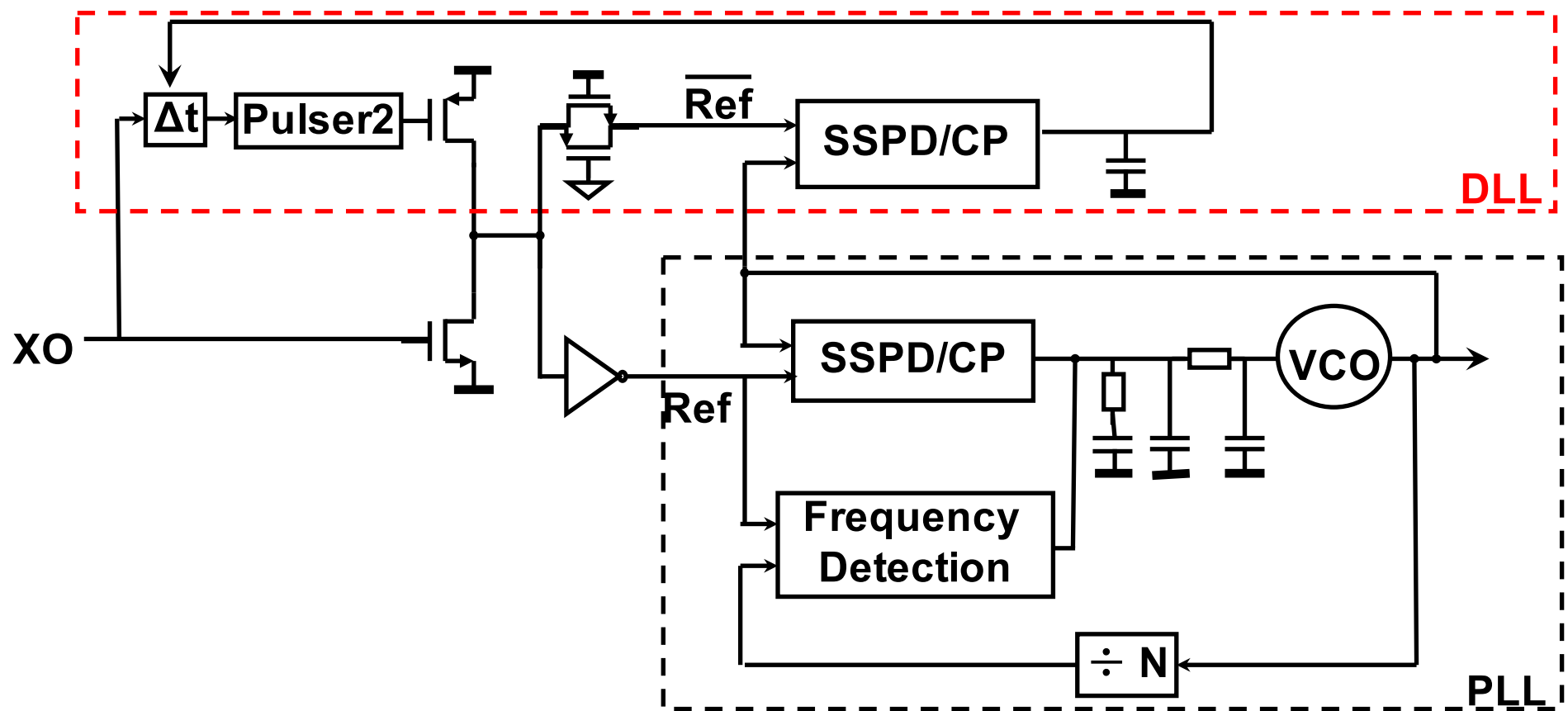

- 1. BFSK
  - 2. Charge injection
  - 3. Charge sharing
- compensated by dummy
- minimized by DLL tuning

■ VCO buffer can be used for even lower spur (power penalty)

# Die Photograph

 


- 0.18um CMOS
- Active Area: 0.2mm<sup>2</sup>
- 24-pin LLP package
- VDD: 1.8V
- Power Consumption
  - Whole PLL 2.1mA
  - DLL <5%

[5] X. Gao, E. Klumperink, G. Socci, M. Bohsali and B. Nauta, "Spur Reduction Techniques for Phase-Locked Loops Exploiting a Sub-Sampling Phase Detector," *IEEE J. Solid-State Circuits*, vol. 45, no.9, pp. 1809-1821, Sept. 2010.
 
# Spur Statistics

- Spur from 20 chips with a large  $f_{BW}/f_{ref} = 1/20$



# Outline

---

- Classical CP PLL and PLL FOM
- Sub-Sampling(SS) PLL
- SSPLL Power Reduction Techniques
- SSPLL Spur Reduction Techniques
- **Recent SSPLL Development and Discussion**

# SSPLL Generalized

---

■ The sampled waveform does not need to be sine-wave. The key is high detection gain by sampling high  $dv/dt$  slope.

■ It works with any waveform, can also be applied to e.g. ring oscillators [7-8]. Just the phase detection gain need to be generalized:


$$\beta_{SSPD} = \frac{\Delta V_{sam}}{\Delta \phi_{VCO}} = \frac{SR_{sam}}{2\pi f_{VCO}}$$

■ In more advanced process, SSPD can sample faster and utilize steeper slopes, thus benefiting from scaling. SSPLLs working at 10s-of-GHz have been demonstrated [9-10].
 
# Sub-Sampling TDC

---

■ If we digitize the sampled voltage with an ADC , it will effectively become a time-to-digital converter (TDC)



$$\Delta t_{\text{TDC}} = \frac{\Delta V_{\text{ADC LSB}}}{SR_{\text{sam}}}$$


$$\text{e.g.} \quad = \frac{1\text{mV}}{10\text{GV} / \text{s}} = 0.1\text{ps}$$

- The resolution is nearly two orders of magnitude finer than gate delay and is easily scalable.
- Can be used to implement digital SSPLLs [14-16]

# Extend SSPLL to Fractional-N

 
## ■ DTC based frac-N SSPLL [17-19]

- Use DTC to modulate Ref edges and realize frac-N operation so SSPD only need to handle small phase error



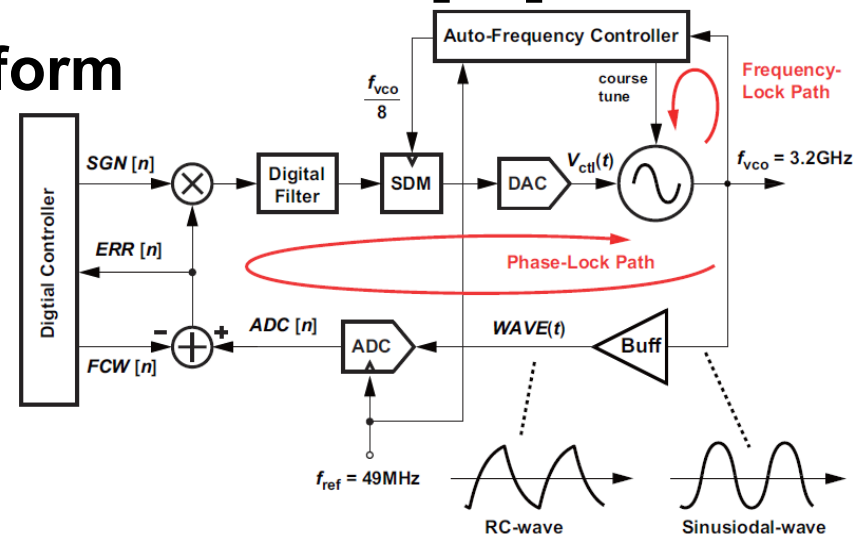
## ■ SSTDC plus extensive digital calibration [16]

- SSTDC digitizes entire waveform
- Extensive digital calibration linearizes the SSTDC over a wide detection range


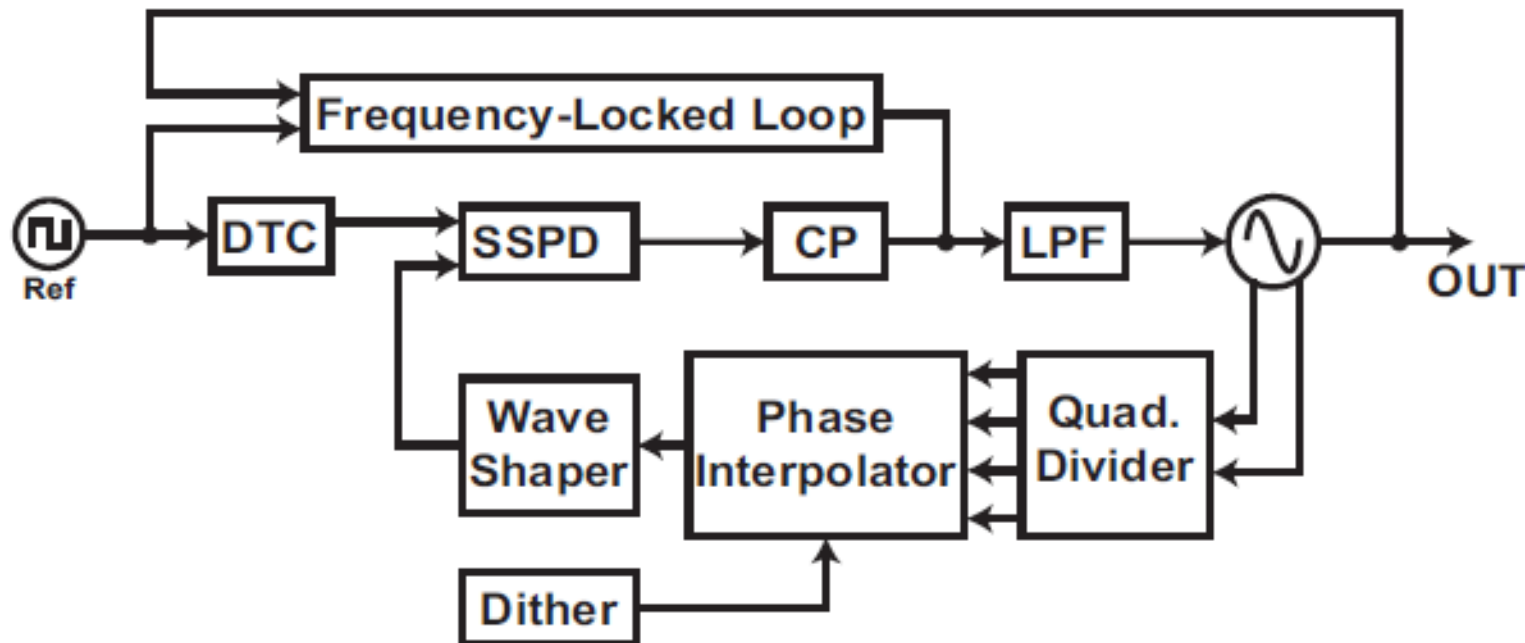
# Extend SSPLL to Fractional-N, Cont'd

- **DTC + Phase Interpolator frac-N SSPLL [26]**
  - The use of phase interpolator together with DTC relaxes the DTC's resolution and dynamic range requirement
  - Achieved -246dB FOM, current record for frac-N PLLs





# References

---

1. X. Gao, E. Klumperink, P. J. F. Geraedts and B. Nauta, "Jitter Analysis and a Benchmarking Figure-of-Merit for Phase-Locked Loops," *IEEE Trans. Circuits Syst. II*, vol. 56, no. 2, pp. 117-121, Feb. 2009.
2. X. Gao, E. Klumperink, M. Bohsali and B. Nauta, "A Low Noise Sub-Sampling PLL in Which Divider Noise is Eliminated and PD/CP Noise is not Multiplied by  $N^2$ ," *IEEE J. Solid-State Circuits*, vol. 44, no. 12, pp. 3253-3263, Dec. 2009.
3. C.-W. Hsu, K. Tripurari, S.-A. Yu and P. R. Kinget, "A Sub-Sampling-Assisted Phase-Frequency Detector for Low-Noise PLLs With Robust Operation Under Supply Interference," *IEEE Trans. Circuits Syst. I*, vol. 62, no. 1, pp. 90-99, Jan. 2015.
4. X. Gao, E. Klumperink, G. Socci, M. Bohsali and B. Nauta, "A 2.2 GHz Sub-Sampling PLL with 0.16 ps<sub>rms</sub> Jitter and -125 dBc/Hz In-band Phase Noise at 700  $\mu$ W Loop-Components Power," *IEEE Symposium on VLSI Circuits*, pp. 139-140, Jun. 2010.
5. X. Gao, E. Klumperink, G. Socci, M. Bohsali and B. Nauta, "Spur Reduction Techniques for Phase-Locked Loops Exploiting a Sub-Sampling Phase Detector," *IEEE J. Solid-State Circuits*, vol. 45, no. 9, pp. 1809-1821, Sept. 2010.
6. D. Cai, *et. al.*, "A Dividerless PLL With Low Power and Low Reference Spur by Aperture-Phase Detector and Phase-to-Analog Converter," *IEEE Trans. Circuits Syst. I*, vol. 60, no. 1, pp. 37-50, Jan. 2013.
7. S. D. Vamvakos, *et. al.*, "A 8.125–15.625 Gb/s SerDes using a sub-sampling ring-oscillator phase-locked loop," *IEEE Custom Integrated Circuits Conference (CICC)*, paper 10.1, Sept. 2014.
8. K. Sogo, A. Toya and T. Kikkawa, "A ring-VCO-based sub-sampling PLL CMOS circuit with -119 dBc/Hz phase noise and 0.73 ps jitter," *IEEE European Solid State Circuits Conference (ESSCIRC)*, pp. 253-256, Sept. 2012.
9. X. Yi, C. C. Boon, J. Sun, N. Huang and W. M. Lim, "A low phase noise 24/77 GHz dual-band sub-sampling PLL for automotive radar applications in 65 nm CMOS technology," *IEEE Asian Solid-State Circuits Conference (A-SSCC)*, pp. 417-420, Nov. 2013.
10. T. Siriburanon, *et. al.*, "A 60-GHz sub-sampling frequency synthesizer using sub-harmonic injection-locked quadrature oscillators," *IEEE Radio Frequency Integrated Circuits Symposium (RFIC)*, pp. 105-108, Jun. 2014.
11. C.-F. Liang and K.-J. Hsiao, "An Injection-Locked Ring PLL with Self-Aligned Injection Window," *IEEE Int. Solid-State Circuits Conference (ISSCC)*, pp. 90-92, Feb. 2011.
12. I.-T. Lee, *et. al.*, "A divider-less sub-harmonically injection-locked PLL with self-adjusted injection timing," *IEEE Int. Solid-State Circuits Conference (ISSCC)*, pp. 414-415, Feb. 2013.
13. X. Gao, "Low Jitter Low Power Phase Locked Loops Using Sub-Sampling," PhD thesis, University of Twente, ISBN-978-90-365-3022-4, 2010.

# References Cont'd

---

14. T. Siriburanon, *et. al.*, "A 2.2GHz -242dB-FOM 4.2mW ADC-PLL using digital sub-sampling architecture," *IEEE Solid-State Circuits Conference - (ISSCC)*, paper 25.2, Feb. 2015.
15. Z. Ru, P. Geraedts, E. Klumperink and B. Nauta, "A 12GHz 210fs 6mW Digital PLL with Sub-sampling Binary Phase Detector and Voltage-Time Modulated DCO," *IEEE Symp. VLSI Circuits*, pp. 194-195, June 2013.
16. Z.-Z. Chen, *et. al.*, "Sub-sampling all-digital fractional-N frequency synthesizer with -111dBc/Hz in-band phase noise and an FOM of -242dB," *IEEE Solid-State Circuits Conference - (ISSCC)*, paper 14.9, Feb. 2015.
17. K. Raczkowski, N. Markulic, B. Hershberg, J. Van Driessche, and J. Craninckx, "A 9.2-12.7 GHz wideband fractional-N subsampling PLL in 28nm CMOS with 280fs RMS jitter," *IEEE Radio Frequency Integrated Circuits Symposium (RFIC)*, pp.89-92, Jun. 2014.
18. W.-S. Chang, P.-C. Huang and T.-C. Lee, "A Fractional-N Divider-Less Phase-Locked Loop With a Subsampling Phase Detector," *IEEE J. Solid-State Circuits*, vol.49, no.12, pp.2964-2975, Dec. 2014.
19. N. Markulic, K. Raczkowski, P. Wambacq and J. Craninckx, "A 10-bit, 550-fs step Digital-to-Time Converter in 28nm CMOS," *IEEE European Solid State Circuits Conference (ESSCIRC)*, pp.79-82, Sept. 2014.
20. S. Ikeda, S.-Y. Lee, H. Ito, N. Ishihara and K. Masu, "A 0.52-V 5.7-GHz low noise sub-sampling PLL with dynamic threshold MOSFET," *IEEE Asian Solid-State Circuits Conference (A-SSCC)*, pp.365-368, Nov. 2014.
21. J. Liang, Z. Zhou, J. Han and D. G. Elliott, "A 6.0-13.5 GHz Alias-Locked Loop Frequency Synthesizer in 130 nm CMOS," *IEEE Trans. Circuits Syst. I*, vol.60, no.1, pp.108-115, Jan. 2013.
22. P. Kinget, "Integrated GHz voltage controlled oscillators," *Analog Circuit Design: (X)DSL and Other Communication Systems; RF MOST Models; Integrated Filters and Oscillators*, Kluwer, 1999, pp.353-381.
23. C. S. Vaucher, *Architectures for RF Frequency Synthesizers*. Boston, MA: Kluwer, 2002.
24. I.-T. Lee, K.-H. Zeng and S.-I. Liu, "A 4.8-GHz Dividerless Subharmonically Injection-Locked All-Digital PLL With a FOM of -252.5 dB," *IEEE Trans. Circuits Syst. II*, vol.60, no.9, pp.547-551, Sept. 2013.
25. Z. Ru, C. Palattella, P. Geraedts, E. Klumperink and B. Nauta, "A High-Linearity Digital-to-Time Converter Technique: Constant-Slope Charging," *IEEE J. Solid-State Circuits*, vol.50, no.6, pp.1412-1423, Jun. 2015.
26. A. T. Narayanan, *et. al.*, "A Fractional-N Sub-Sampling PLL using a Pipelined Phase-Interpolator with a FoM of -246dB," *IEEE European Solid State Circuits Conference (ESSCIRC)*, pp.380-383, Sept. 2015.