

Methods for Finding Globally Maximum-efficiency Impedance Matching Networks with Lossy Passives

**Chandrakanth R Chappidi and Kaushik Sengupta,
Electrical Engineering,
Princeton University**




Outline

- Concept of Impedance Matching and Motivation
 - Non Optimality of Conjugate Matching Networks
 - Globally Optimal Impedance Matching Networks
 - Design Examples
-

Outline


- Concept of Impedance Matching and Motivation
 - Non Optimality of Conjugate Matching Networks
 - Globally Optimal Impedance Matching Networks
 - Design Examples
-

Impedance Matching

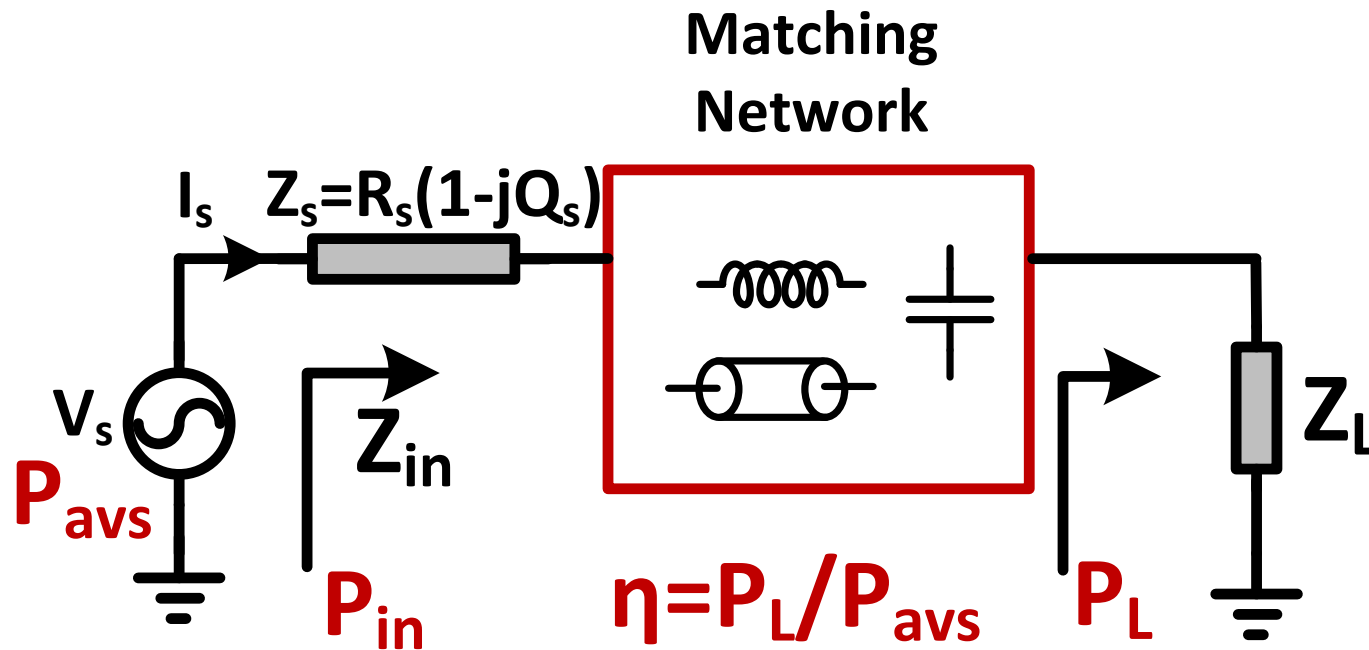


- For maximum power transfer from the source, $Z_{in,opt} = Z_s^*$
- Matching network transforms Z_L to $Z_{in,opt}$ at the given frequency of operation.

Impedance Matching Examples

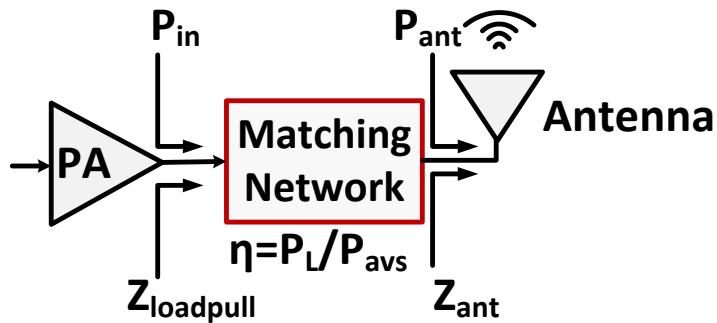

Power Amplifier

$$\eta_{total} = \eta_{PA} * \eta_{MN}$$


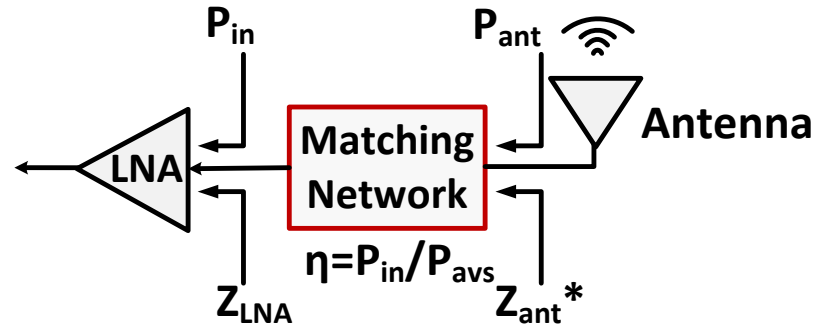


Low-noise Amplifier

$$NF \sim NF_{LNA} + \eta_{MN}(\text{dB})$$


- Maximize power transfer to the antenna at the transmitter front-end.
- **Loss in matching network directly affects PA/Tx efficiency.**
- Maximize power transfer to the LNA at the receiver front end
- **Loss in matching network directly affects LNA/Rx noise figure.**

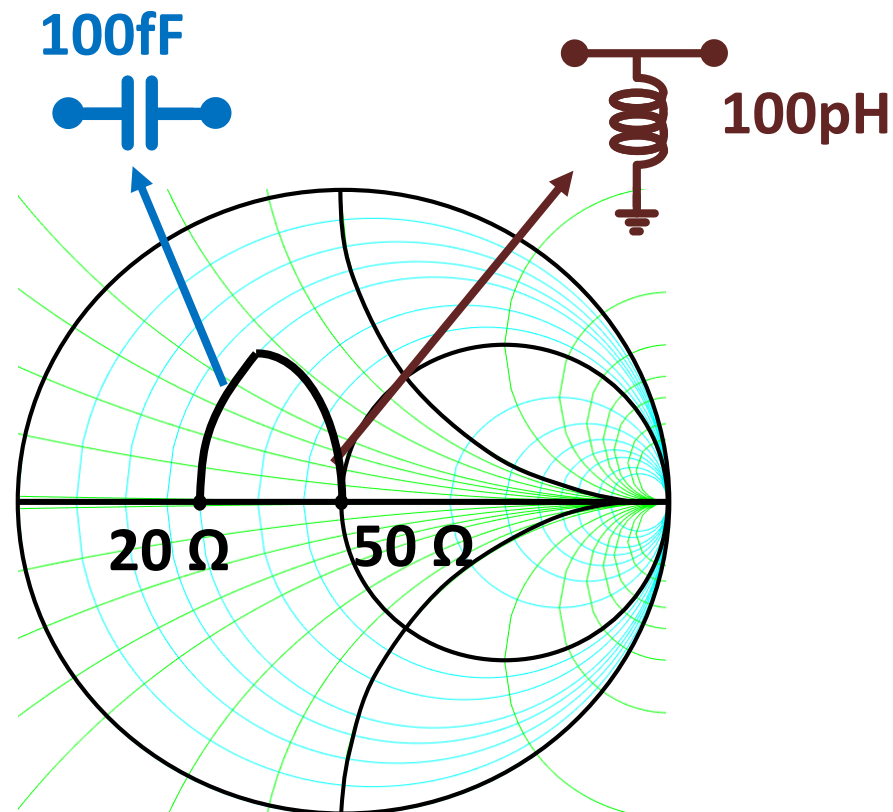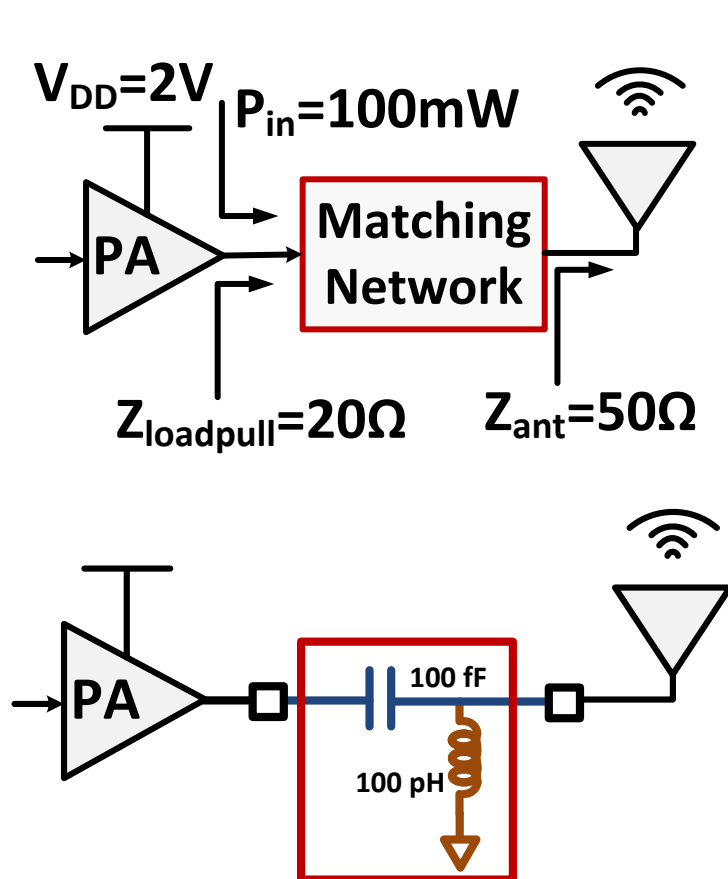Impedance Matching Example on Smith Chart





- Impedance transformation can be represented by a path on the Smith Chart

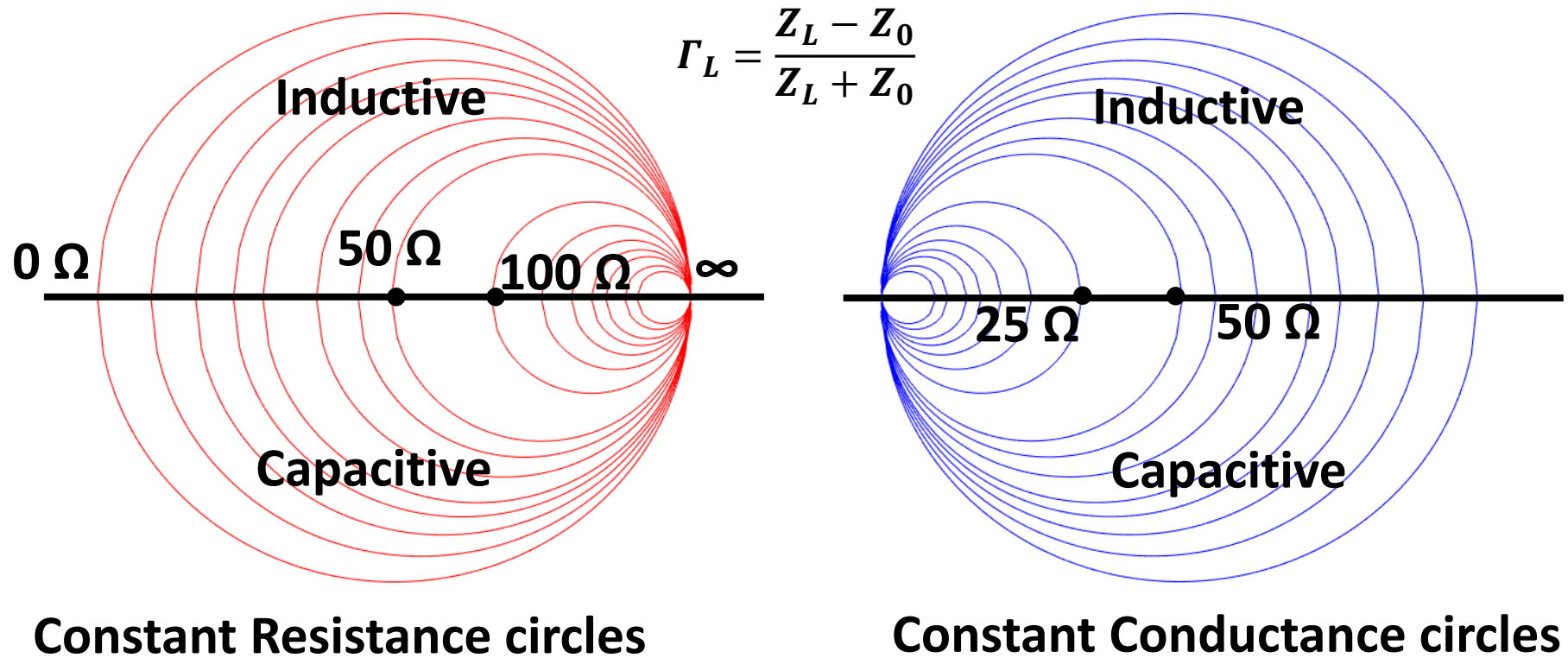Smith Chart as a Graphical Representation




- Smith Chart is a graphical representation of impedance and transformation between impedances

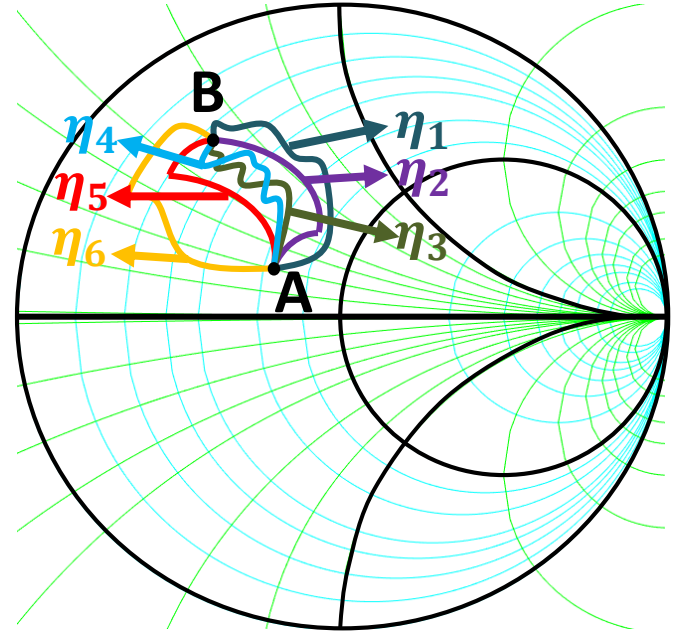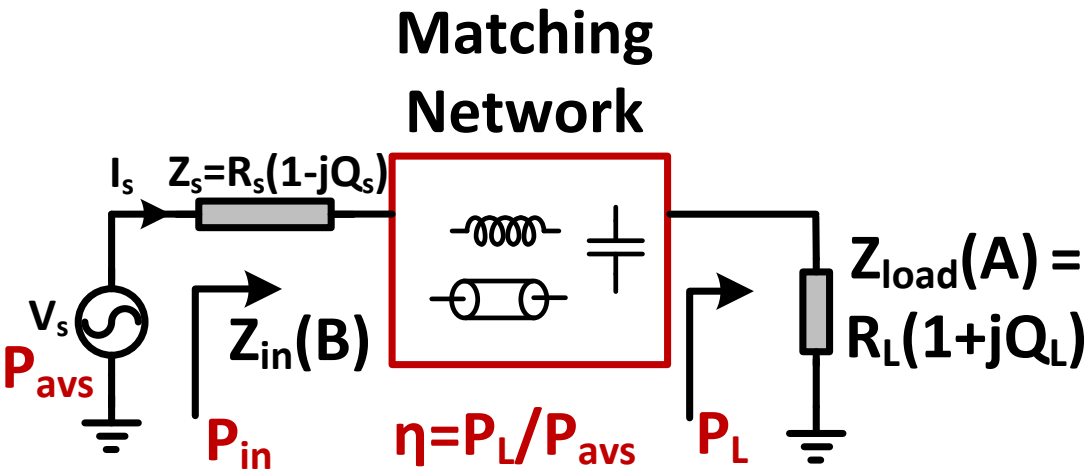Number of Possible Paths in Transformation





- The matching network for given Z_L and Z_{in} is not unique
- Ideally, there are infinite possible paths between the impedances (A and B) on the Smith Chart: **Which one's the most efficient?**

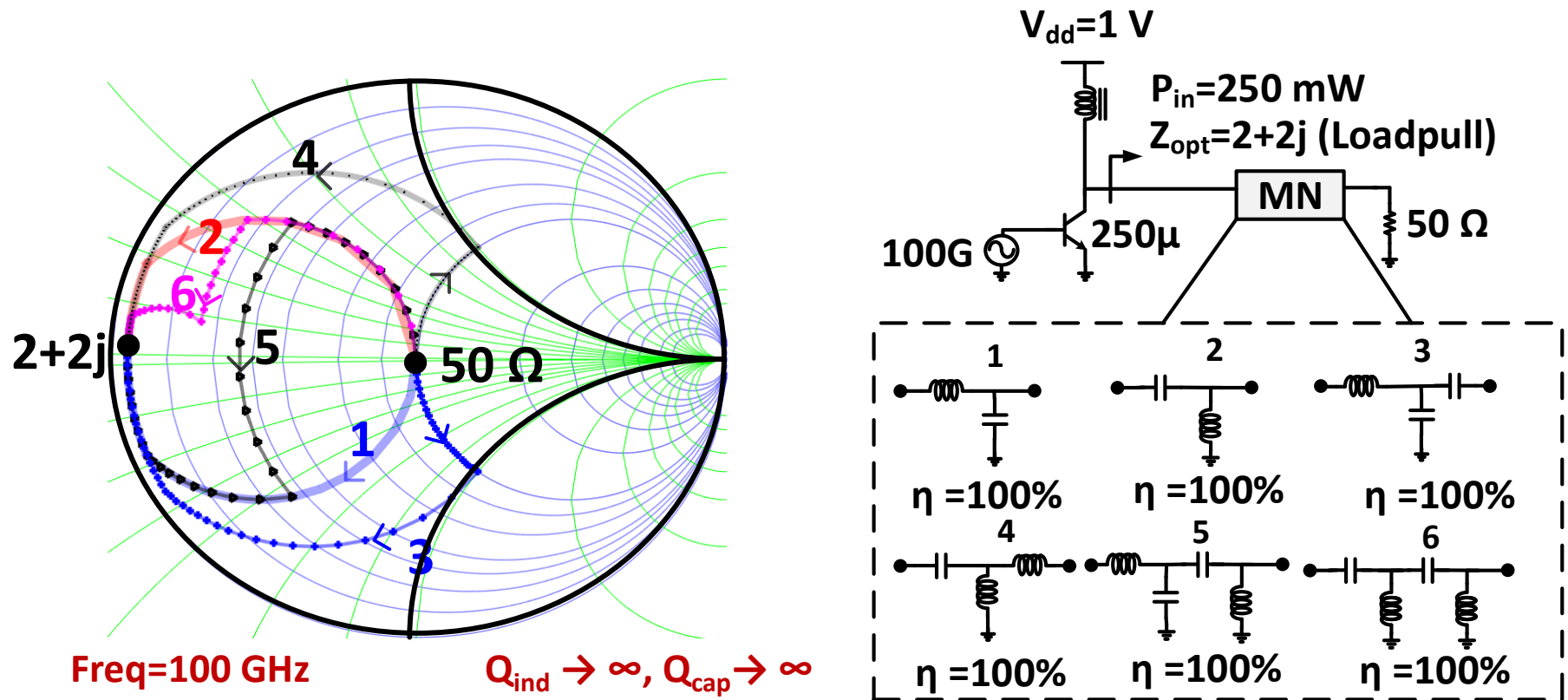Matching Network with **Lossless** Passives



- Of course, for lossless passives, the efficiency of all paths are the same (100%)
- However, they will have different bandwidths.

Matching Network with **Lossy** Passives

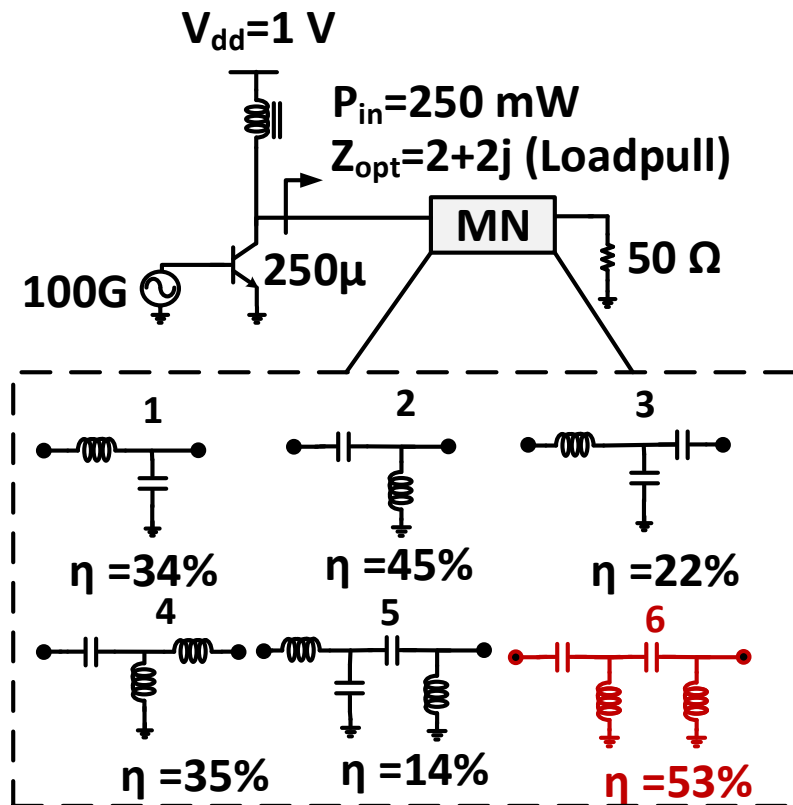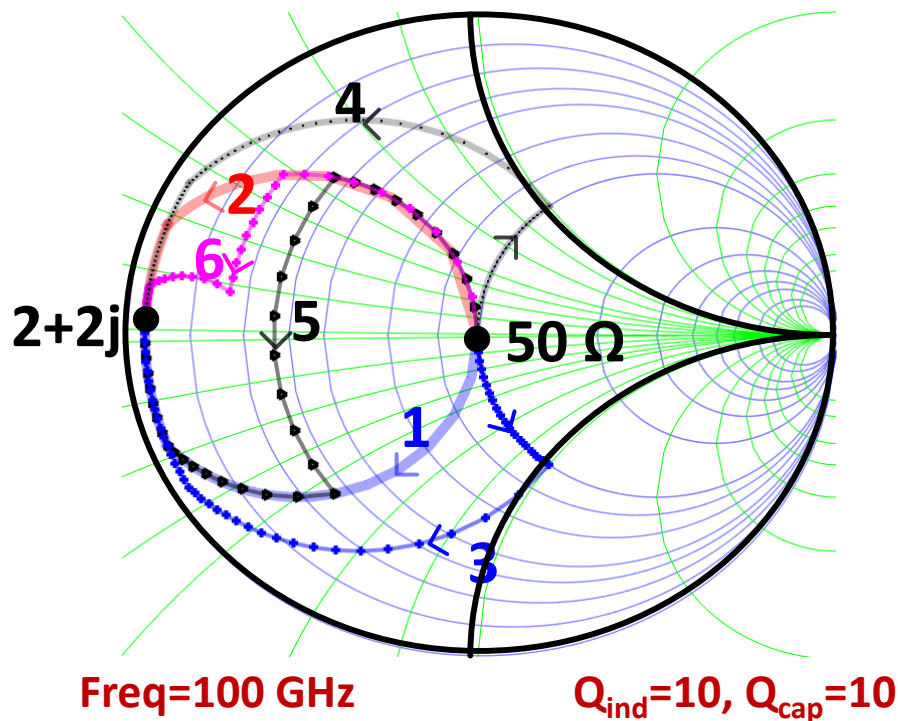


- Efficiency of each path (representing different matching network) is different for lossy passives.
- η_{max} (observed here) = **53% for a two-stage network.**

Outline


- Concept of Impedance Matching and Motivation
 - **Non Optimality of Conjugate Matching Networks**
 - Globally Optimal Impedance Matching Networks
 - Design Examples
-

Non-optimality of Conjugate Matching

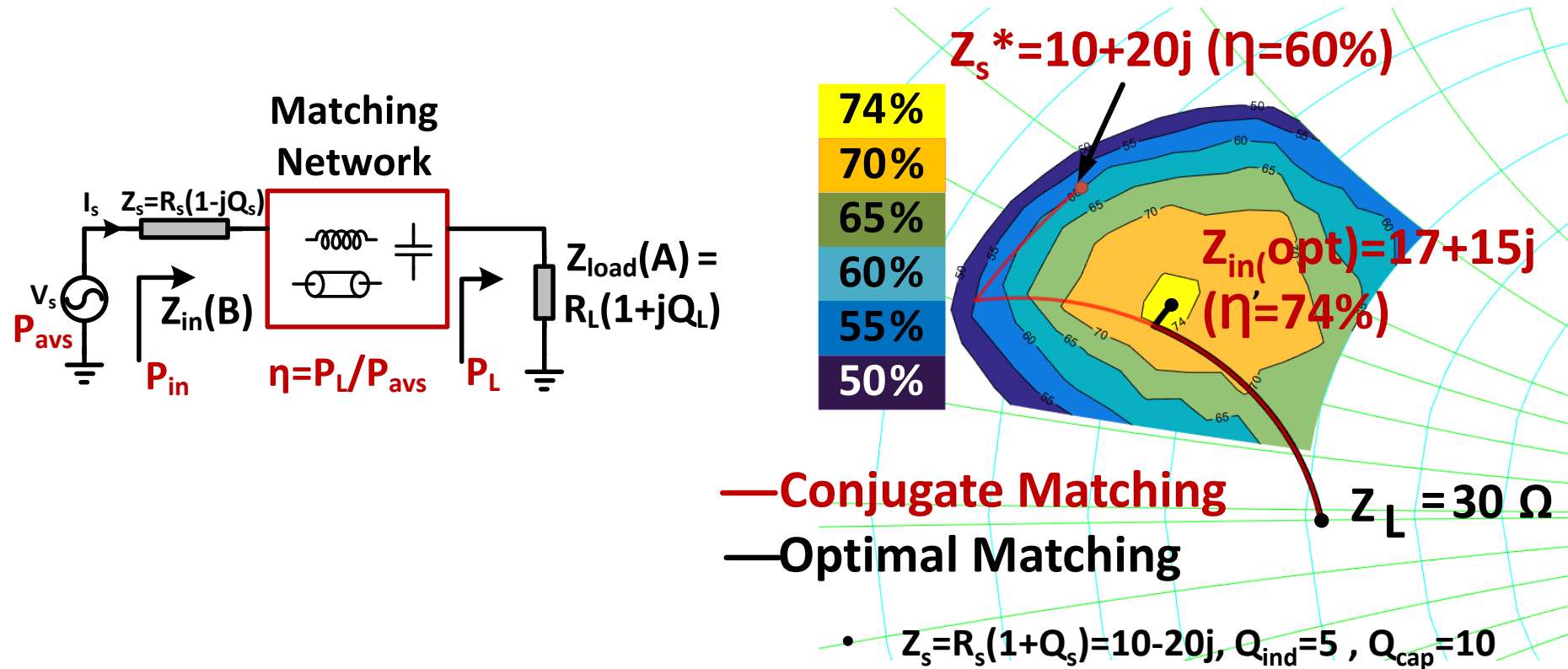


- Conjugate matching may be sub-optimal because more power may be wasted in transforming to $Z_{in} = Z_s^*$
- Maximizing P_{in} does not necessarily maximize P_L

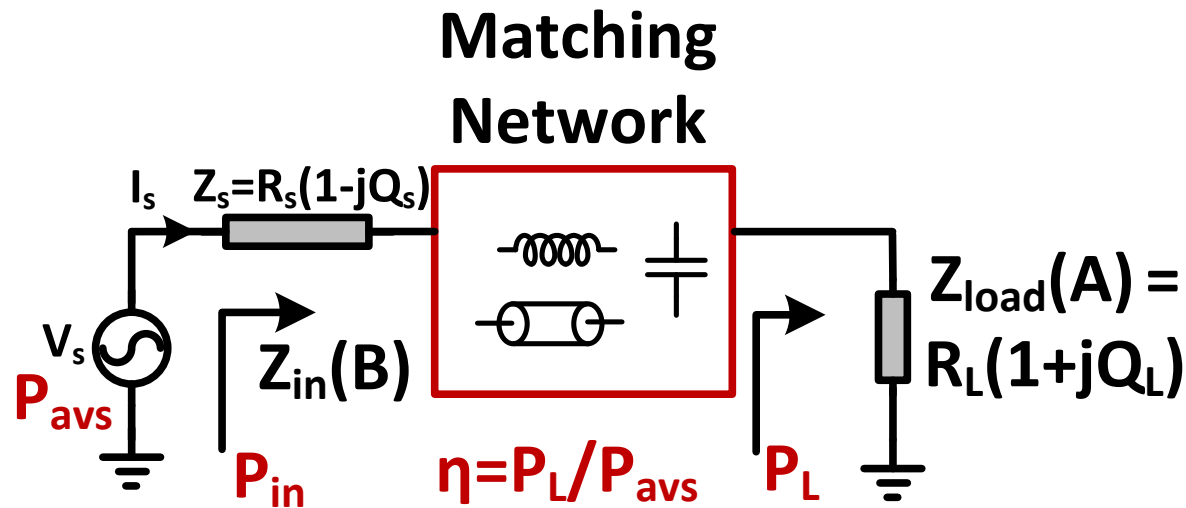Analysis of Optimal Inductor-only matching




- $P_{reac} = \frac{1}{2} I_s^2 X_{in} = P_{ind} - P_{cap} + P_{reac,L}$
- $P_{loss} = \frac{P_{ind}}{Q_{ind}} + \frac{P_{cap}}{Q_{cap}} \geq \left| \frac{P_{ind} - P_{cap}}{Q_{ind}} \right| = \frac{P_X - P_{reac,L}}{Q_{ind}}$
- $X_{in,opt} = R_s \frac{Q_{ind}^2 Q_s - Q_s - 2Q_{ind}}{1 + Q_{ind}^2}$, $R_{in,opt} = R_s \frac{2Q_{ind} Q_s + Q_{ind}^2 - 1}{1 + Q_{ind}^2}$, $P_{Load,Max} =$
 $P_{avs} \frac{1 + Q_{ind}^2}{Q_{ind}(Q_{ind} + Q_s) \left(1 - \frac{Q_L}{Q_{ind}}\right)}$

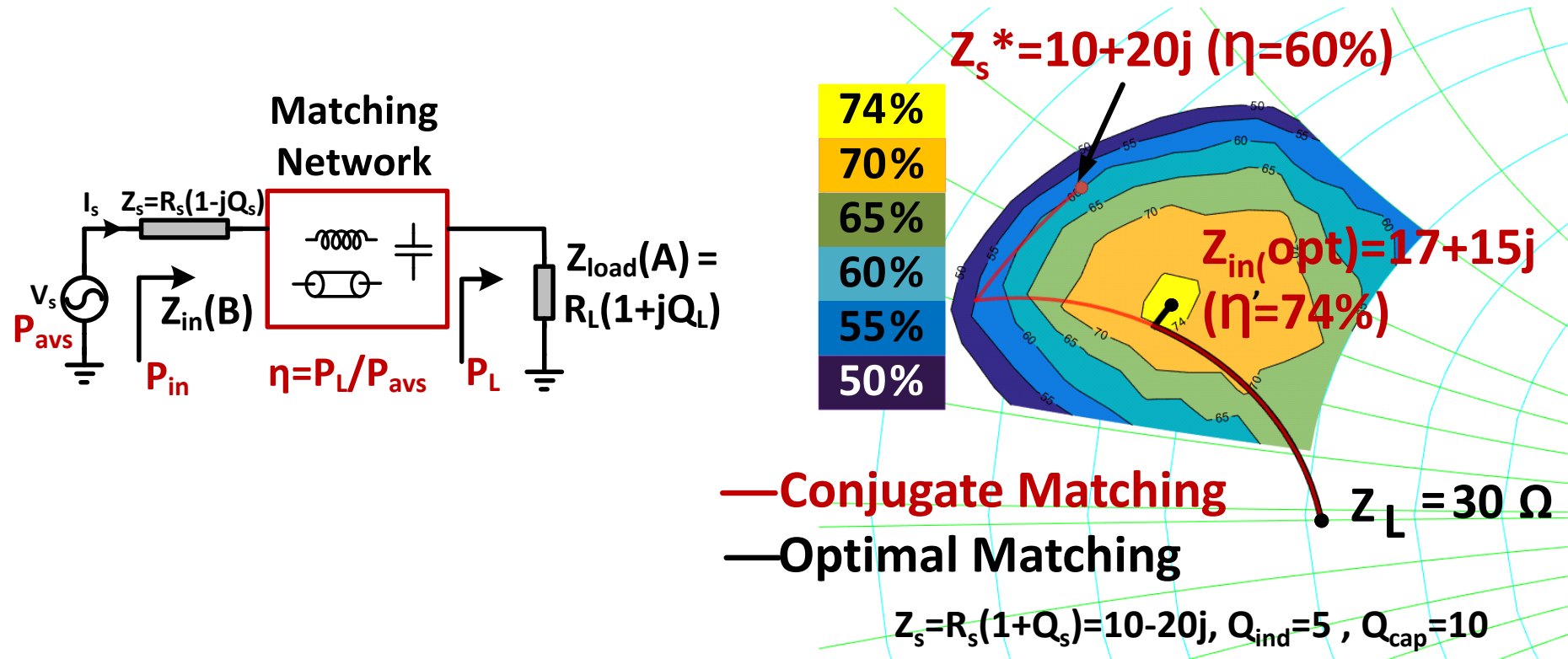Analysis of Optimal Inductor-only matching




- $R_{in,opt} = R_s \frac{2Q_{ind}Q_s + Q_{ind}^2 - 1}{1 + Q_{ind}^2} = 17$, $X_{in,opt} = R_s \frac{Q_{ind}^2 Q_s - Q_s - 2Q_{ind}}{1 + Q_{ind}^2} = 15$,
- $P_{Load,Max} = P_{avs} \frac{1 + Q_{ind}^2}{Q_{ind}(Q_{ind} + Q_s) \left(1 - \frac{Q_L}{Q_{ind}}\right)} = 0.74$, $P_{in} = 0.9 P_{avs}$

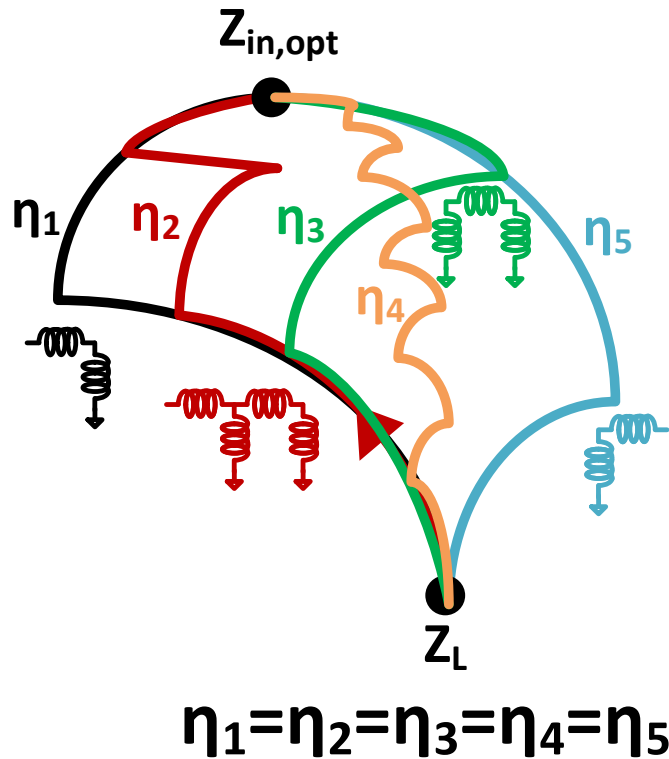Inductor-only matching (Smith Chart Coverage)



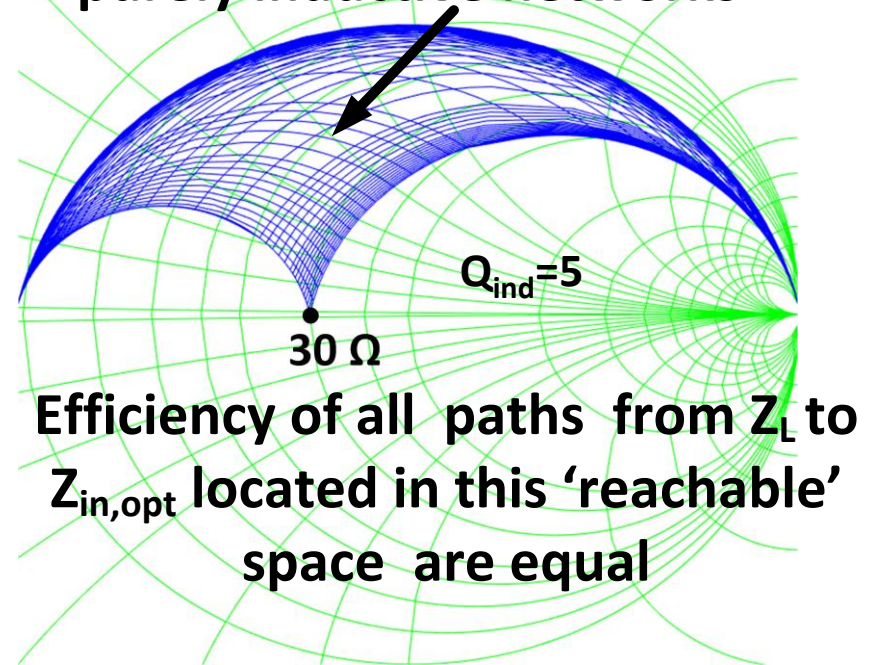Range of possible $Z_{in,opt}$ through purely inductive networks





- Inductor-only paths are optimal and have the same efficiency
- Given Z_L , there is a limited coverage on the Smith Chart for Inductor-only matching

Outline


- Concept of Impedance Matching and Motivation
 - Non Optimality of Conjugate Matching Networks
 - **Globally Optimal Impedance Matching Networks**
 - Design Examples
-

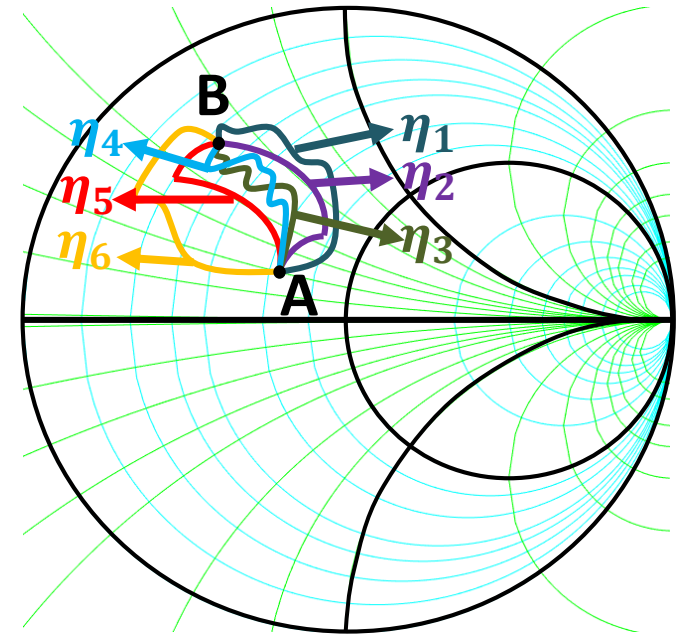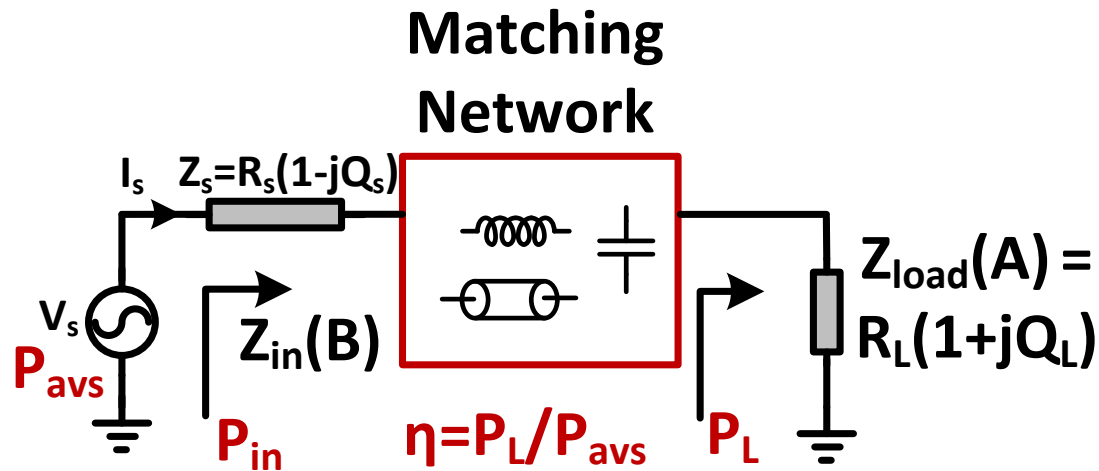Globally Optimal Path between Z_A and Z_B




- What is the globally optimally efficient path between two impedances Z_A and Z_B ?
- Any arbitrary path on the Smith can be realized with infinitesimally small/large elements, if necessary.

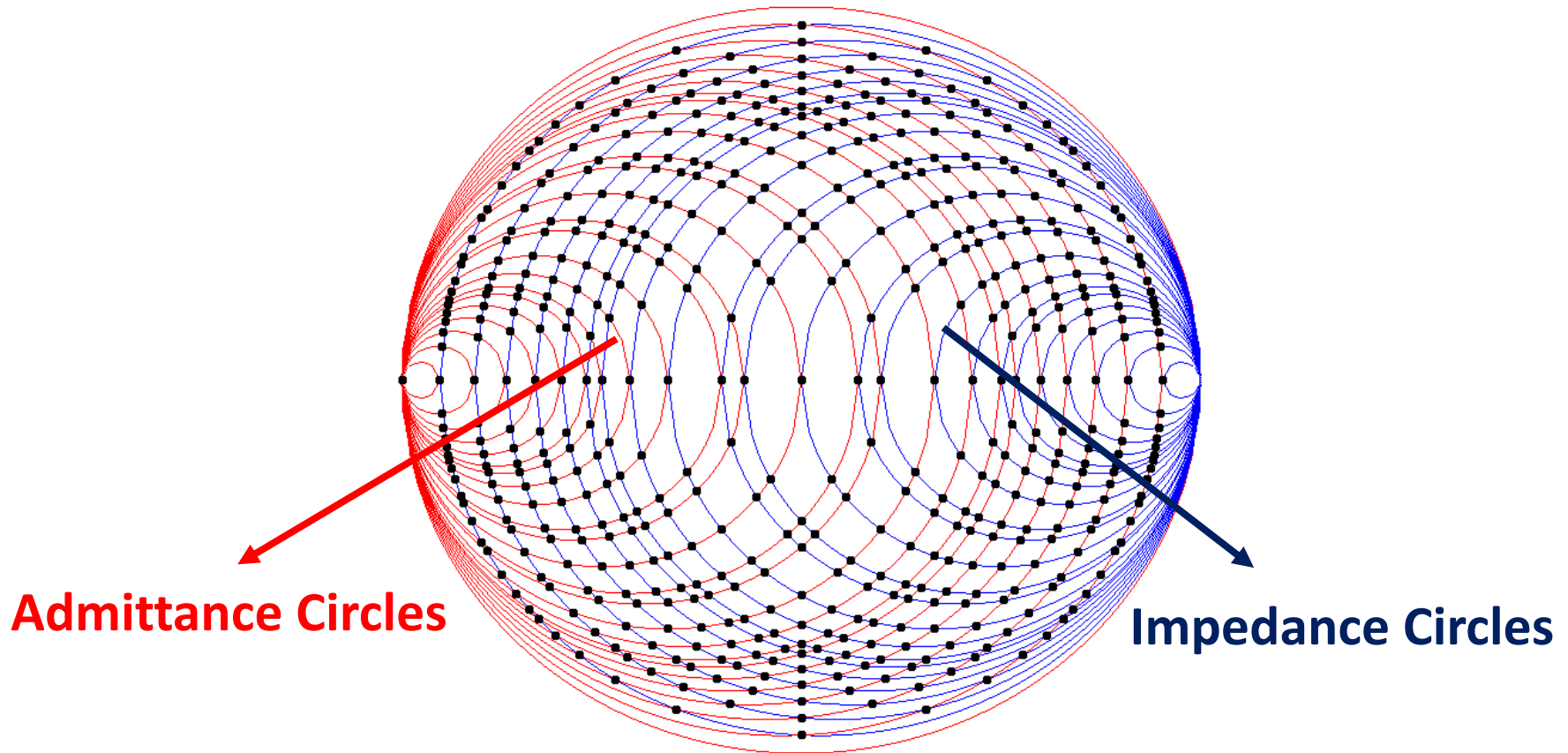Globally Optimal Path between Z_A and Z_B




- Discretize the Smith Chart Space into infinitesimally close admittance and impedances.

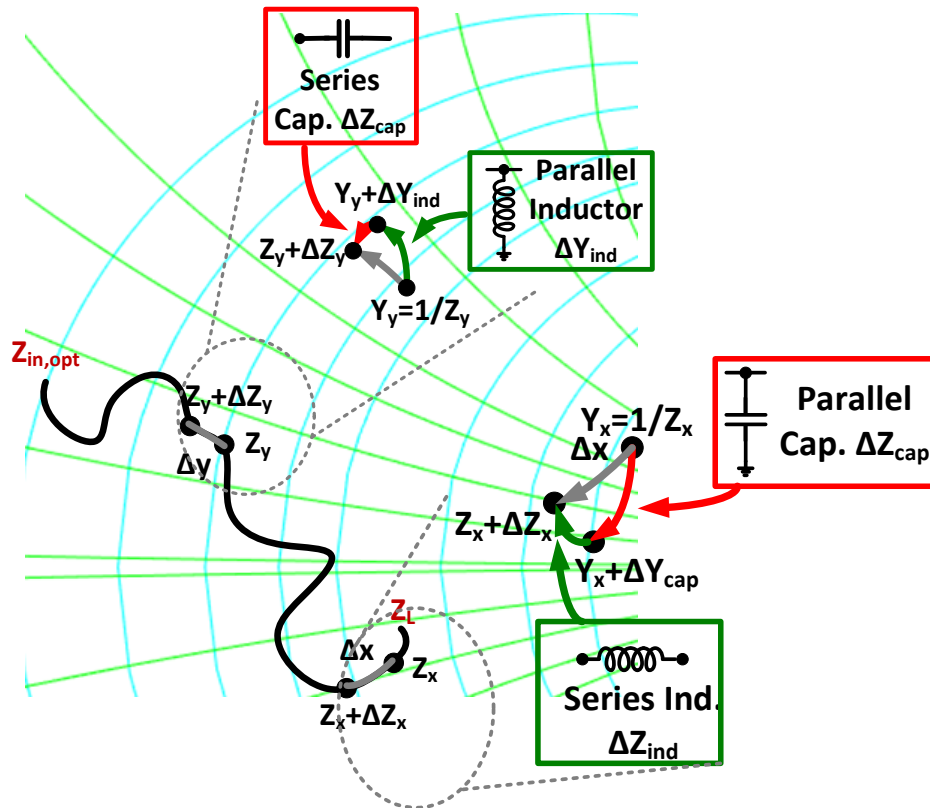Globally Optimal Path between Z_A and Z_B




Loss in series element

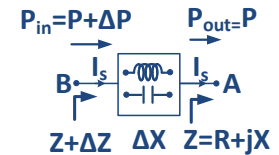

$$\eta = \frac{P_{out}}{P_{in}} = \frac{\frac{I_s^2}{2} R}{\frac{I_s^2}{2} \left(R + \frac{|\Delta X|}{Q} \right)} = \frac{R}{R + \frac{|\Delta X|}{Q}} = \frac{1}{1 + \frac{|\Delta X|}{RQ}}$$

Loss in parallel element

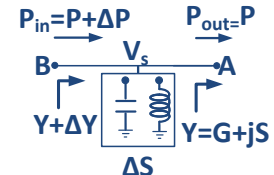


$$\eta = \frac{P_{out}}{P_{in}} = \frac{\frac{V_s^2}{2} G}{\frac{V_s^2}{2} \left(G + \frac{|\Delta S|}{Q} \right)} = \frac{G}{G + \frac{|\Delta S|}{Q}} = \frac{1}{1 + \frac{|\Delta S|}{GQ}}$$

$$P_{loss} = \int dP \approx \sum \Delta P \quad \eta_{path} = \prod_{i=1}^n \eta_i$$

- Efficiency of any arbitrary path can be reduced to the product of efficiencies of the constituent sub-paths.

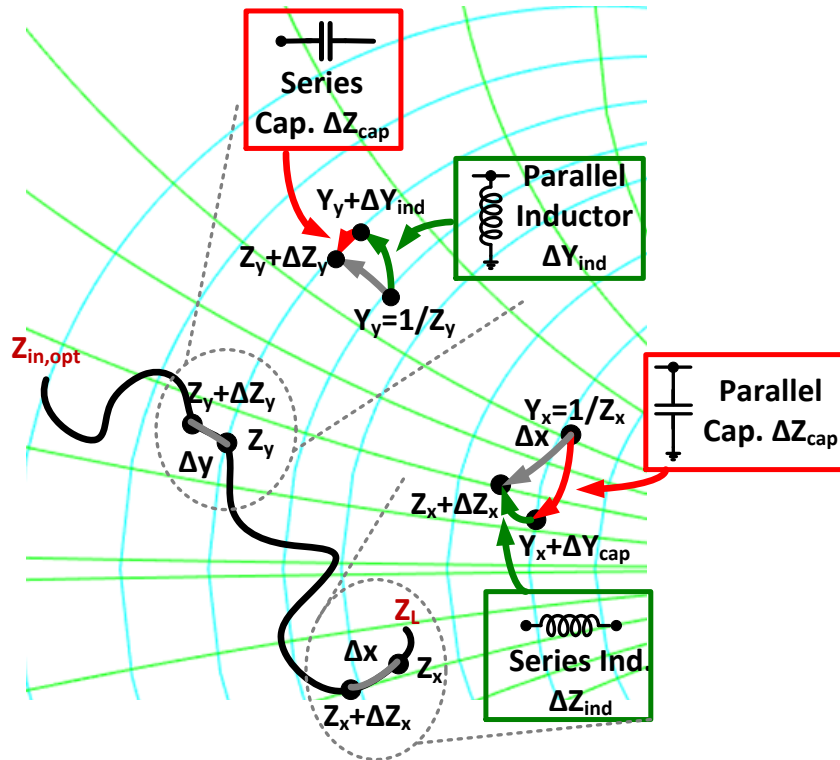Globally Optimal Path between Z_A and Z_B




$$P_{loss} = \int dP \approx \sum \Delta P$$

$$\eta_{path} = \prod_{i=1}^n \eta_i$$


Defining $d_i = -\ln(\eta_i) \Rightarrow d_{tot} = \sum d_i$
Maximize $\eta \Rightarrow Minimize d_{tot}$

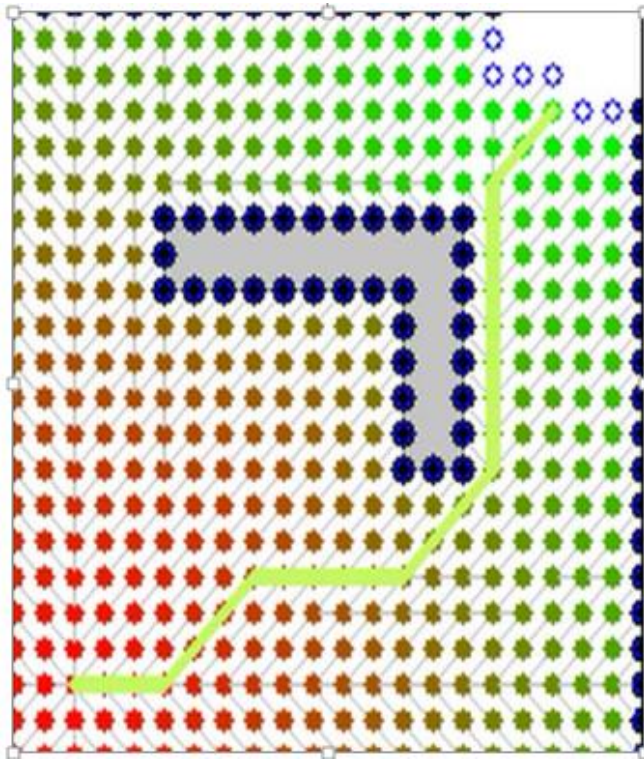- **Problem of optimally efficient matching network reduces to finding the shortest distance in a transformed space.**

Shortest Path (Maximally Efficient) Algorithm: Dijkstra's Algorithm





Dijkstra's Algorithm (Wikipedia)

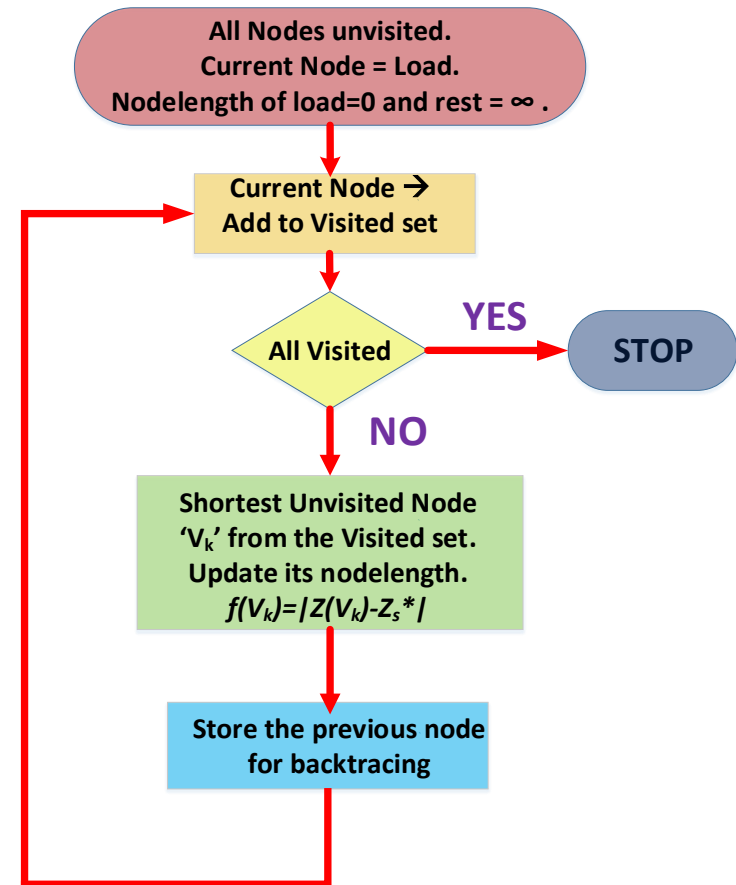


- Globally maximally efficient algorithm can be obtained from Dijkstra's Algorithm with complexity $O(V^2)$ (V =no. of nodes in the graph)

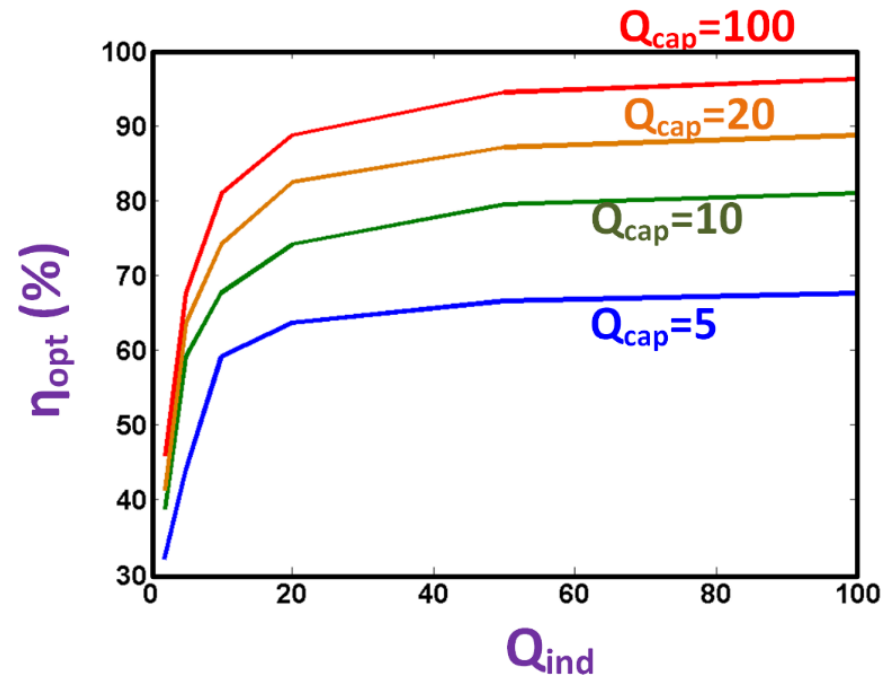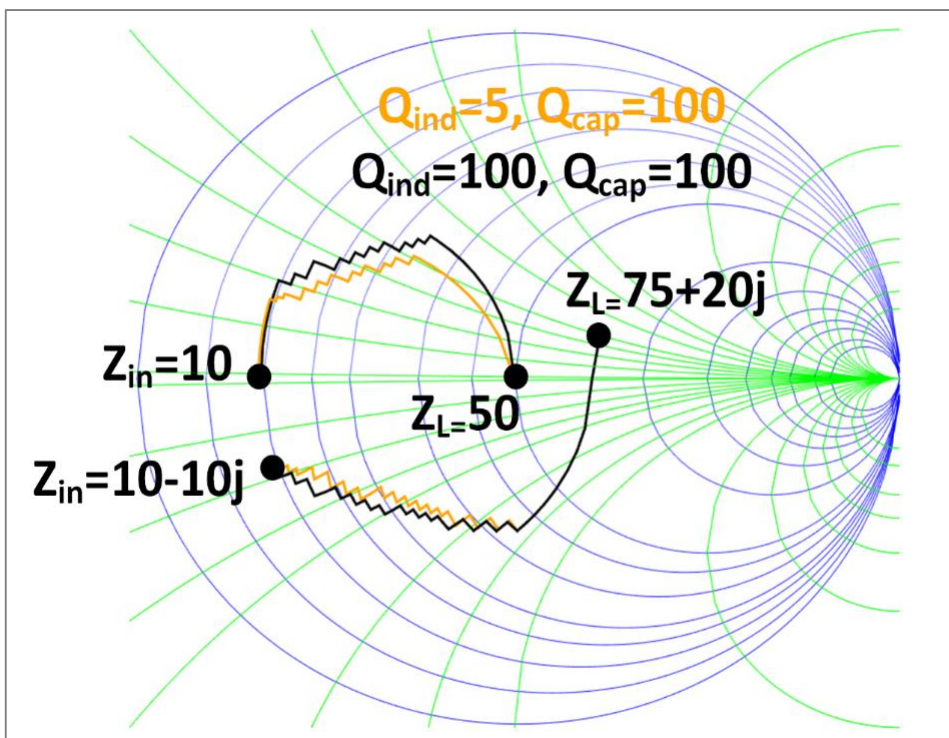Globally Optimally Efficient Path (Example)



- Optimal paths vary with passive quality factors.
- Globally optimal paths can employ elements with infinitesimally small/large values.

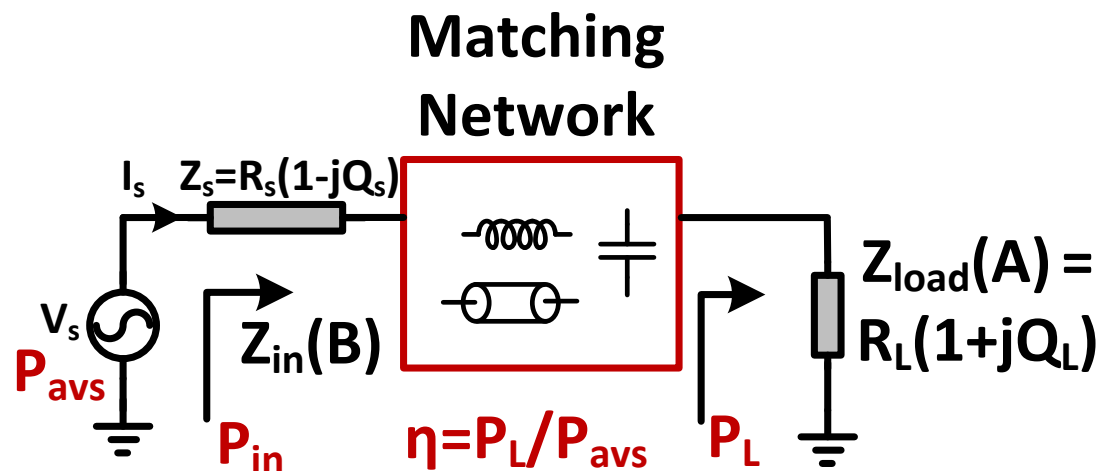Globally Optimally Efficient Power Transfer




- $$\eta_s = \frac{P_{in}}{P_{avs}} = \frac{\frac{0.5 V_s^2 R_{in}}{|Z_s + Z_{in}|^2}}{0.5 \frac{V_s^2 R_s}{(R_s + R_s)^2}} = \frac{4 R_{in} R_s}{|Z_s + Z_{in}|^2}, \quad \eta_{MN} = \frac{P_L}{P_{avs}},$$
- $$\eta_{total} = \frac{P_L}{P_{avs}} = \eta_s \eta_{MN}$$
- Change the function $f(V_k) = -\ln(\eta_{tot})$
- $P_{out} = e^{-f(V_n)}$

Outline


- Concept of Impedance Matching and Motivation
 - Non Optimality of Conjugate Matching Networks
 - Globally Optimal Impedance Matching Networks
 - **Design Examples**
-

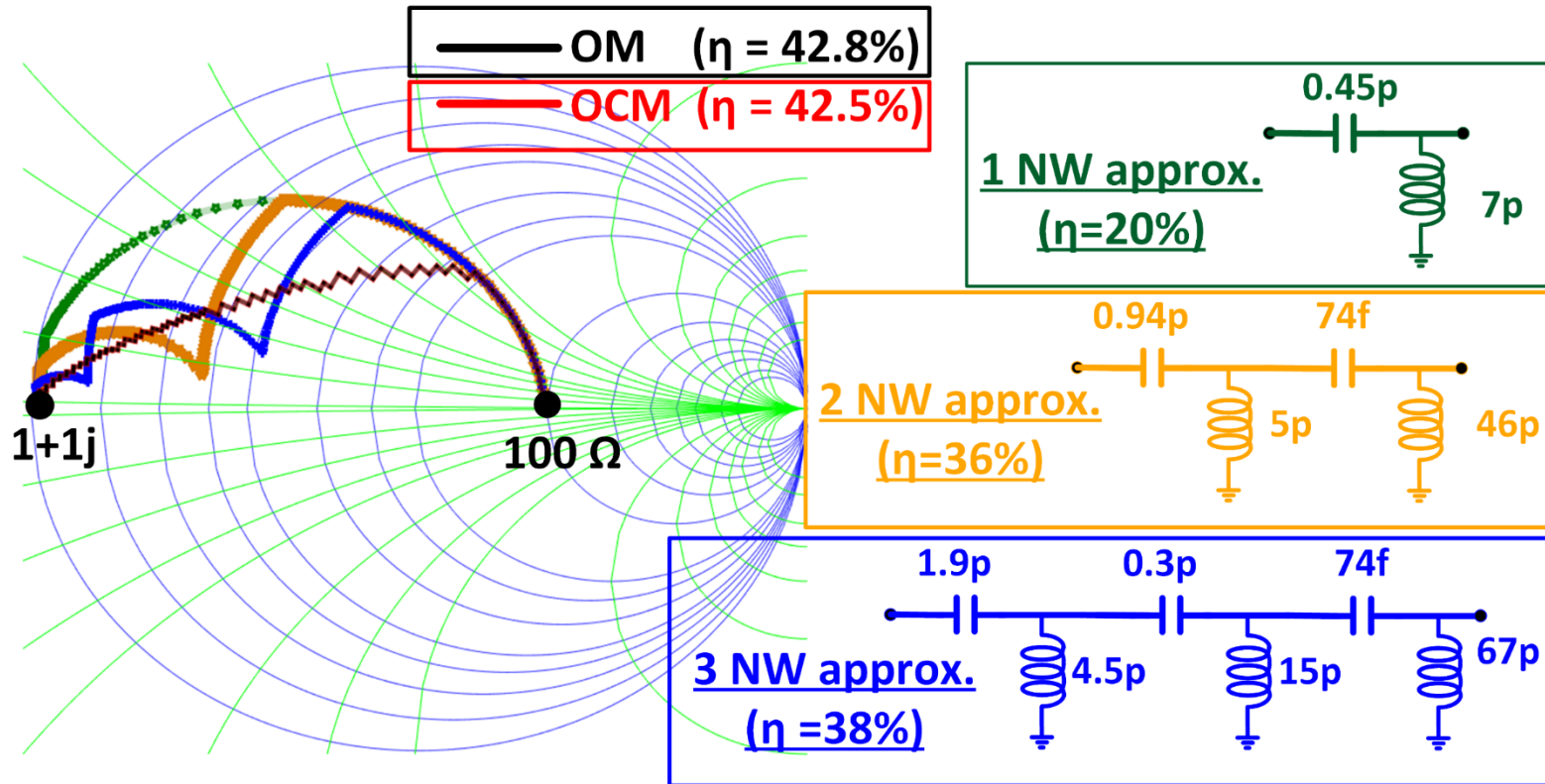Example1: Approximation by finite network @100G




- Globally optimal network provides insight into an optimally efficient network of finite order

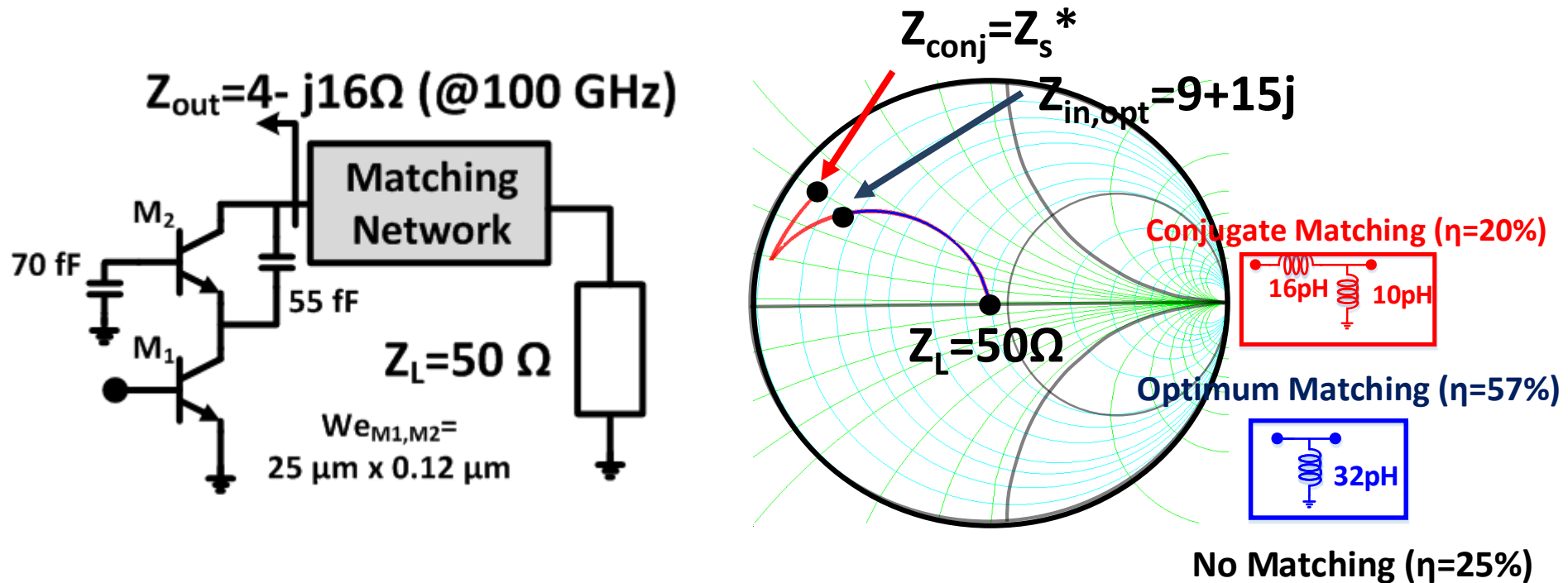Ex. 2: Optimal Matching Vs Optimal Conjugate





- Optimally matching (even no matching) can have significantly higher efficiency than conjugate matching.

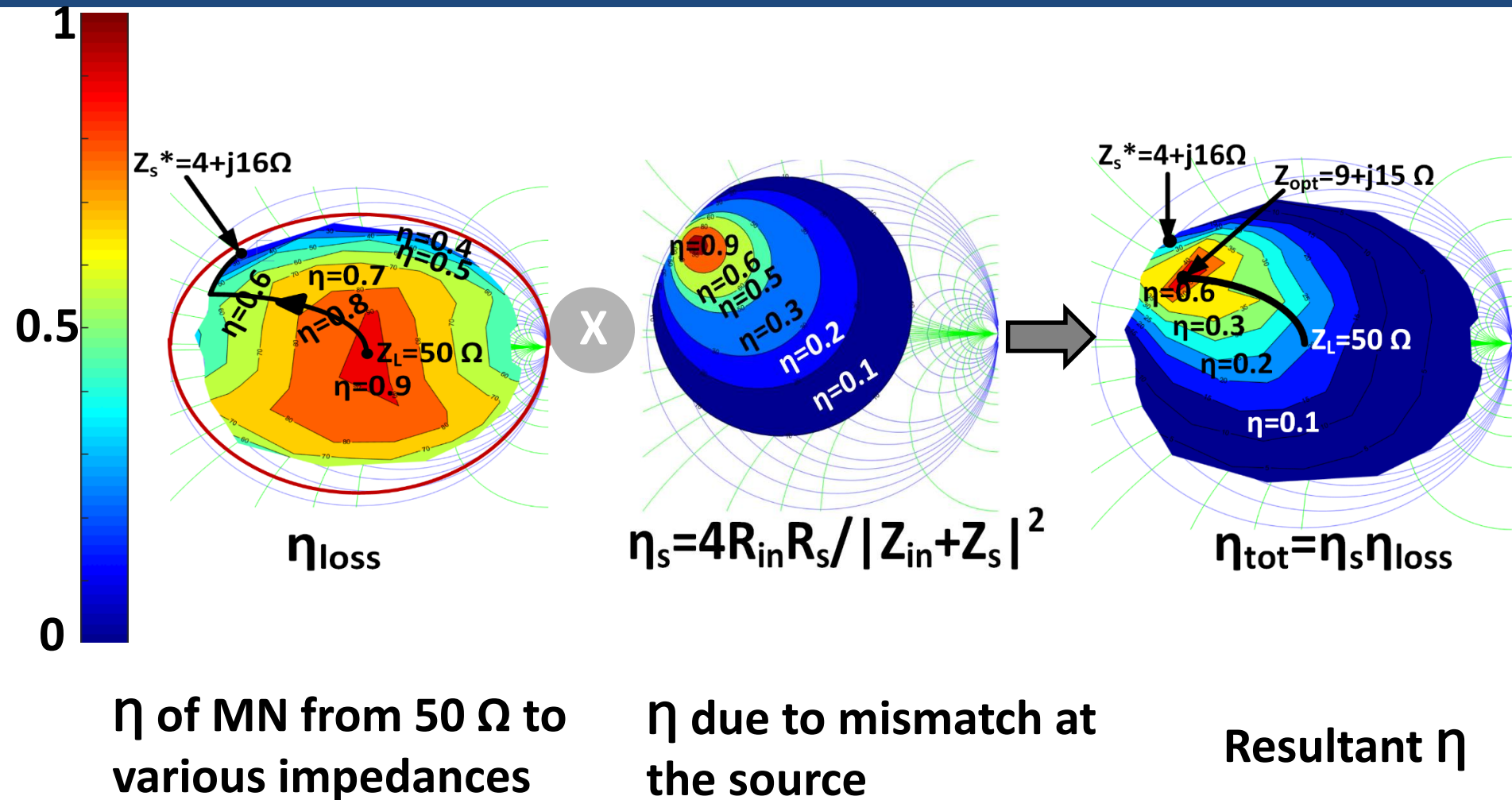Ex. 2: Optimal Matching Vs Optimal Conjugate



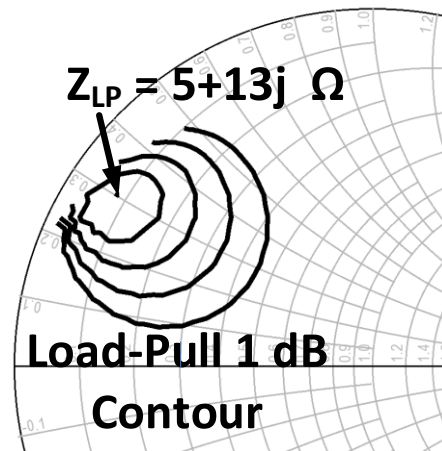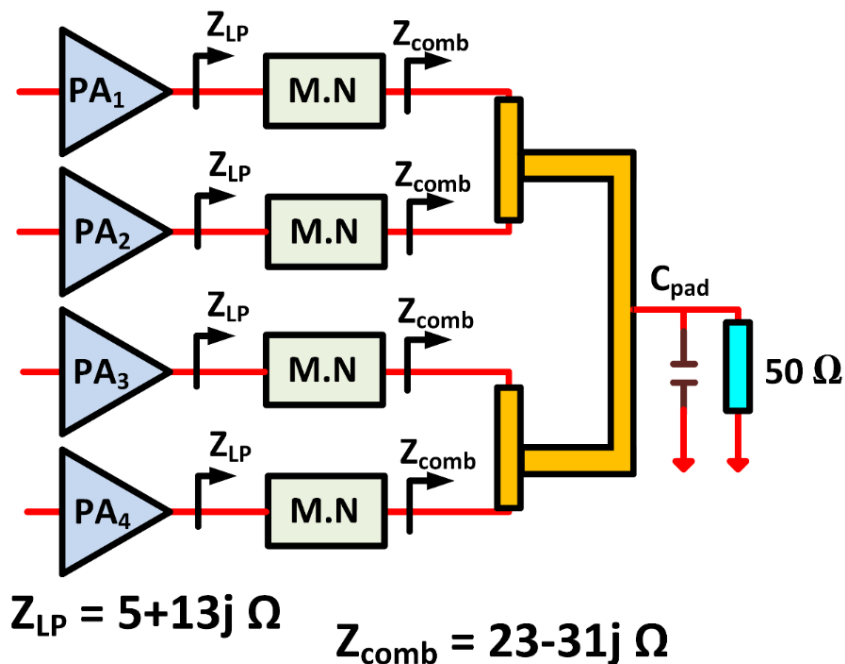Combiner Network for mm-Wave PA (100 GHz)



Algorithm for Optimal Matching

X

$$Z_{LP} = 5 + 13j \, \Omega$$

$$Z_{opt} = 6 + 12j \, \Omega$$

Optimal Loadpull matching


Optimum matching

22 pH


20 pH

$$Z_{comb} = 23 - 31j \, \Omega$$

100 GHz PA Chip Micrograph

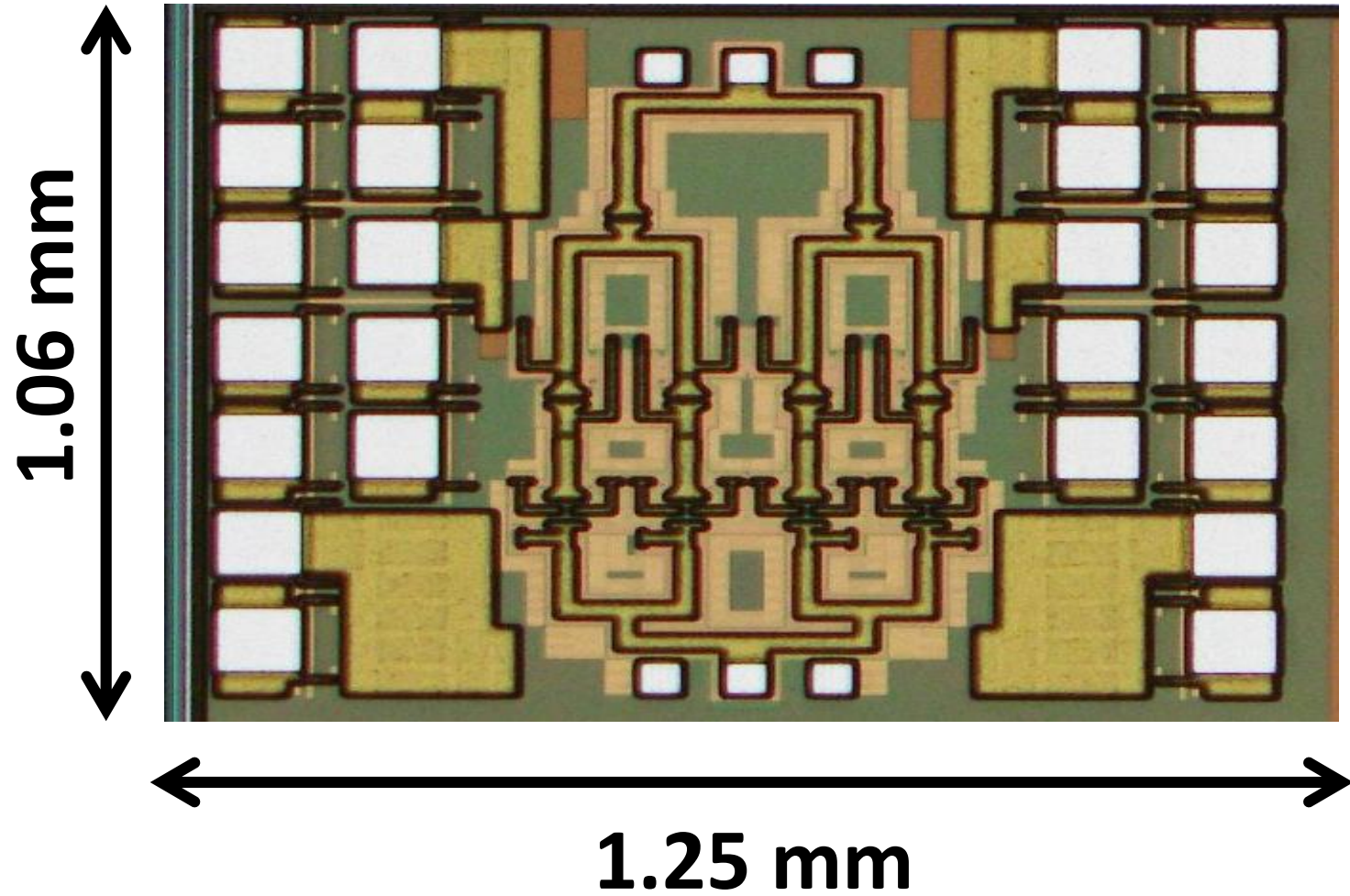

Measured Sparameters of 100 GHz PA chip

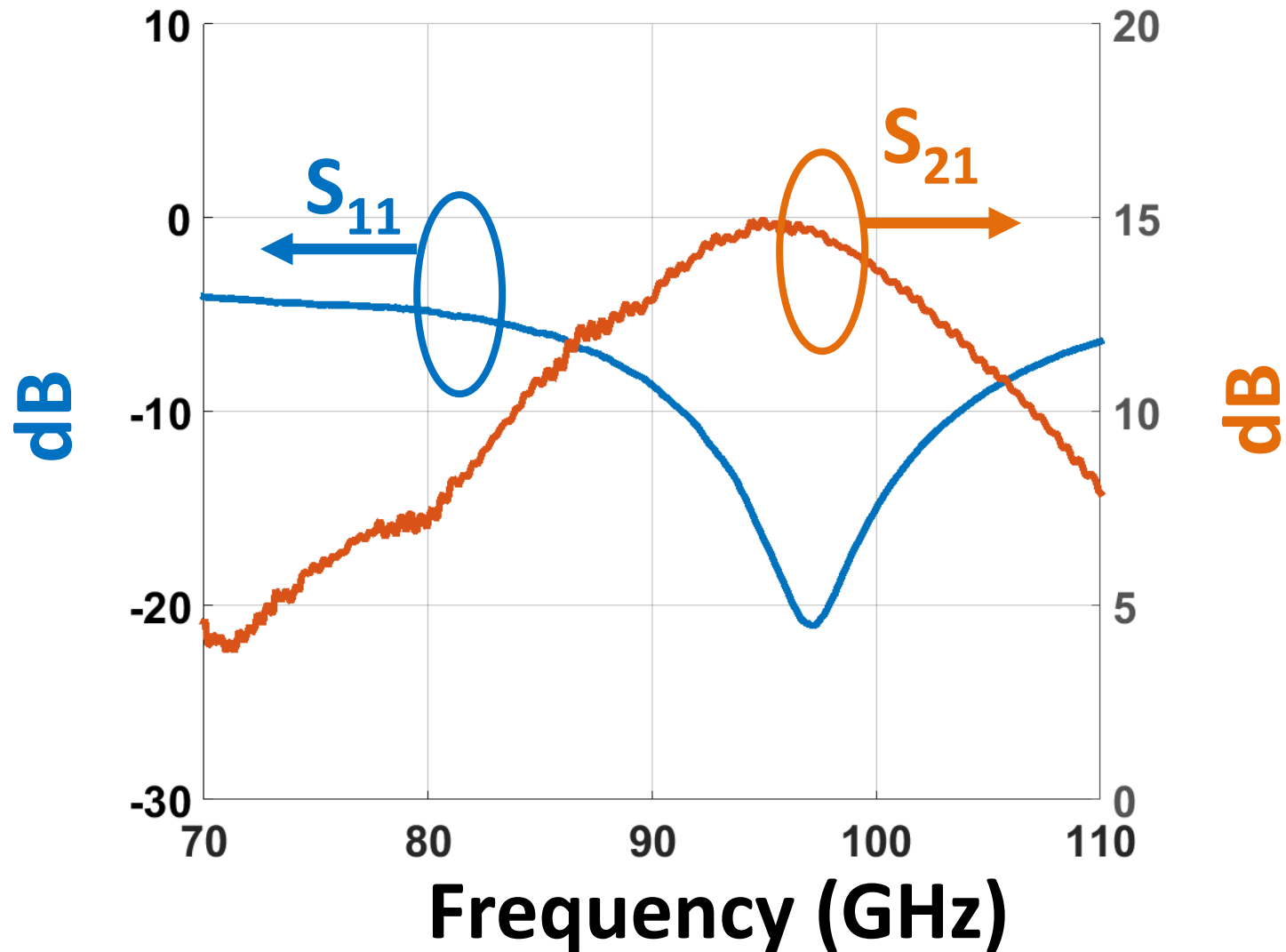


Acknowledgement

- All the members of IMRL, Princeton for technical discussions.
- National Science Foundation and Office of Naval Research.
- MOSIS and IBM for chip fabrication.

THANK YOU...

Passive Modelling

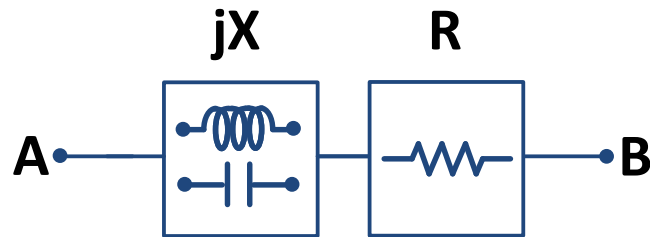


Series Model

$$Z_{AB} = R + jX$$

$$Y_{AB} = 1/Z_{AB} = a + jb$$

$$Q_s = |X/R| = |a/b|$$

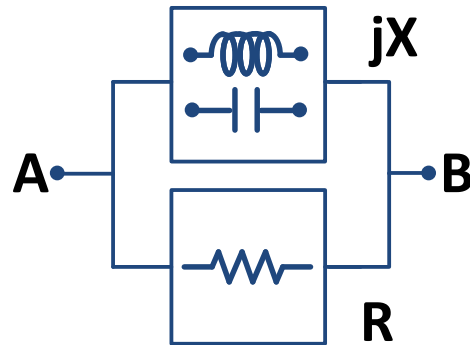


Parallel Model

$$Y_{AB} = 1/R + 1/jX = a + jb$$


$$Z_{AB} = 1/Y_{AB}$$

$$Q_p = |R/X| = |b/a|$$

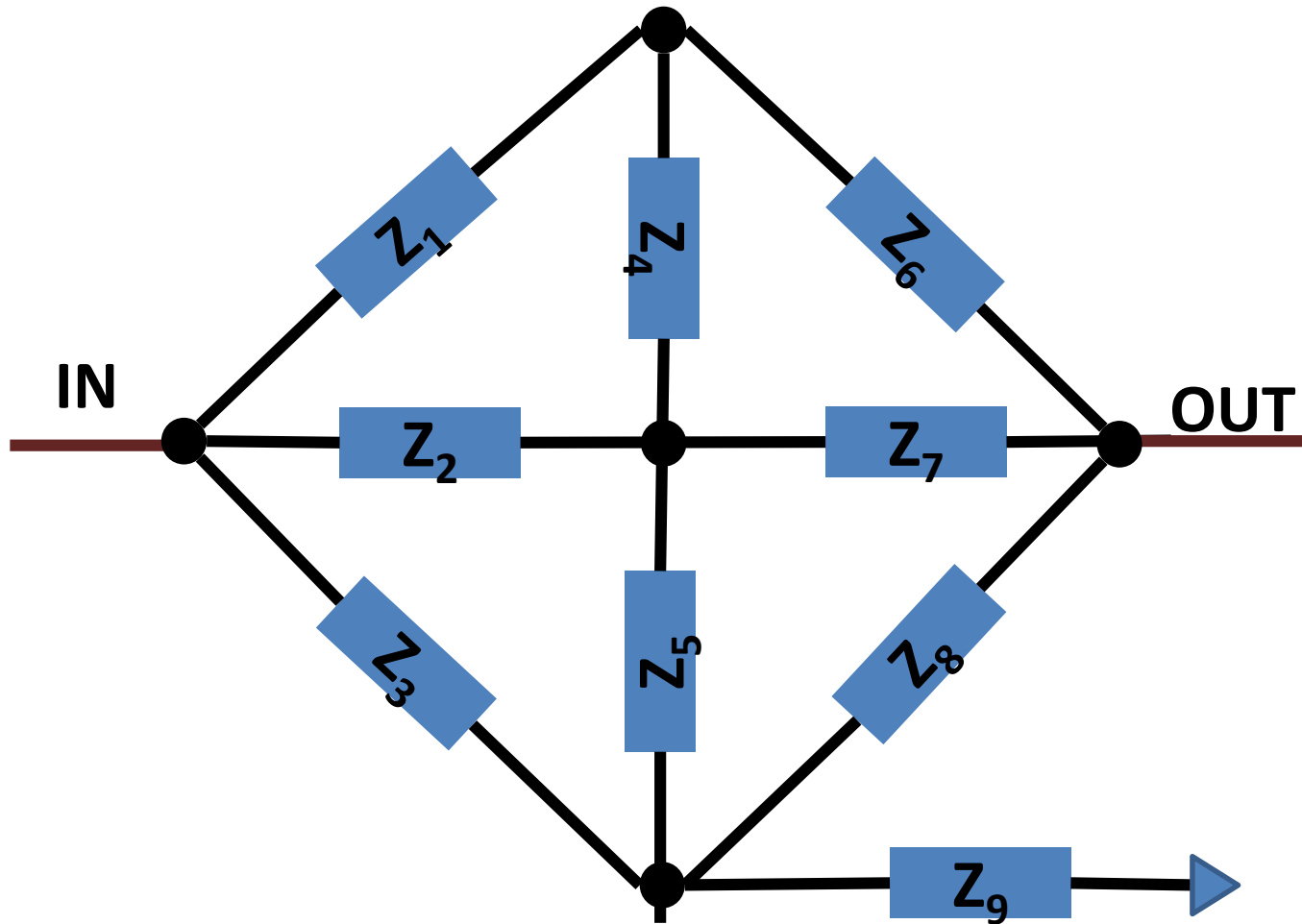
Complex circuit → Combination of Series / Parallel Passives





Delta to T conversion

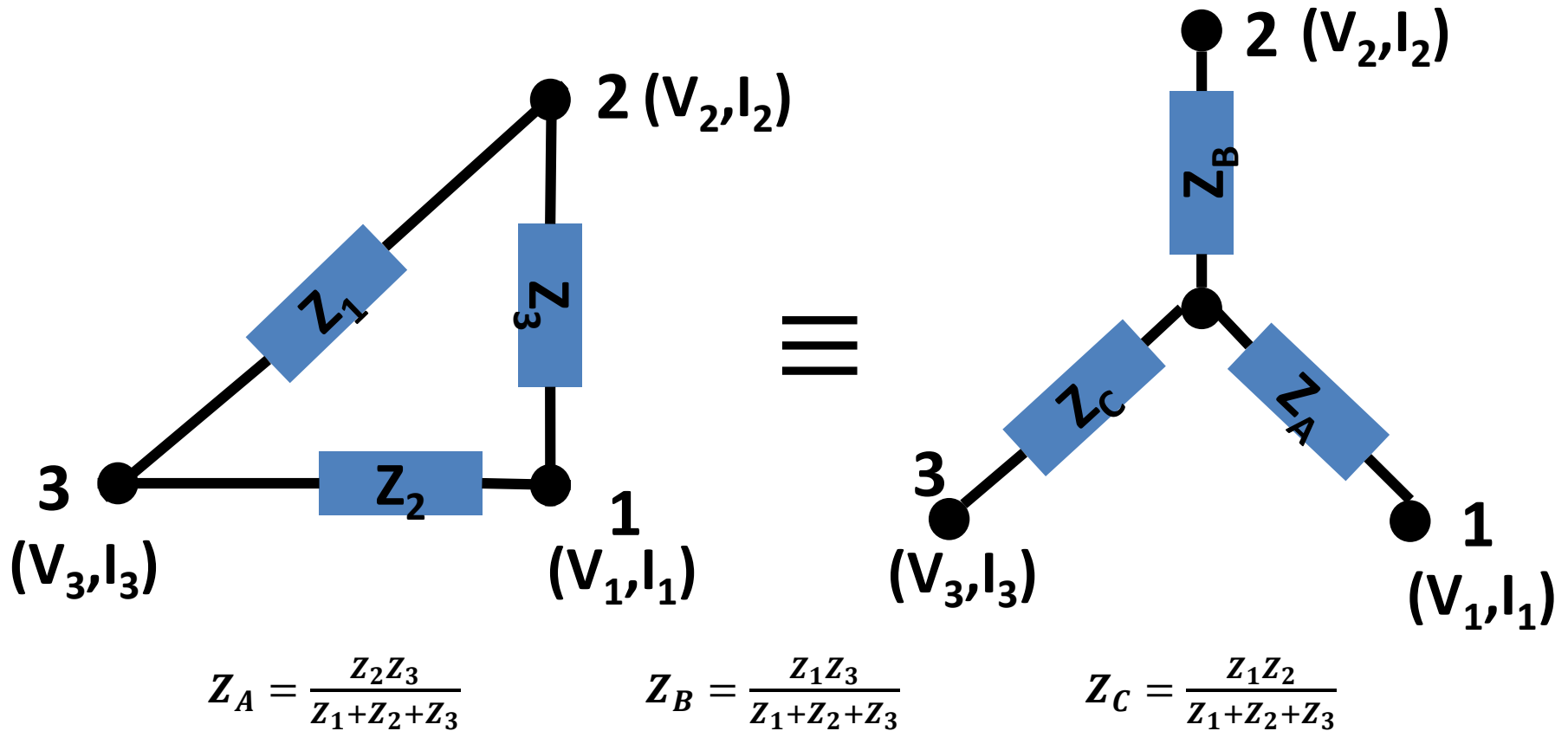


Complex Circuit

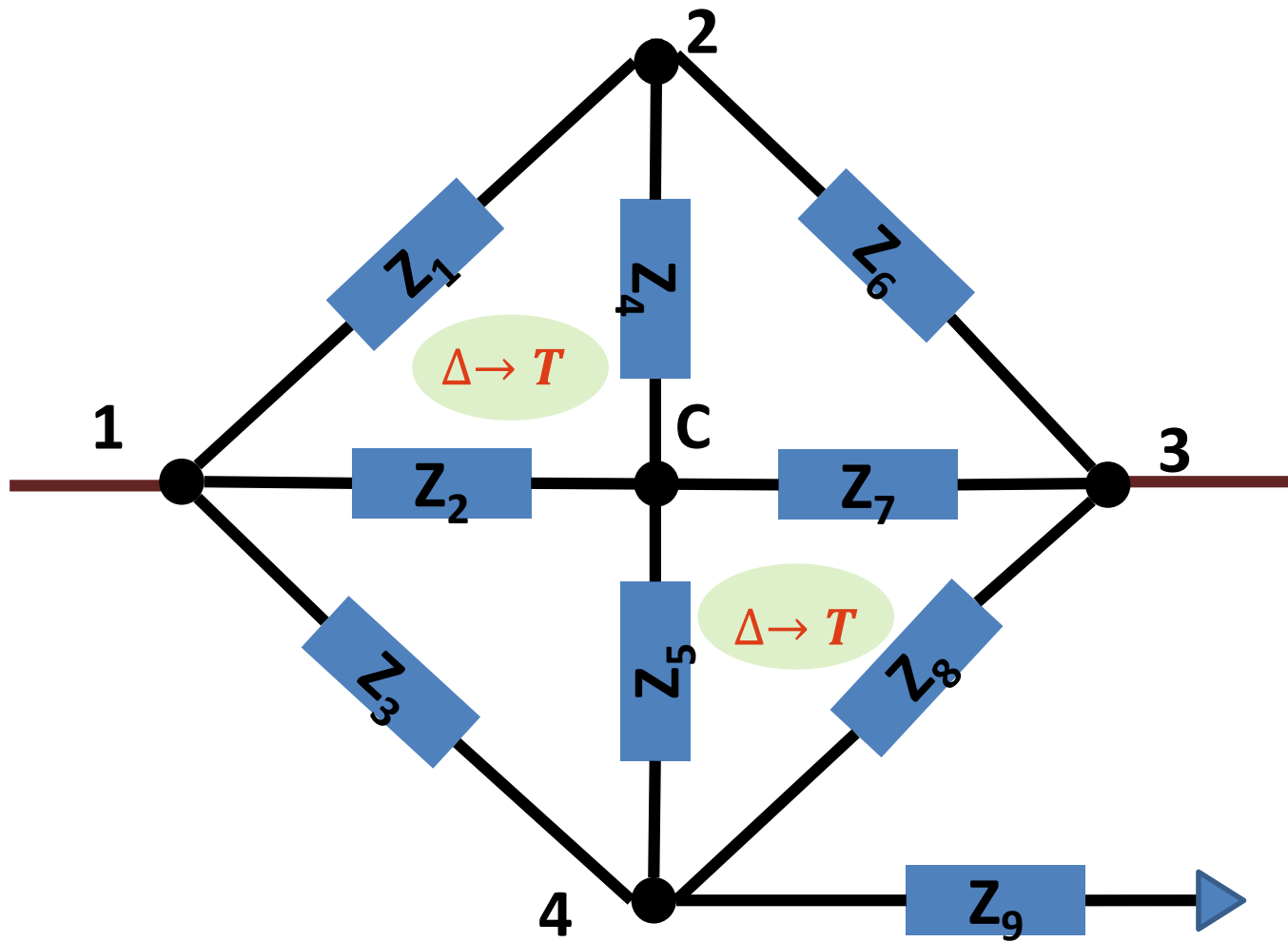


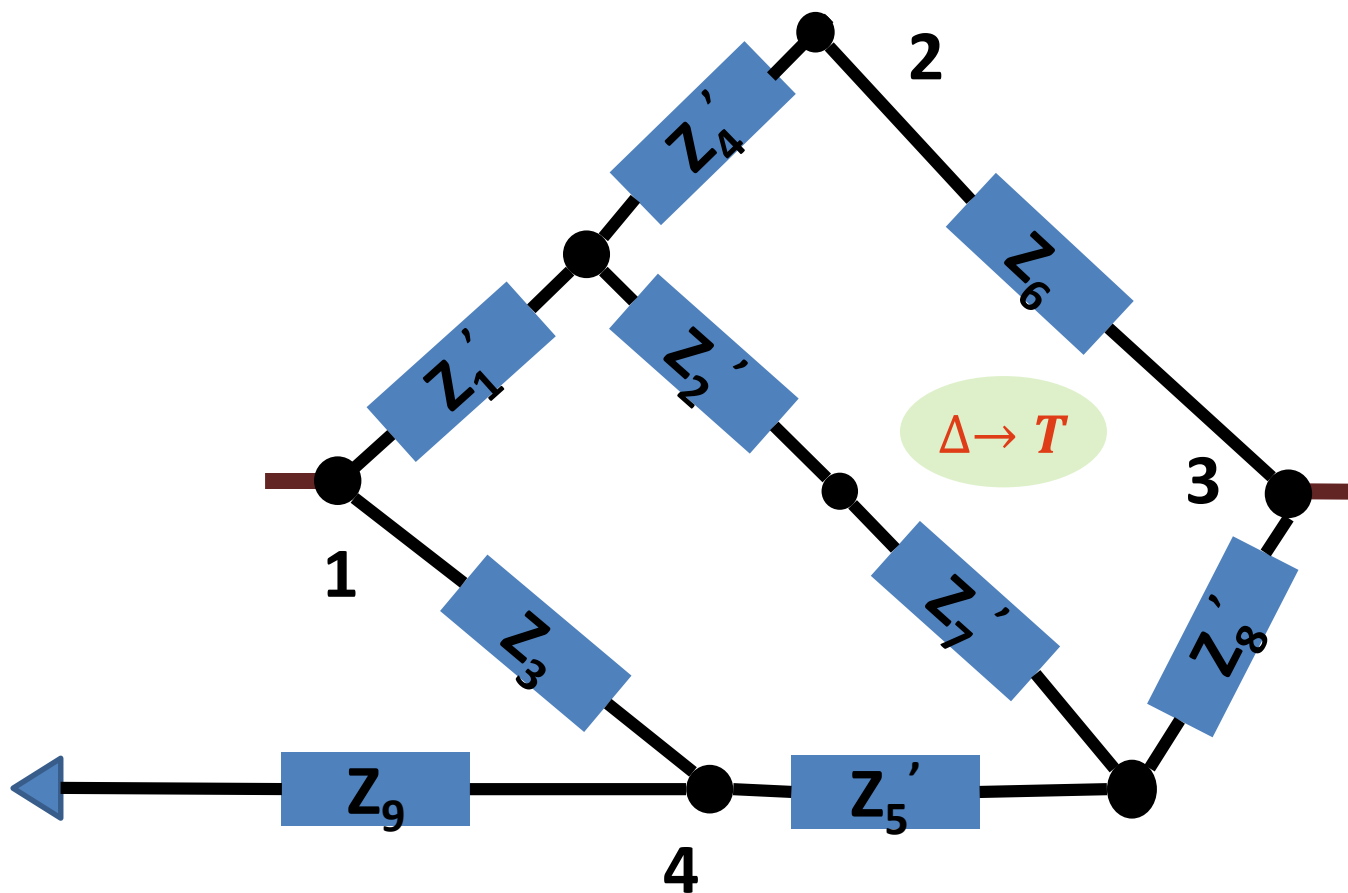

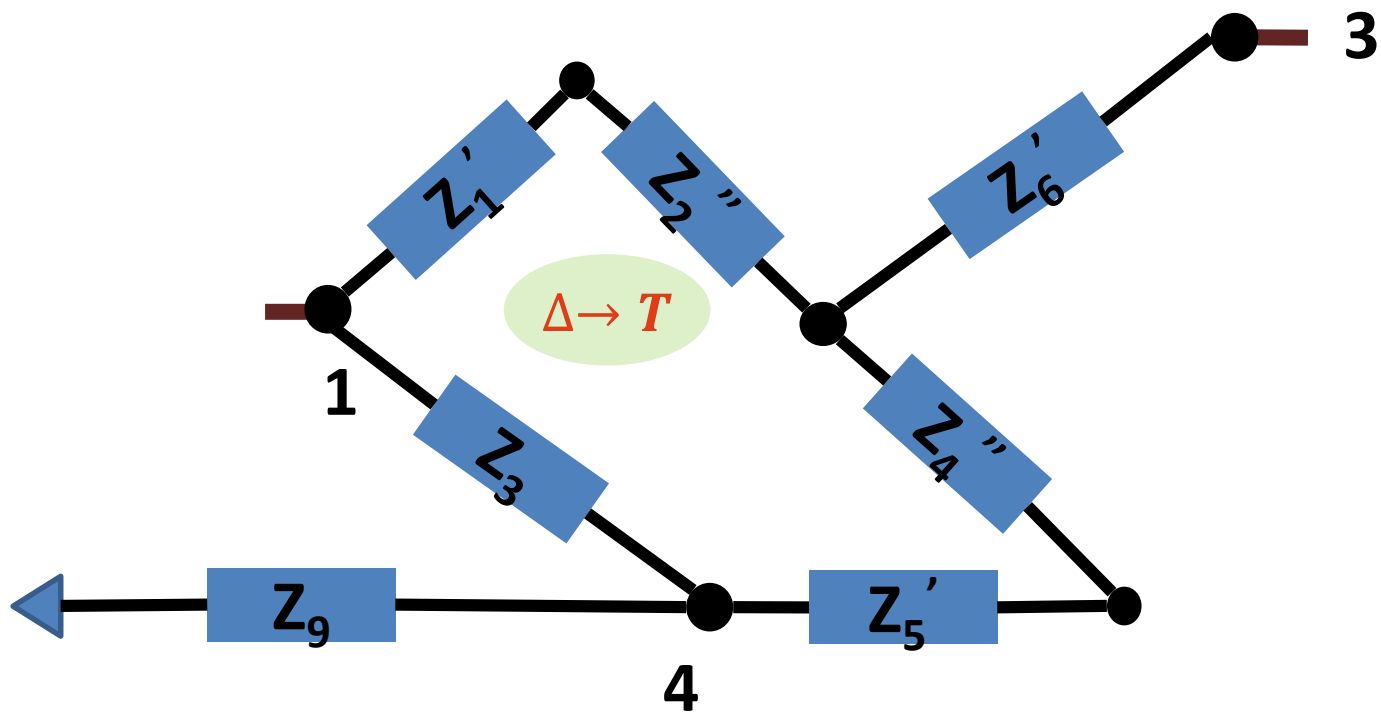

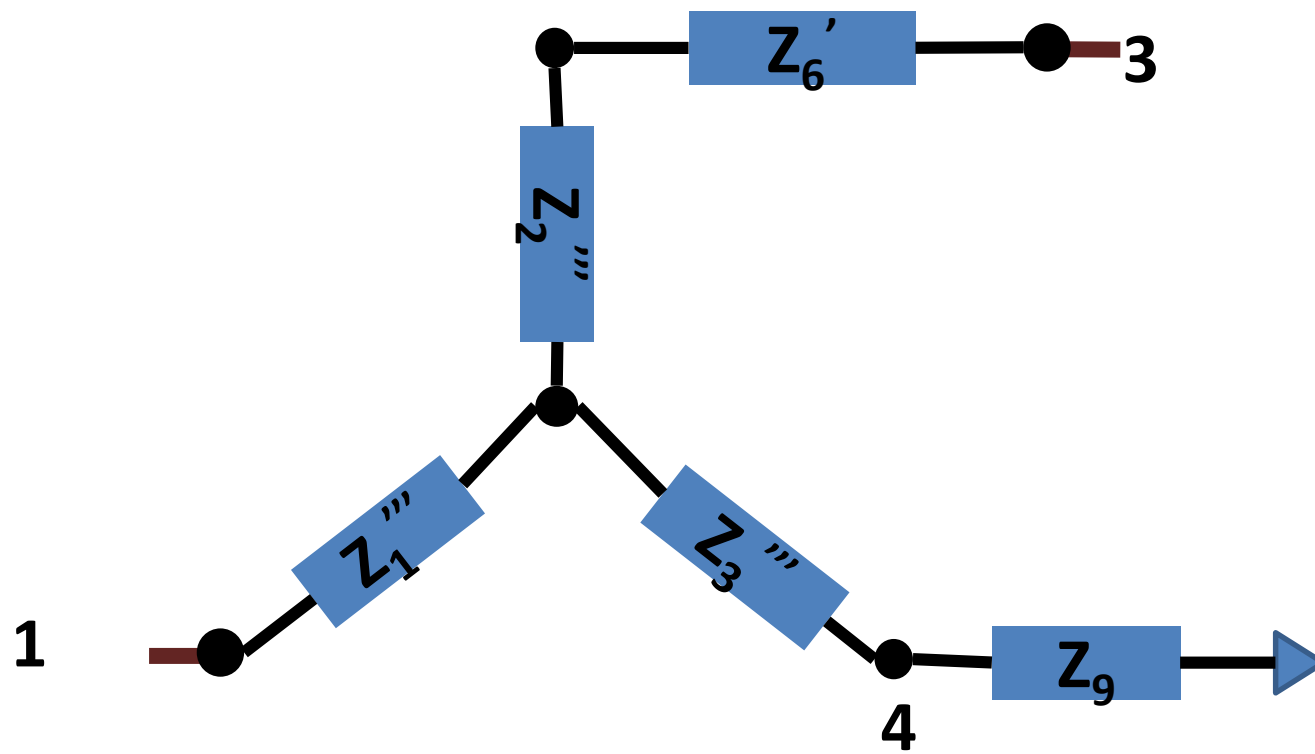

Reduced form of Complex Circuit

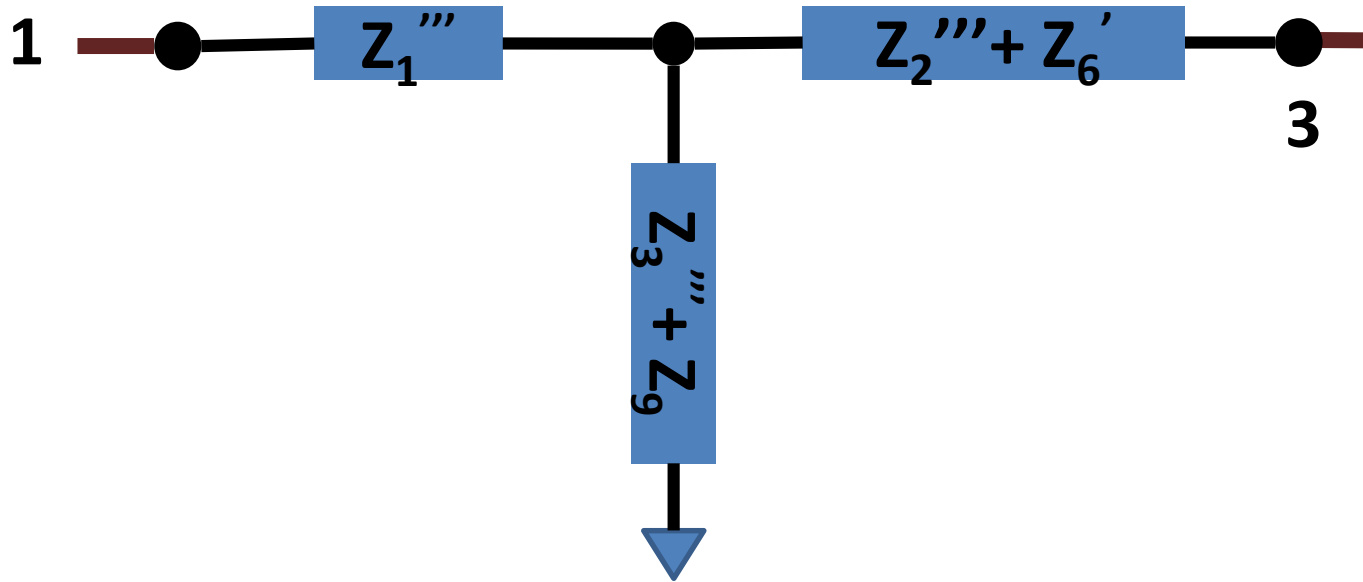

- Every complex combination of passives can be reduced to a combination of series / parallel passives